18/A/C/S-2/4/E

Booklet Series - A

033/231

PAPER-I **ELECTRICIAN** (THEORY) SEMESTER-II

TIME: 3 Hrs.

MARKS: 150

Note: - Attempt all the questions.

All questions carry equal marks.

This paper carries negative marking 25% marks will be deducted for each wrong answer.

- Choose the correct answer: The maximum value of sine wave of AC voltage is 10V. What is its RMS value? a) 1.414 V b) 6.060 V c) 7.070 V d) 14.140 V 2. Which of the following oscillators is suitable for frequencies in the range of mega hertz? a) RC phase shift b) Wien bridge c) Hartley d) Both (a) and (c) 3. In a BJT circuit a pnp transistor is replaced by npn transistor. To analyse the new circuita) All calculations done earlier have to be repeated b) Replace all calculated voltages by reverse values c) Replace all calculated currents by reverse values d) Replace all calculated voltages and currents by reverse values 4. When the value of capacitance is increased in series resonance circuit, the frequency willa) Decrease b) Increase c) No change d) Becomes zero
- The output indicated on the name plate of any motor is always the-5.
 - a) Gross power

b) Power drawn in volt amperes

c) Power drawn in watts

- d) Output power at the shaft
- To protect the diodes in a rectifier and capacitor input filter circuit it is necessary to use-6.
 - a) Surge resistor

b) Surge inductor

c) Surge capacitor

- d) Both (a) and (b)
- 7. The D.C shunt motor speed is to be varied from zero to above normal with reversing facility having inherent stability of speed at all loads. What speed control method is to be used?
 - a) Supply voltage speed control method
- b) Ward-Leonard system of speed control
- c) Shunt field control method
- d) Armature speed control method

- 8. An RC oscillator uses
 - a) One RC combination c) At last three RC combinations

- d) Either (a) or (b)

b) Two RC combinations



18/A/C/S-2/4/E

Booklet Series - A

033/231

9,	fault for this effect? a) Line voltage too high c) Pitted starter contact terminals	b) Short circuit of the field winding d) Wrong grade of carbon brushes	
10.	The gain of an FET amplifier can be change a) r_{m} c) R_{d}	ed by changing- b) g _m d) None of these	
4.4			
11.	The direction of rotation of a D.C motor is a) Fleming's right hand rule c) Ampere's right hand grip rule	b) Fleming's left hand rule d) Maxwell's cork screw rule	
12.	A 220V, DC machine has an armature resistance of 0.5 ohm. If the armature current is 20		
	amps, the induced emf when the machine w (i) Generator (ii) Motor will be respectively a) 220V, 210V c) 200V, 230V		
13.	 The D.C motor works on the principle that the- a) Current carrying conductor placed in a uniform magnetic field experiences a force on it b) Conductor moves when kept in a uniform magnetic field c) Magnetic field set up by varying current which produces force in the conductor 		
	d) Combined magnetic field set up by two c between them	surrent carrying conductors produces a force	
14.	A DC shunt motor is running on no-load. It the condition of the motor?	If the field winding gets opened, what will be	
	a) The motor will stopc) The motor will run at high speed	b) The motor will burn outd) The motor will make noise	
15.	The starting current of a 220V, 10 HP shunt motor having an armature resistance of ohms, without starter is		
	a) 11 amps c) 1100 amps	b) 110 amps d) 11000 amps	
16			
16.	The starting resistance of 3 point starter in I a) Parallel across the armature		
	c) Parallel across the field winding	b) Series with the armatured) Series with the field winding	
17.	The standard rated value of secondary current of current transformer as per IS 2705 (Part 1) – 1981 shall be either		
	a) 5 Ampere or 10 Ampere	b) 2.5 Ampere or 5 Ampere	
	c) 1.5 Ampere or 6 Ampere	d) 1 Ampere or 5 Ampere	

Contd...3/-



-3-

18/A/C/S-2/4/E

Booklet Series - A

033/231

	18.	The rated secondary voltage of a single pha	ise notential transformer is	
	10.	a) 240V	b) 230V	
		c) 115V	,	
		c) 113 v	d) 110V	
	19.	Efficiency of transformer is determined by	I knowing its input and output name. What is	
	17.		knowing its input and output power. What is	
		the unit used for input and output when		
		a) KVAR	b) KW	
		c) KVA	d) KWh	
	20.	The function of conservator in a transformed		
		a) To prevent flow of moisture into the tan	k	
		b) To prevent flow of air into the tank		
		c) To regulate the expansion and contraction	on of oil	
		d) To improve power factor		
		-) power lactor		
	21.	What will happen to 415V/240V 1KVA	transformer when it is connected to a D.C	
		supply?	transformer when it is connected to a D.C	
		a) The output will be 240V	L) The content will be 41537	
			b) The output will be 415V	
		c) The transformer may burn	d) Remain as it is-	
	00			
	22.	The EMF (E_S) equation of the transformer is		
		a) $E_S = 4.44 \phi_m f N_P Volt$	b) $E_S = 4.44 \phi_m N_S \text{ volt}$	
		c) $E_S = 4.44 \phi_m f N_S \text{ volt}$	d) $E_S = 4.44 \phi_m f \text{ volt}$	
	23.		acity power transformers. The purpose of the	
		Buchholz relay is to		
		a) Arrest the flow of moisture into the tank		
		b) Disconnect the transformer, when dead s	hort circuit fault occurs	
		c) Flow insulating oil from the conservator	tank	
		d) Control the level of oil tank	* WAAAA	
		a) constant the level of our think		
	24.	A 5KVA 400V/200V transformer delivers	a current of 25 Amps in secondary. What is	
		the current in primary side?	a current of 25 Amps in secondary. What is	
		a) 50 Amps	1) 05 4	
			b) 25 Amps	
		c) 17.5 Amps	d) 12.5 Amps	
		1- C 11 ti Ci ti i C (1)		
	2000	in the wave reconcation, if the input freque	ney is 50 Hz, then frequency at the output of	
		filter is-		
		a) 50 Hz	b) 0 Fz	
-		c) 100 Hz	d) 75 Hz	
	26.	In a CE amplifier circuit the ac voltage between	een enlitter and pround-	
7		a) Is very high	b) May be high or low	
		c) Is zero	d) Depends upon circuit 20 Signation	
			a) Dopones epon out at the garanous	
	21	Which material is used for wiring continue.	po breaka 9	
		c) Soth (A) and (R)	b) Copper	
		A rough (million track)	d)/None of these	•
			Contd4/-	
			created with	
		- RU (18)	Bittee PCF professional	
		80 10 9/40	download the free trial golfice at rictory. The property of the second s	

1

The state of the s

28.	When the coil moves at right angle to a) Oscillating c) Zero	b) Minimum d) Maximum		
29.	Which among these is a method of wa) Joint box c) Loop in system	b) Tee system d) All of these		
30.	The magnitude of the induced emf. at zero degree angle is given by the formula			
	E ₀ = BLV sin 0. a) Induced voltage b) Velocity of loop rotation c) Value of the magnetic flux density d) Velocity of the cutting force by magnetic flux			
31.	The direction of rotation of dc shunt a) The supply terminals	motor can be reversed by interchanging- b) The field terminals		
7	c) The armature terminals only	d) Either field or armature terminals		
32.	With the increase in the speed of a dc motor- a) Both back emf as well as line current increase b) Both back emf and line current fall c) Back emf increases but the line current falls d) Back emf falls and line current increases			
33.	According to the IS recommendation the clearance between the bottom part of the ceiling fan and the floor should not be less than —			
		b) 2.0 m		
	c) 2.25 m	d) 2.40 m		
34.	connected is –	n domestic wiring unless the appliance to be		
	N	b) Double insulated		
	c) Controlled by ELCB	d) Controlled by MCB		
35.	D.C. shunt motors are commonly used in-			
	a) Cranesc) Elevators	b) Electric traction d) Lathe machines		
36.	Size of the plate electrode used for plate earthing should not be less than -			
	a) 12.5 x 12.5 x 0.12 cm	b) 20 x 20 x 0.25 cm d) 60 x 60 x 0.315 cm		
37.	In which principle, the earth resistance tester does work?			
	\	b) Fall of potential method d) Fall of conductivity method		
	0- F	-, or consecuting monitor		

18/A/C/S-2/4/E

Booklet Series - A

033/231

- 38. What is the function of current reverses which is used in earth resistance tester?
 - a) To convert AC voltage into DC voltage
 - b) To convert DC voltage into AC voltage
 - c) To reduce the vibration of the pointer
 - d) To reduce the effect of electrolytic emf
- You have to select a PF meter suitable for connecting in a circuit for PF measurements on 39. what basis you will select its range?
 - a) Suitability for the type of load (Inductive / capacitive/ Resistance)
 - b) PF range of meter (Lagging / Leading)Unity)
 - c) Voltage and current range of meter suitable to load
 - d) Current and PF range of meter matching to load
- 40. Ammeters used for current measurements in circuits with short over load time, differs from other application. Ammeter used in short overload time circuit have
 - a) Non-linear scale

b) Extended scale

c) Linear scale

- d) Fine scale
- 41. Instruments which must not be used in the circuit when the power is ON are
 - a) Watt meter and PF meter

b) Frequency meter and Tong tester

c) Phase sequence meter and energy meter d) Ohmmeter and Megger

- 42. Two types of multimeters are in use. Analog type and Digital type. Chose the correct statement applicable for both the types. Both the meters –
 - a) Have moving elements, hence must be used in horizontal position
 - b) Can be used for current and voltage measurement without battery
 - c) Need manual zero setting for resistance measurement
 - d) Need battery for resistance measurements
- 43. Power drawn by a welding shop which has 3 phase, 415 V, 50Hz supply has to be measured. The following loads are connected. (a) 2 welding set of each 5KVA across L1,L2 and L3. (b) One set of 5KVA across L2 and L3. What is the type of wattmeter you would choose for this measurement?
 - a) 3 element 3 wire type 3 phase wattmeter
 - b) One single phase wattmeter connected between any two phase and multiply reading by
 - c) 3 element 4 wire 3 phase watt meter
 - d) 2 element types 3 phase watt meter
- 44. D.C shunt motor is also called as
 - a) Constant flux motor

- b) Constant voltage motor
- c) Variable voltage motor
- d) Constant current motor
- To keep the continuity of serial lamp set circuit even across the fuse bulb it is customary 45. to connect a device across the each bulb as precaution. What is the name of such device?
 - a) NTC thermistors

b) PTC thermistors

c) Voltage dependent resistor

d) Flasher

Contd...6/-

