

ELECTRONIC MECHANIC

NSQF LEVEL - 5

2nd Semester

TRADE PRACTICAL

SECTOR: Electronics and Hardware



Directorate General of Training

DIRECTORATE GENERAL OF TRAINING
MINISTRY OF SKILL DEVELOPMENT & ENTREPRENEURSHIP
GOVERNMENT OF INDIA



**NATIONAL INSTRUCTIONAL
MEDIA INSTITUTE, CHENNAI**

Post Box No. 3142, CTI Campus, Guindy, Chennai - 600 032

Sector : Electronics & Hardware

Duration : 2 - Year

Trade : Electronic Mechanic 2nd Semester - Trade Practical - NSQF level 5

Copyright ©2018 National Instructional Media Institute, Chennai

First Edition : November 2018 Copies : 1,000

First Reprint : February 2019 Copies : 2,000

Rs.185/-

All rights reserved.

No part of this publication can be reproduced or transmitted in any form or by any means, electronic or mechanical, including photocopy, recording or any information storage and retrieval system, without permission in writing from the National Instructional Media Institute, Chennai.

Published by:

NATIONAL INSTRUCTIONAL MEDIA INSTITUTE
P. B. No.3142, CTI Campus, Guindy Industrial Estate,
Guindy, Chennai - 600 032.
Phone : 044 - 2250 0248, 2250 0657, 2250 2421
Fax : 91 - 44 - 2250 0791
email : chennai-nimi@nic.in, nimi_bsnl@dataone.in
Website: www.nimi.gov.in

FOREWORD

The Government of India has set an ambitious target of imparting skills to 30 crores people, one out of every four Indians, by 2020 to help them secure jobs as part of the National Skills Development Policy. Industrial Training Institutes (ITIs) play a vital role in this process especially in terms of providing skilled manpower. Keeping this in mind, and for providing the current industry relevant skill training to Trainees, ITI syllabus has been recently updated with the help of Mentor Councils comprising various stakeholder's viz. Industries, Entrepreneurs, Academicians and representatives from ITIs.

The National Instructional Media Institute (NIMI), Chennai, has now come up with instructional material to suit the revised curriculum for **Electronic Mechanic 2nd Semester Trade Practical NSQF Level - 5 in Electronics & Hardware Sector under semester pattern**. The NSQF Level - 5 Trade Practical will help the trainees to get an international equivalency standard where their skill proficiency and competency will be duly recognized across the globe and this will also increase the scope of recognition of prior learning. NSQF Level - 5 trainees will also get the opportunities to promote life long learning and skill development. I have no doubt that with NSQF Level - 5 the trainers and trainees of ITIs, and all stakeholders will derive maximum benefits from these IMPs and that NIMI's effort will go a long way in improving the quality of Vocational training in the country.

The Executive Director & Staff of NIMI and members of Media Development Committee deserve appreciation for their contribution in bringing out this publication.

Jai Hind

RAJESH AGGARWAL

Director General/ Addl. Secretary
Ministry of Skill Development & Entrepreneurship,
Government of India.

New Delhi - 110 001

PREFACE

The National Instructional Media Institute (NIMI) was established in 1986 at Chennai by then Directorate General of Employment and Training (D.G.E & T), Ministry of Labour and Employment, (now under Directorate General of Training, Ministry of Skill Development and Entrepreneurship) Government of India, with technical assistance from the Govt. of the Federal Republic of Germany. The prime objective of this institute is to develop and provide instructional materials for various trades as per the prescribed syllabi under the Craftsman and Apprenticeship Training Schemes.

The instructional materials are created keeping in mind, the main objective of Vocational Training under NCVT/NAC in India, which is to help an individual to master skills to do a job. The instructional materials are generated in the form of Instructional Media Packages (IMPs). An IMP consists of Theory book, Practical book, Test and Assignment book, Instructor Guide, Audio Visual Aid (Wall charts and Transparencies) and other support materials.

The trade practical book consists of series of exercises to be completed by the trainees in the workshop. These exercises are designed to ensure that all the skills in the prescribed syllabus are covered. The trade theory book provides related theoretical knowledge required to enable the trainee to do a job. The test and assignments will enable the instructor to give assignments for the evaluation of the performance of a trainee. The wall charts and transparencies are unique, as they not only help the instructor to effectively present a topic but also help him to assess the trainee's understanding. The instructor guide enables the instructor to plan his schedule of instruction, plan the raw material requirements, day to day lessons and demonstrations.

IMPs also deals with the complex skills required to be developed for effective team work. Necessary care has also been taken to include important skill areas of allied trades as prescribed in the syllabus.

The availability of a complete Instructional Media Package in an institute helps both the trainer and management to impart effective training.

The IMPs are the outcome of collective efforts of the staff members of NIMI and the members of the Media Development Committees specially drawn from Public and Private sector industries, various training institutes under the Directorate General of Training (DGT), Government and Private ITIs.

NIMI would like to take this opportunity to convey sincere thanks to the Directors of Employment & Training of various State Governments, Training Departments of Industries both in the Public and Private sectors, Officers of DGT and DGT field institutes, proof readers, individual media developers and coordinators, but for whose active support NIMI would not have been able to bring out this materials.

Chennai - 600 032

**R. P. DHINGRA
EXECUTIVE DIRECTOR**

ACKNOWLEDGEMENT

National Instructional Media Institute (NIMI) sincerely acknowledges with thanks for the co-operation and contribution extended by the following Media Developers and their sponsoring organisations to bring out this Instructional Material (**Trade Practical**) for the trade of **Electronic Mechanic** under Electronics and Hardware sector for ITIs.

MEDIA DEVELOPMENT COMMITTEE MEMBERS

Smt. K. Arul selvi	—	Training officer NSTI (W), Trichy.
Shri. C. Anand	—	Vocational Instructor Govt. ITI for women, Puducherry.
Shri. A. Jayaraman	—	Training officer (Retd.), Govt. of India, CTI, Chennai-32.
Shri. R.N. Krishnasamy	—	Vocational Instructor (Retd.), Govt. of India, VRC, Chennai-32.
Shri. S. Gopalakrishnan	—	Assistant Manager, Co-ordinator, NIMI, Chennai - 32.

NIMI records its appreciation for the Data Entry, CAD, DTP operators for their excellent and devoted services in the process of development of this Instructional Material.

NIMI also acknowledges with thanks the invaluable efforts rendered by all other NIMI staff who have contributed towards the development of this Instructional Material.

NIMI is also grateful to everyone who has directly or indirectly helped in developing this Instructional Material.

INTRODUCTION

TRADE PRACTICAL

The trade practical manual is intended to be used in workshop . It consists of a series of practical exercises to be completed by the trainees during the Second Semester course of the Electronic Mechanic Trade supplemented and supported by instructions/ informations to assist in performing the exercises. These exercises are designed to ensure that all the skills in compliance with NSQF Level-5 prescribed syllabus are covered.

The manual is divided into ten modules. The distribution of time for the practical in the ten modules are given below.

Module 1	Transistor Amplifier	75 Hrs
Module 2	Oscillators	25 Hrs
Module 3	Wave shaping circuits	25 Hrs
Module 4	Power Electronic components	50 Hrs
Module 5	MOSFET & IGBT	25 Hrs
Module 6	Opto-Electronics	25 Hrs
Module 7	Basic Gates, Combinational circuits, Flip Flops	75 Hrs
Module 8	Electronic Circuit Simulator	50 Hrs
Module 9	Counter & Shift Registers	75 Hrs
Module 10	Op - Amp & Timer 555 Applications	100 Hrs
	Project work	50 Hrs
	Total	575 Hrs

The skill training in the computer lab is planned through a series of practical exercises centred around some practical project. However, there are few instances where the individual exercise does not form a part of project.

While developing the practical manual a sincere effort was made to prepare each exercise which will be easy to understand and carry out even by below average trainee. However the development team accepts that there is a scope for further improvement. NIMI, looks forward to the suggestions from the experienced training faculty for improving the manual.

TRADE THEORY

The manual of trade theory consists of theoretical information for the First Semester course of the Electronic Mechanic Trade. The contents are sequenced according to the practical exercise contained in the manual on Trade practical. Attempt has been made to relate the theoretical aspects with the skill covered in each exercise to the extent possible. This co-relation is maintained to help the trainees to develop the perceptual capabilities for performing the skills.

The Trade Theory has to be taught and learnt along with the corresponding exercise contained in the manual on trade practical. The indicating about the corresponding practical exercise are given in every sheet of this manual.

It will be preferable to teach/learn the trade theory connected to each exercise at least one class before performing the related skills in the shop floor. The trade theory is to be treated as an integrated part of each exercise.

The material is not the purpose of self learning and should be considered as supplementary to class room instruction.

CONTENTS

Exercise No.	Title of the Exercise	Page No.
	Module 1: Transistor Amplifier	
2.1.102	Identify different transistors with respect to different package type, B-E-C pins, power, switching transistor, heatsink etc	1
2.1.103	Test the condition of a given transistor using Ohm-meter	4
2.1.104	Measure and Plot input and output characteristics of a transistor CE amplifier	7
2.1.105	Construct and test a transistor based switching circuit to control a relay (use relays of different coil voltages and transistors of different β)	10
2.1.106	Construct and test fixed bias, emitter bias, and voltage divider bias transistor amplifier	12
2.1.107	Construct and test a CE amplifier with and without emitter bypass capacitors	16
2.1.108	Construct and test a Common Base amplifier	20
2.1.109	Construct and test a Common Collector/Emitter Follower amplifier	23
2.1.110	Construct and test a Darlington amplifier	26
2.1.111	Construct and a two stage test RC-coupled Amplifier	29
2.1.112	Construct and test class-B complementary push-pull amplifier	31
2.1.113	Construct and test Class C Tuned Amplifier	33
	Module 2: Oscillators	
2.2.114	Demonstrate Colpitt's oscillator, Hartley oscillator circuits and compare the output frequency of the oscillator by CRO	35
2.2.115	Construct and test RC phase-shift oscillator circuits	37
2.2.116	Construct and test a crystal oscillator circuit	39
2.2.117	Demonstrate Astable, Monostable and Bistable multivibrator using circuits transistors	40
	Module 3: Wave shaping circuits	
2.3.118	Construct and test shunt clipper	43
2.3.119	Construct and test series and dual clipper circuit using diodes	45
2.3.120	Construct and test clamper circuit using diodes	47
2.3.121	Construct and test zener diode as a peak clipper	49

Exercise No.	Title of the Exercise	Page No.
	Module 4: Power Electronic components	
2.4.122	Identify different power electronic components, their specification and terminals	50
2.4.123	Construct and test a FET Amplifier	53
2.4.124	Construct and test a circuit of SCR using UJT triggering	55
2.4.125	Identify different heatsinks used in SCRs	57
2.4.126	Construct a snubber circuit for protecting SCR use freewheeling diode to reduce back emf	59
2.4.127	Construct a jig circuit to test DIAC	60
2.4.128	Construct a simple dimmer circuit using TRIAC	62
2.4.129	Construct UJT based free running oscillator and change its frequency	64
	Module 5: MOSFET & IGBT	
2.5.130	Identify various power MOSFETs by its number and test by using multimeter	66
2.5.131	Identify different heatsinks used with various power MOSFET devices	67
2.5.132	Construct MOSFET test circuit with a small load	69
2.5.133	Identify IGBTs by their numbers and test by using multimeter	70
2.5.134	Construct IGBT test circuit with a small load	71
	Module 6: Opto-Electronics	
2.6.135	Test LEDs with DC supply and measure voltage drop and current using multimeter	72
2.6.136	Construct a circuit to test photo voltaic cell	73
2.6.137	Construct a circuit to switch a lamp load using photo diode	75
2.6.138	Construct a circuit to switch a lamp load using photo transistor	76
2.6.139	Identify Opto coupler input and output terminals and measure the quantum of Isolation between input/output terminals and operate a relay by connecting a switch	77
	Module 7: Basic Gates, Combinational circuits, Flip Flops	
2.7.140	Identify different logic gates (AND, OR, NAND, NOR, EX-OR, EX- NOR, NOT ICs) by the number printed on them	79
2.7.141	Verify the truth tables of all logic Gate ICs by connecting switches and LEDs	80
2.7.142	Construct and verify the truth table of all the gates using NAND and NOR gates	84
2.7.143	Use digital IC tester to test the various digital ICs (TTL and CMOS)	91
2.7.144	Construct Half Adder circuit using ICs and verify the truth table	93

Exercise No.	Title of the Exercise	Page No.
2.7.145	Construct Full adder with two Half adder circuit using ICs and verify the truth table	94
2.7.146	Construct the adder cum subtractor circuit and verify the result	95
2.7.147	Construct and test a 2 to 4 Decoder	97
2.7.148	Construct and test a 4 to 2 Encoder	98
2.7.149	Construct and test a 4 to 1 Multiplexer	99
2.7.150	Construct and test a 1 to 4 Demultiplexer	101
2.7.151	Identify different Flip-Flop ICs by the number printed on them	103
2.7.152	Construct and test four bit latch using 7475	104
2.7.153	Construct and test R-S Flip-Flop using IC 7400 with clock and without clock pulse	106
2.7.154	Verify the truth tables of Flip-Flop ICs (RS, D, T, JK, MSJK) by connecting switches and LEDs	108
	Module 8: Electronic Circuit Simulator	
2.8.155	Prepare simple digital and electronic circuits using the software	112
2.8.156	Simulate and test the prepared digital and analog circuits	119
2.8.157	Convert the prepared circuit into a layout diagram	121
2.8.158	Prepare simple, power electronic and domestic electronic circuit using simulation software	123
	Module 9: Counter & Shift Registers	
2.9.159	Construct and test a four bit asynchronous binary counter using IC 7493	127
2.9.160	Construct and test 7493 as a modulus - 12 counter	128
2.9.161	Construct and test a four bit synchronous binary counter using IC 74163	130
2.9.162	Construct and test synchronous Decade counter	132
2.9.163	Construct and test an UP/DOWN synchronous decade counter using 74190 and monitor the output on LEDs	133
2.9.164	Identify and test common anode and common cathode seven segment LED display using multimeter	135
2.9.165	Display the two digit count value on seven segment display using decoder/driver ICs	136
2.9.166	Construct a shift register using RS/D/JK Flip- Flop and verify the result	139
2.9.167	Construct a test four bit SIPO register	142
2.9.168	Construct and test four bit PIPO register	143
2.9.169	Construct and test bidirectional shift register	144

Exercise No.	Title of the Exercise	Page No.
	Module 10: Op-Amp & Timer 555 Applications	
2.10.170	Use analog IC tester to test various analog ICs	147
2.10.171	Construct and test various Op-Amp circuits Inverting, Non-inverting, Summing Amplifiers	149
2.10.172	Construct and test Differentiator and integrator	152
2.10.173	Construct and test a zero crossing detector	154
2.10.174	Construct and test instrumentation amplifier	155
2.10.175	Construct and test a Binary weighted and R-2R Ladder type Digital-to-Analog converters	156
2.10.176	Construct and test Astable multivibrator circuit using IC 555	158
2.10.177	Construct and test Monostable multivibrator circuit using IC 555	160
2.10.178	Construct and test VCO (V to F converter) using IC 555	162
2.10.179	Construct and test 555 timers as pulse width modulator	163

LEARNING/ ASSESSABLE OUTCOME

On completion of this book you shall be able to

- **Construct, test and verify the input/output characteristics of various analog circuits.**
- **Plan and construct different power electronic circuits and analyze the circuit functioning.**
- **Select the appropriate optoelectronic components and verify the characteristics in different circuits.**
- **Simulate and analyze the analog and digital circuits using Electronic simulator software.**
- **Identify, place, solder, desolder and test different SMD discrete components and ICs package with due care and following safety norms using proper tools/setup.**
- **Construct and test different circuits using ICs 741 Operational Amplifiers & ICs 555 Timer, Linear integrated circuits and Execute the result.**

SYLLABUS FOR ELECTRONIC MECHANIC TRADE

SECOND SEMESTER

Duration: 06 Months

Week No.	Learning outcome Reference	Professional Skills (Trade Practical) With indicative hours	Professional Knowledge (Trade Theory) with respect to different
27	<ul style="list-style-type: none"> Construct, test and verify the input/ output characteristics of various analog circuits. 	Transistor 102. Identify different transistors with respect to different package type, B-E-C pins, power, switching transistor, heat sinks etc. (5 hrs) 103. Test the condition of a given transistor using ohm-meter. (5 hrs) 104. Measure and plot input and output characteristics of a CE amplifier. (7 hrs) 105. Construct and test a transistor based switching circuit to control a relay (use Relays of different coil voltages and Transistors of different β) (8 hrs)	Construction, working of a PNP and NPN Transistors, purpose of E, B & C Terminals. Significance of α , β and relationship of a Transistor. Need for Biasing of Transistor. VBE, VCB, VCE, IC, IB, Junction Temperature, junction capacitance, frequency of operation. Transistor applications as switch and amplifier. Transistor input and output characteristics. Transistor power ratings & packaging styles and use of different heat sinks.
28-29	<ul style="list-style-type: none"> Construct, test and verify the input/ output characteristics of various analog circuits. 	Amplifier 106. Construct and test fixed-bias, emitter-bias and voltage divider-bias transistor amplifier. (12 hrs) 107. Construct and Test a common emitter amplifier with and without bypass capacitors (5 hrs) 108. Construct and Test common base amplifier. (5 hrs) 109. Construct and Test common collector/emitter follower amplifier. (5 hrs) 110. Construct and Test Darlington amplifier. (5 hrs) 111. Construct and test a two stage RC Coupled amplifier. (5 hrs) 112. Construct and test a Class B complementary push pull amplifier. (8 hrs) 113. Construct and test class C Tuned amplifier. (5 hrs)	Different types of biasing, various configurations of transistor (C-B, C-E & C-C), their characteristics and applications. Transistor biasing circuits and stabilization Techniques. Classification of amplifiers according to frequency, mode of operation and methods of coupling. Voltage amplifiers - voltage gain, loading effect. Single stage CE amplifier and CC amplifier. Emitter follower circuit and its advantages. RC coupled amplifier, Distinguish between voltage and power amplifier, Push pull amplifier and class C tuned amplifier. Alpha, beta, voltage gain, Concept of dB dBm. Feedback and its types.
30	<ul style="list-style-type: none"> Construct, test and verify the input/ output characteristics of various analog circuits. 	Oscillators 114. Demonstrate Colpitts oscillator, Hartley oscillator circuits and compare the output frequency of the oscillator by CRO. (7 hrs) 115. Construct and test a RC phase shift oscillator circuits. (5 hrs) 116. Construct and test a crystal oscillator circuits. (5 hrs)	Introduction to positive feedback and requisites of an oscillator. Study of Colpitts, Hartley, Crystal and RC oscillators. Types of multi vibrators and study of circuit diagrams.

		117. Demonstrate Astable, monostable, bistable circuits using transistors. (8 hrs)	
31	<ul style="list-style-type: none"> Construct, test and verify the input/ output characteristics of various analog circuits 	Wave shaping circuits 118. Construct and test shunt clipper. (6 hrs) 119. Construct and test series and dual clipper circuit using diodes. (7 hrs) 120. Construct and test clamper circuit using diodes. (5 hrs) 121. Construct and test Zener diode as a peak clipper. (7 hrs)	Diode shunt clipper circuits, Clamping / limiting circuits and Zener diode as peak clipper, uses their applications.
32-33	<ul style="list-style-type: none"> Plan and construct different power electronic circuits and analyse the circuit functioning. 	Power Electronic Components 122. Identify different power electronic components, their specification and terminals. (6 hrs) 123. Construct and test a FET Amplifier. (6 hrs) 124. Construct a test circuit of SCR using UJT triggering. (7 hrs) 125. Identify different heat sinks used in SCRs. (3 hrs) 126. Construct a snubber circuit for protecting SCR use freewheeling diode to reduce back emf. (7 hrs) 127. Construct a jig circuit to test DIAC. (7 hrs) 128. Construct a simple dimmer circuit using TRIAC. (7 hrs) 129. Construct UJT based free running oscillator and change its frequency. (7 hrs)	Construction of FET & JFET, difference with BJT. Purpose of Gate, Drain and source terminals and voltage / current relations between them and Impedances between various terminals. Heat Sink- Uses & purpose. Suitability of FET amplifiers in measuring device applications. Working of different power electronic components such as SCR, TRIAC, DIAC and UJT.
34	<ul style="list-style-type: none"> Plan and construct different power electronic circuits and analyse the circuit functioning 	MOSFET & IGBT 130. Identify various Power MOSFET by its number and test by using multimeter. (5 hrs) 131. Identify different heat sinks used with various power MOSFET devices. (5 hrs) 132. Construct MOSFET test circuit with a small load. (5 hrs) 133. Identify IGBTs by their numbers and test by using multimeter. (5 hrs) 134. Construct IGBT test circuit with a small load. (5 hrs)	MOSFET, Power MOSFET and IGBT, their types, characteristics, switching speed, power ratings and protection. Differentiate FET with MOSFET. Differentiate Transistor with IGBT.
35	<ul style="list-style-type: none"> Select the appropriate opto electronics components and verify the characteristics in different circuit. 	Opto Electronics 135. Test LEDs with DC supply and measure voltage drop and current using multimeter. (5 hrs) 136. Construct a circuit to test photo voltaic cell. (5 hrs) 137. Construct a circuit to switch a lamp load using photo diode. (5	Working and application of LED, IR LEDs, Photo diode, photo transistor, their characteristics and applications.

		hrs) 138. Construct a circuit to switch a lamp load using photo transistor. (5 hrs) 139. Identify opto coupler input and output terminals and measure the quantum of isolation between input/output terminals and operate a relay by connecting a switch. (5 hrs)	Optical sensor, opto-couplers, circuits with opto isolators. Characteristics of LASER diodes.
36	<ul style="list-style-type: none"> Assemble, test and troubleshoot various digital circuits. 	Basic Gates 140. Identify different Logic Gates (AND, OR, NAND, NOR, EXOR, EX-NOR, NOT ICs) by the number printed on them. (6 hrs) 141. Verify the truth tables of all Logic Gate ICs by connecting switches and LEDs. (8 hrs) 142. Construct and verify the truth table of all the gates using NAND and NOR gates. (6 hrs) 143. Use digital IC tester to test the various digital ICs (TTL and CMOS). (5 hrs)	Introduction to Digital Electronics. Difference between analog and digital signals. Logic families and their comparison, logic levels of TTL and CMOS. Number systems (Decimal, binary, octal, Hexadecimal). BCD code, ASCII code and code conversions. Various Logic Gates and their truth tables.
37	<ul style="list-style-type: none"> Assemble, test and troubleshoot various digital circuits. 	Combinational Circuits 144. Construct Half Adder circuit using ICs and verify the truth table. (3 hrs) 145. Construct Full adder with two Half adder circuit using ICs and verify the truth table. (5 hrs) 146. Construct the adder cum subtractor circuit and verify the result. (5 hrs) 147. Construct and Test a 2 to 4 Decoder. (3 hrs) 148. Construct and Test a 4 to 2 Encoder. (3 hrs) 149. Construct and Test a 4 to 1 Multiplexer. (3 hrs) 150. Construct and Test a 1 to 4 De Multiplexer. (3 hrs)	Combinational logic circuits such as Half Adder, Full adder, Parallel Binary adders, 2-bit and four bit full adders. Magnitude comparators. Half adder, full adder ICs and their applications for implementing arithmetic operations. Concept of encoder and decoder. Basic Binary Decoder and four bit binary decoders. Need for multiplexing of data. 1:4 line Multiplexer / Demultiplexer.
38	<ul style="list-style-type: none"> Assemble, test and troubleshoot various digital circuits.. 	Flip Flops 151. Identify different Flip-Flop (ICs) by the number printed on them. (5 hrs) 152. Construct and test four bit latch using 7475. (5 hrs) 153. Construct and test R-S flipflop using IC7400 with clock and without clock pulse. (5 hrs) 154. Verify the truth tables of FlipFlop ICs (RS, D, T, JK, MSJK) by connecting switches and LEDs. (10 hrs)	Introduction to Flip-Flop. S-R Latch, Gated S-R Latch, D- Latch. Flip-Flop: Basic RS Flip Flop, edge triggered D Flip Flop, JK Flip Flop, T Flip Flop. Master-Slave flip flops and Timing diagrams. Basic flip flop applications like data storage, data transfer and frequency division.

39-40	<ul style="list-style-type: none"> Simulate and analyze the analog and digital circuits using Electronic simulator software. 	Electronic circuit simulator 155. Prepare simple digital and electronic circuits using the software (10 hrs) 156. Simulate and test the prepared digital and analog circuits (16 hrs) 157. Convert the prepared circuit into a layout diagram. (10 hrs) 158. Prepare simple, power electronic and domestic electronic circuit using simulation software. (14 hrs)	Study the library components available in the circuit simulation software. Various resources of the software.
41-43	<ul style="list-style-type: none"> Assemble, test and troubleshoot various digital circuits. 	Counter & shift Registers 159. Construct and test a four bit asynchronous binary counter using 7493 (4 hrs) 160. Construct and test 7493 as a modulus-12 counter. (4 hrs) 161. Construct and test a four bit Synchronous binary counter using 74163. (5 hrs) 162. Construct and test synchronous Decade counter. (4 hrs) 163. Construct and test an up/down synchronous decade counter using 74190 and monitor the output on LEDs. (5 hrs) 164. Identify and test common anode and common cathode seven segment LED display using multi meter. (3 hrs) 165. Display the two digit count value on seven segment display using decoder/driver ICs. (4 hrs) 166. Construct a shift register using RS/ D/JK flip flop and verify the result. (5 hrs) 167. Construct and test four bit SIPO register. (5 hrs) 168. Construct and test four bit PIPO register. (5 hrs) 169. Construct and test bidirectional shift registers. (5 hrs)	Basics of Counters, types, two bit and three bit Asynchronous binary counters and decade counters with the timing diagrams. 3-bit Synchronous counters and synchronous decade counters. Types of seven segment display. BCD display and BCD to decimal decoder. BCD to 7 segment display circuits. Basics of Register, types and application of Registers.
44-47	<ul style="list-style-type: none"> Construct and test different circuits using ICs 741 operational amplifiers & ICs 555 linear integrated circuits and execute the result. 	Op – Amp & Timer 555 Applications 170. Use analog IC tester to test the various analog ICs. (5 hrs) 171. Construct and test various Op-Amp circuits Inverting, Non-inverting and Summing Amplifiers. (15 hrs) 172. Construct and test Differentiator and Integrator (10 hrs) 173. Construct and test a zero crossing detector. (5 hrs) 174. Construct and test Instrumentation amplifier (10 hrs) 175. Construct and test a Binary weighted and R-2R Ladder type	Block diagram and Working of Op-Amp, importance, Ideal characteristics, advantages and applications. Schematic diagram of 741, symbol. Non-inverting voltage amplifier, inverting voltage amplifier, summing amplifier, Comparator, zero cross detector, differentiator, integrator and instrumentation amplifier, other popular Op-Amps. Block diagram of 555, functional

		Digital-to-Analog Converters (15hrs.) 176. Construct and test Astable timer circuit using IC 555 (10 hrs) 177. Construct and test mono stable timer circuit using IC 555. (10 hrs) 178. Construct and test VCO (V to F Converter) using IC 555. (10 hrs) 179. Construct and test 555 timers as pulse width modulator (10 hrs)	description w.r.t. different configurations of 555 such as monostable, astable and VCO operations for various application.
48-49	Project work / Industrial visit Broad Areas: <ol style="list-style-type: none"> 1. Delayed automatic power on circuit. 2. Neon flasher circuit using IC 741 3. UJT act as a relaxation oscillator 4. Up/down synchronous decade counter 5. Portable continuity cum capacitor tester 		
50-51	Revision		
52	Examination		

Identify different transistors with respect to different package type, B-E-C pins, power, switching transistor, heatsink etc

Objectives : At the end of this exercise you shall be able to

- identify transistor by different package type, pin configuration
- identify power, switching transistor, heat sinks etc from the data manuals/books.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
• Trainees tool kit	- 1 Set	• Different types of transistor packages from T0-1, T0-5, T0-18, T0-39, T0-72, T0-92, T0-3, T0-66, T0-126, T0-202, T0-220, T0-3P, T0-247	- 15 Nos
• Transistor databook	- as reqd		
• Multimeter/DMM with probes	- 1 No	• Different Heat sinks suitable for above transistors	- 10 Nos

Note:

- 1 The Instructor has to select and label the transistors used for this exercise.
- 2 A minimum of one number in each type of package has to be arranged.
- 3 Label the heat sinks also in the similar way

PROCEDURE

TASK 1 : Identification of transistor by different package type, pin configuration, power rating, type of transistor & heat sink

- 1 Pick one of the Labelled transistors from given assorted lot, identify the code number, and record them in Table 1.
- 2 Refer to the Chart 1 semiconductor data book, identify the type of package, all other details as required in Table 1 and record them.
- 3 Refer to the Chart 2, different types of heat sinks used for transistors, compare, verify the details of a transistor in the above Table 1 and select the heat sink suitable for the transistor in hand.
- 4 Record the heat sink type in Table 1 and repeat the above step for remaining labelled transistors.
- 5 Some metallic transistor have notch on its surface. Identify the mark or notch available in transistor. (Terminal adjacent to the notch or mark will be emitter.)

Table 1

Sl.No.	Label No	Transistor code number	Transistor package type	Package diagram with pin description	Current & Voltage		Power rating	Suitable Heatsink type
					Current rating	Voltage rating		

- 6 Get the work checked by the Instructor.

CHART1


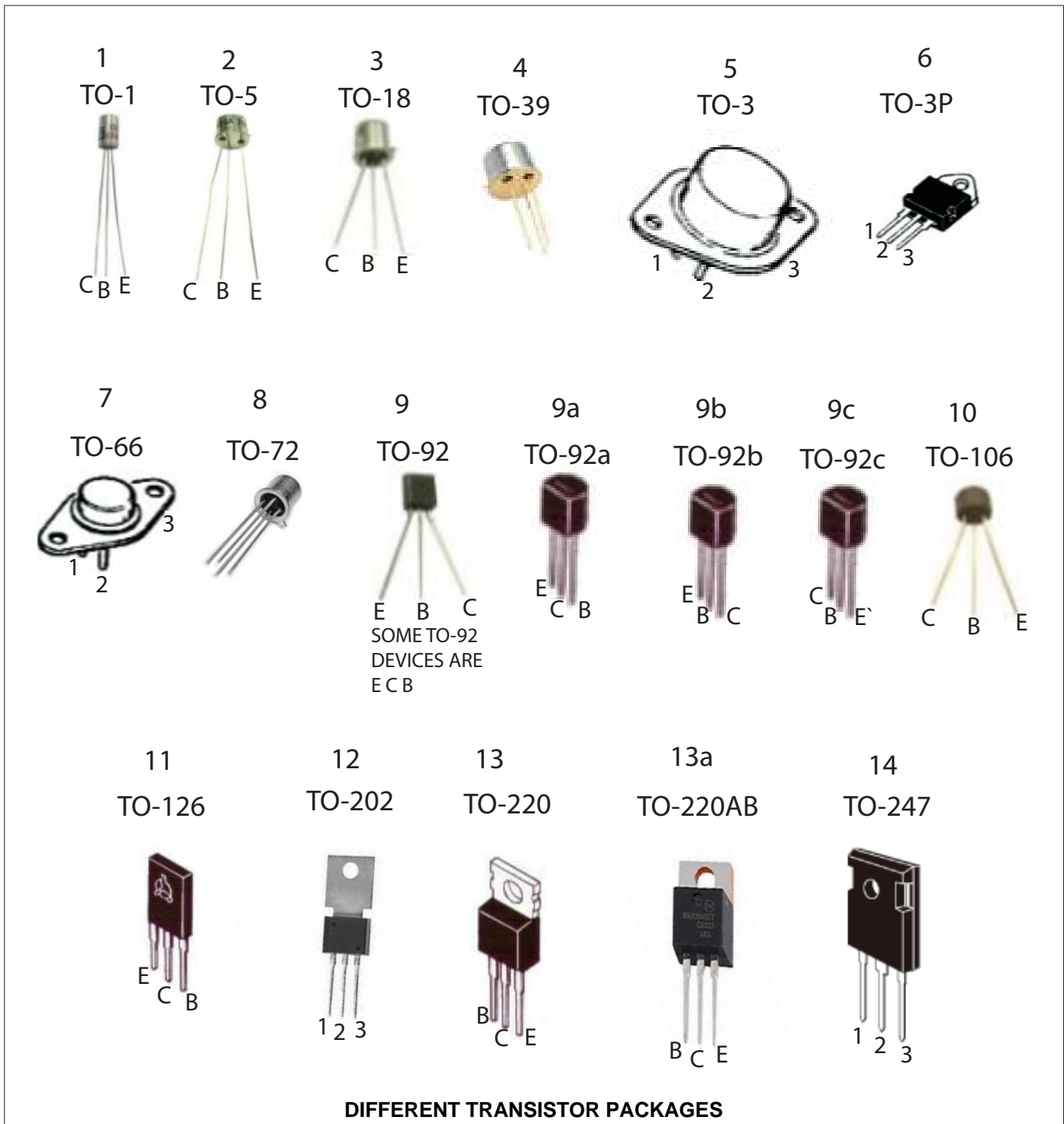
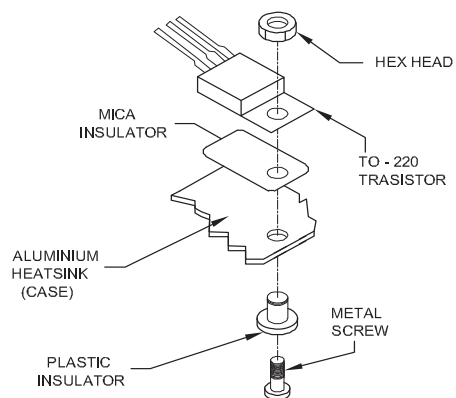
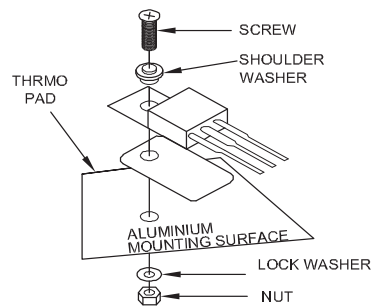
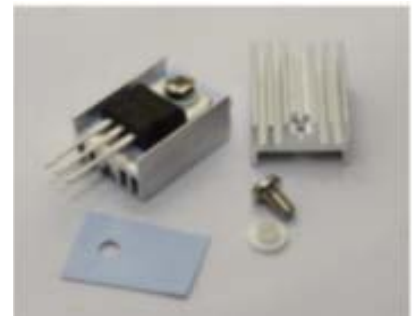
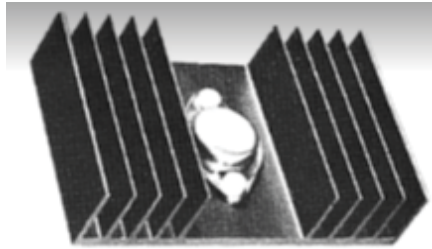


CHART2

Chart showing different types of heatsinks used for transistor packages

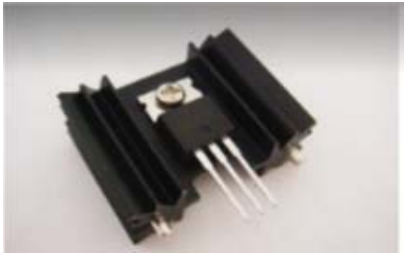

Test the condition of a given transistor using Ohm-meter

Objectives: At the end of this exercise you shall be able to

- test the condition of transistor using ohm meter/multimeter.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Digital multimeter/Analog multimeter with crocodile clip probes - 1 Set

Materials/Components

- Transistor assorted types (T0-3, T0-5, T0-66, T0-18, T0-72, T0-92A, 92B, T0-202, T0-220, T0-247) - 10 Nos
- Transistor data book - as reqd

Note :

- 1 The instructor has to arrange a minimum of one number in each type and label the transistors used for this exercise
- 2 Incase, the Analog type multimeter is not available, skip the Task 1 and proceed with Task 2 of this exercise using Digital multimeter.

PROCEDURE

TASK 1 : Testing transistor using analog multimeter

- 1 Pick one of the labelled transistor from given assorted lot and enter its number in the Table -1.
- 2 Verify the label number, and other details recorded in the Table 1 of Exercise No.2.1.102. Refer the databook, identify the transistor type, pin diagram and record details in Table 1.

In some power transistor, the metal body itself is connected to the collector terminal. All transistors will not have shield pin.

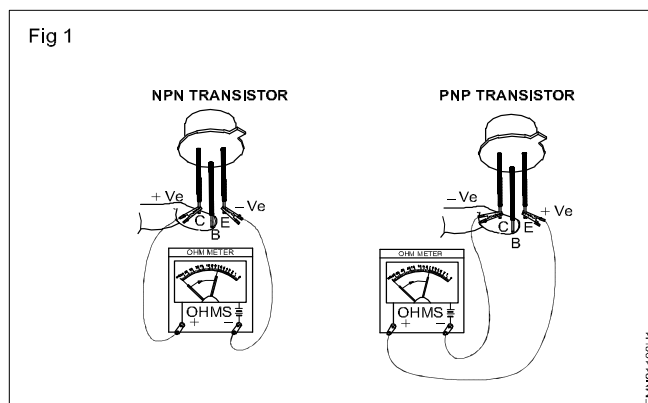


Table 1

Sl.No.	Label No	Code no.of transistor	Package type	Forward/Reverse	Measured resistance between			Remarks
					B-E	B-C	E-C	
1				Forward				
2				Reverse				
3				Forward				
4				Reverse				
5				Forward				
6				Reverse				
7								
8								
9								
10								

- 3 Connect crocodile clip probes to the analog multimeter & select ohms range for testing.

In using analog multimeter, select resistance range RX100 Ohm, low range may damage low power transistors.

- 4 Identify the transistor terminals as Base, Emitter and Collector.

Testing the transistor using the analog type Ohm meter is shown in Fig 1 for guidance.

- 5 Test resistance value between Base & Emitter terminals in forward and reverse direction by connecting probes as shown in Fig 1 and record readings in Table 1.
- 6 Repeat the above step between Base & collector terminals and record readings.
- 7 Repeat the step between Emitter & collector and record readings.
- 8 Repeat steps 4 to 7 for all the remaining labelled transistors.
- 9 Get the work checked by the Instructor.

Task 2: Testing the condition of transistor using Digital multimeter (DMM)

- 1 Pick one of the labelled transistor from the given lot, enter its number in Table 2.
- 2 Verify the details like transistor type, pin configuration etc recorded in the Table 1 of Ex.No.2.1.102/Refer to the data book, identify all the details required.
- 3 Connect the crocodile clip probe to the DMM and set the selector, switch to the Diode testing position/range.
- 4 Connect the positive test probe of the DMM to the Base (B) terminal and the negative probe to the Emitter (E) of the transistor as shown in Fig 2.

For a good NPN transistor, the meter should show between 0.45V to 0.9V and for a PNP transistor, the meter should show "OL" (Over Limit) means infinity.


- 5 Observe the reading displayed on the DMM, record the value in Table 2.
- 6 Keep the positive probe at Base and connect the negative probe to the collector (C) terminal, observe the reading on the DMM, record it in Table 2.

For a good NPN transistor the meter should show between 0.45 to 0.9V and for a PNP type transistor, the meter should show "OL" (Over Limit) means infinity.

- 7 Repeat steps 4,5 and 6 with reversed polarities of DMM and record those readings in Table 2.
- 8 Connect the positive probe to the Emitter terminal and negative probe to the Collector (C) of transistor as shown in Fig 2; Record the observations in Table 2.

- 9 Repeat step 8 with reversed polarities of DMM.
- 10 Carry out steps 4 to 9 for all the remaining labelled transistors and record readings in Table 2.
- 11 Get the work checked by the Instructor.

Fig 2

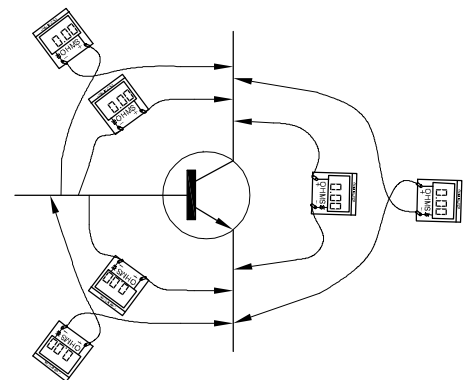

TESTING TRANSISTOR USING DMM

Note:

Compare the resistance values recorded in forward and reverse directions between B-E, B-C and E-C terminals.

Conclude the condition of tested transistor is defective/unserviceable if the resistance value is same on both directions for B-E or B-C junctions, shorted / open junctions show same resistance value in both directions otherwise, the transistor is good/serviceable.

Table 2

Sl.No.	Lable No NPN/PNP	Transistor Code No and type	Meter reading between the terminals				Remarks
			Direction	Base to emitter	Base to collector	Emitter to collector	
1			Forward				
2			Reverse				
3			Forward				
4			Reverse				
5			Forward				
6			Reverse				
7			Forward				
8			Reverse				
9			Forward				
10			Reverse				

Measure and Plot input and output characteristics of a transistor CE amplifier

Objectives: At the end of this exercise you shall be able to

- measure and plot the input characteristics of a transistor in CE configuration
- measure and plot the output characteristics of a transistor in CE configuration.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit
- DC milliammeter, 0-100mA - 1 Set
- DC microammeter, 0-500 μ A - 1 No
- DC millivoltmeter, 0-1000mV - 1 No
- Regulated DC dual power supply 0-30V/2A - 1 No
- Semiconductor data manual - 1 No

Materials/Components

- Tagboard - 1 No
- Transistors, SL 100, - 1 No
- Resistors
 - 120 Ω , $\frac{1}{4}$ W - 1 No
 - 10k Ω , $\frac{1}{4}$ W - 1 No
 - 3.3k Ω , $\frac{1}{4}$ W - 1 No
 - 1 k Ω , POT, linear - 1 No
- Hook up wires and patch cords - as reqd

PROCEDURE


TASK 1 : Measurement and plotting of input characteristics (V_{BE} versus I_B) of given transistor as CE amplifier

- 1 Collect the transistor, identify the number, refer the data book and record the details and condition of the transistor in Table 1.

Table - 1

Label No	Transistor No and type	β or h_{FE} (typical)	Condition from quick tests

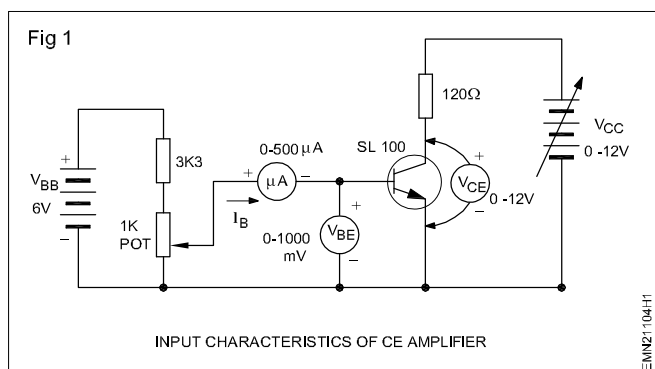- 2 Construct the circuit as shown in Fig 1.



- 3 Switch ON 6V DC supply V_{BB} and adjust 1 K pot such that $V_{BE} = 0V$.
- 4 Adjust the DC supply for V_{CC} to 0 volt such that $V_{CE} = 0$ volt.
- 5 Increase V_{BE} from zero volt, in steps of 100 mV upto 700 mV; At each setting record value of base current I_B in Table 2.

Table - 2

V_{CE} set at 0 volts, constant							
V_{BE} in mV	0	200 mV	300 mV	400 mV	500 mV	600 mV	700 mV
I_B in μ A							

- 6 Set $V_{BE} = 0$ volts by adjusting the pot; Set $V_{CE} = 6$ volts, repeat step 5 and record readings in Table 3.

Table - 3


V_{CE} set at 6 volts constant							
V_{BE} in mV	0	200 mV	300 mV	400 mV	500 mV	600 mV	700 mV
I_B in μ A							

- 7 Set $V_{BE} = 0$ volts; Set $V_{CE} = 12$ volts, repeat step 6 and record the readings in Table 4.

Table - 4


V_{CE} set at 12 volts constant							
V_{BE}	0	200 mV	300 mV	400 mV	500 mV	600 mV	700 mV
I_B in μ A							

- 8 Get the recorded readings checked by the instructor.
- 9 Draw the graph of input characteristics of given transistor in CE configuration by taking the readings recorded in Tables 2,3 and 4 shown in Fig 2. (Mark V_{BE} in X-axis and I_B in Y-axis).
- 10 Get the plotted graph checked by the Instructor.

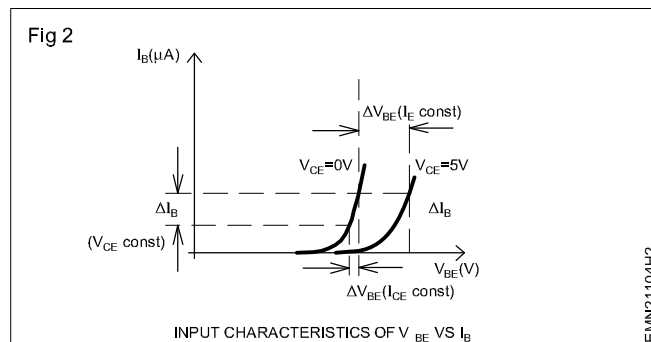

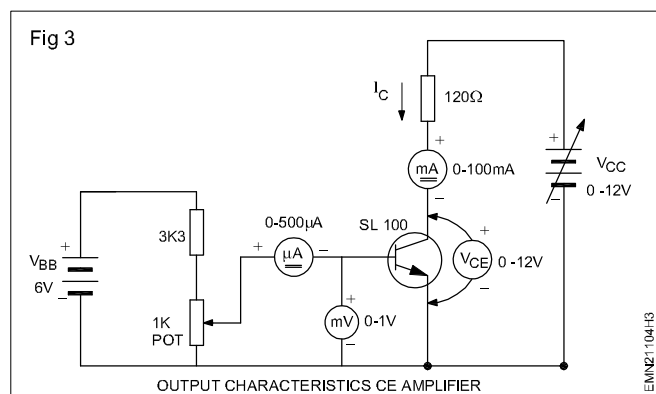TASK 2: Measurement and plotting of output characteristics of given transistor as CE amplifier.

- 1 Modify the circuit connections of Task 1 to make variations in V_{CE} and observe/measure I_C at different values of I_B as shown in Fig 3.



- 2 Set V_{CC} to 0V such that $V_{CE} = 0V$ and adjust the supply V_{BB} such that $I_B = 100 \mu A$.
- 3 Vary V_{CC} such that V_{CE} is increased in steps of 0.2V upto 1V and continue as per the Table 5; observe the output current I_C at each step of V_{CE} and record the readings in Table 5.

- 4 Increase I_B to values 200 μA , 300 μA , 500 μA and at each setting repeat step 3; Record the readings in Table 6, 7 and 8 respectively.
- 5 Get your recorded readings checked by the Instructor.
- 6 Draw the graph of output characteristics of given transistor in CE configuration by taking, plotting the readings recorded in Tables 5,6,7 and 8 as shown in Fig 4.
- 7 Get the plotted graph and get it checked by the instructor.
- 8 Calculate the β_{dc} using the formula with recorded readings, find the dc current gain β of the transistor at V_{CE} of 6V. Record the calculation and result in Table 9.
- 9 Compare the calculated value of β in step 8 and value noted from the data book at step 1.

Output characteristics of transistor

Table - 5

I_B set at 100 μA microAmps constant												
V_{CE}	0.2V	0.4V	0.6V	0.8V	1V	2V	3V	4V	5V	6V	7V	8V
I_C												

Table - 6

I_B set at 200 μA constant												
V_{CE}	0.2V	0.4V	0.6V	0.8V	1V	2V	3V	4V	5V	6V	7V	8V
I_C												

Construct and test a transistor based switching circuit to control a relay (use relays of different coil voltages and transistors of different β)

Objectives : At the end of this exercise you shall be able to

- **construct and test transistor based switching circuit to control a relay**
- **construct and test transistor based relay control circuit using different Beta.**

Requirements			
Tools/Equipments/Instruments			
• Digital multimeter with probes	- 1 Set	• Resistor	
• Trainees tool kit	- 1 Set	• 10 k Ω , 1/4 W/CR25	- 1 No
• Regulated DC Power supply 0-30V/2A	- 1 No	• Solder wire	- 1 No
• Soldering Iron 25W/230V	- 1 No	• Solder flux	- as reqd
Materials/Components		• SPDT switch	- 1 No
• Transistor -BC 147, SL100	- 1 No each	• Connecting wires	- as reqd
• Semiconductor data manual	- as reqd	• Diode -1N4001	- 1 No
• General purpose PCB	- 1 No	• 12V/30mA/10A/1CO	- 1 No each
		• Relay 5V/50 mA/10A 1CO	- 1 No each
		• Bulb (100W/230V A/C) with holder	- 1 No
		• Twisted pair flexible wire	- 2 m

PROCEDURE


TASK 1 : Construction and testing of transistor based switching circuit to control a relay

- 1 Collect all the components required, test them and plan the layout of components on the general purpose PCB.
- 2 Identify the transistor number their leads and record the h_{FE} of given transistor and other parameters with reference to the data sheet in Table 1.

Table 1

Code No. of transistor	Type	I_C	V_{CEO}	V_{CBO}	V_{EBO}	h_{FE}

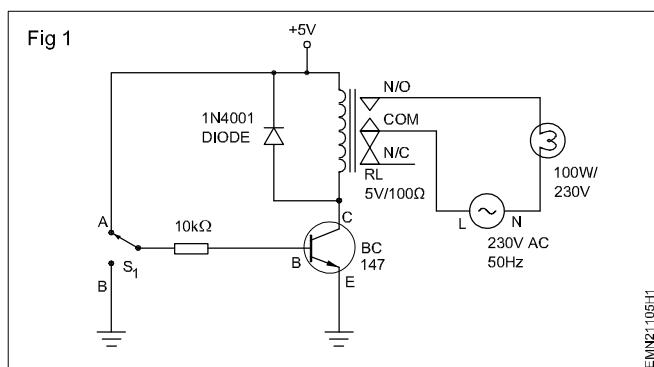- 3 Assemble the circuit as shown in Fig 1.



- 4 Get the circuit checked by the Instructor.
- 5 Keep the switch S_1 in position B.

- 6 Switch ON the 5V, DC supply and AC mains to the circuit.

Take care of 230V AC manins supply link.

- 7 Measure voltage at Base and collector terminals with respect to Emitter terminal; Record the readings in Table 2.
- 8 Change the switch to point A, observe the condition of relay and record the observations in Table 2.

Table 2

Sl. No.	Switch position	Voltage a		Relay condition	Status of bulb
		Base (V_{BE})	Collector (V_{CE})		
1	A				
2	B				

- 9 Switch OFF the DC and AC manis supply.
- 10 Get the work checked by the Instructor.


TASK 2 : Construction and testing of switching circuit to control a relay of higher coil voltage with transistor of different h_{FE} .

- 1 Modify the circuit of Task 1 with 12 V relay and transistor SL 100 for switching circuit.
- 2 Identify the transistor leads, find Beta (h_{FE}) and other parameters in the data sheet, record them in Table 3.

Table 3

Code No.of transistor	Type	I_C	V_{CEO}	V_{CBO}	V_{EBO}	h_{FE}

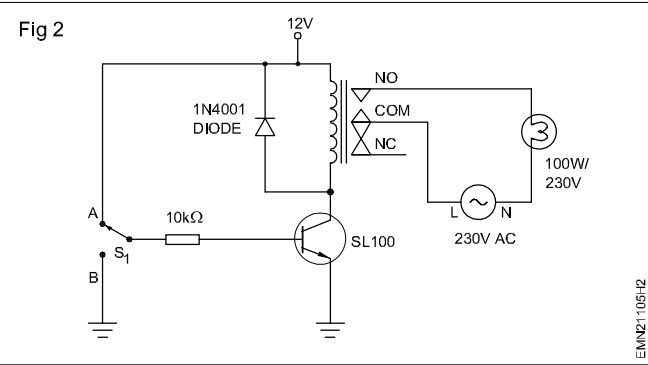- 3 Assemble the circuit as shown in Fig 2 and get it checked by the Instructor.



- 4 Keep the switch S_1 in position 'B', switch ON the 12 VDC supply and AC mains supply to the circuit.

Safety: Take care of 230 VAC mains supply lines

- 5 Measure voltage at Base, collector terminals with respect to Emitter terminals and record the readings in Task 4.
- 6 Change the switch S_1 to point 'A', measure voltages status of relay, lamp and record the observations in Task 4.

Table 4

Sl. No.	Switch position	Voltage a		Relay condition	Status of bulb
		Base (V_{BE})	Collector (V_{CE})		
1		A			
2		B			

- 7 Switch OFF the DC and AC supply to the circuit.
- 8 Get the work checked by the Instructor.

Construct and test fixed bias, emitter bias, and voltage divider bias transistor amplifier

Objectives : At the end of this exercise you shall be able to


- construct and test fixed bias arrangement to transistor amplifier circuit
- construct and test emitter bias arrangement to transistor amplifier circuit
- construct and test voltage divider bias arrangement to transistor amplifier circuit.

Requirements			
Tools/Equipments/Instruments			
• Trainees tool kit	- 1 Set	• Capacitor	
• Digital multimeter with probes	- 1 No	1 μ F/25V	- 1 No
• CRO, 20 MHz, Dual Trace	- 1 No	10kpf	- 2 Nos
• Regulated DC Power Supply, 0-30V/2A	- 1 No	25 μ F/25V	- 2 Nos
• AF signal generator	- 1 No	• Resistor 1/4 W/CR25	
• DC micro ammeter 0-500 μ A	- 1 No	220k Ω	- 1 No
• DC miliammeter 0-30 mA	- 1 No	5.1k Ω	- 1 No
		1.5k Ω	- 2 Nos
		5.6k Ω	- 1 No
		12k Ω	- 1 No
		120 Ω	-1 No
Materials/Components		470 Ω	- 1 No
• Breadboard	- 1 No	1k Ω	- 3 Nos
• Transistor BC 107, SL100	- 1 No each	• Hook up wires	- as reqd

PROCEDURE

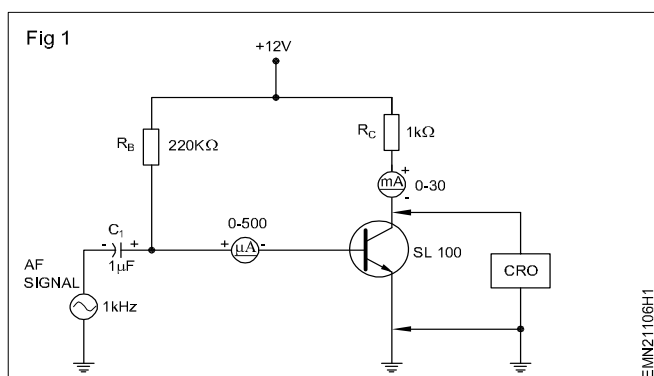TASK 1 : Construction and testing of fixed bias arrangement for transistor amplifier circuit using BJT

- 1 Collect all the components required and check them for good working condition using multimeter.
- 2 Assemble the circuit as shown in Fig 1.
- 7 Compare the calculated values with the observed values.
- 8 Get the values checked by the Instructor.



- 3 Calculate base current ' I_B ' using the formula.

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

- 4 Now switch - ON the DC supply to the circuit and record readings in Table 1 without signal.
- 5 Prepare CRO for measurement and apply AF signal kHz/20mV sine wave from AF signal generator as input.
- 6 Observe and record the values of I_B , I_C and V_{CE} for the fixed bias amplifier circuit in Table-1.

Note:

- 1 We assume that the Amplifier operation is in the active region, and hence $V_{BE} = 0.7$ V.
- 2 β is the amplification factor of the transistor by which the base current gets amplified.
- 3 β dc refers to current gain, when DC bias voltage is applied.
- 4 Output collector current ' I_C ' = β dc x I_B .
- 5 When transistor is in active region, I_C gradually increases towards higher values. At the same time, V_{CE} decreases from peak towards lower values.
- 6 When saturation is attained by amplifier, I_C goes to peak but V_{CE} drops to less than 0.7V.
- 7 For calculating I_C and V_{CE} , following formulae should be used.


$$V_{CE} = V_{CC} - I_C \cdot R_C \text{ Say } \beta = 100 \text{ \& } I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

Table 1

Input condition	Base Current I_B	Collector current I_C	V_{CE}	Voltage across load V_{RL}	Current gain $A_i = I_C / I_B$	$A_v = \frac{V_C}{V_{in}}$
Without signal						
With input Signal						

TASK 2 : Construction and testing of emitter feedback bias amplifier circuit using BJT

1 Modify the circuit as shown in Fig 2.

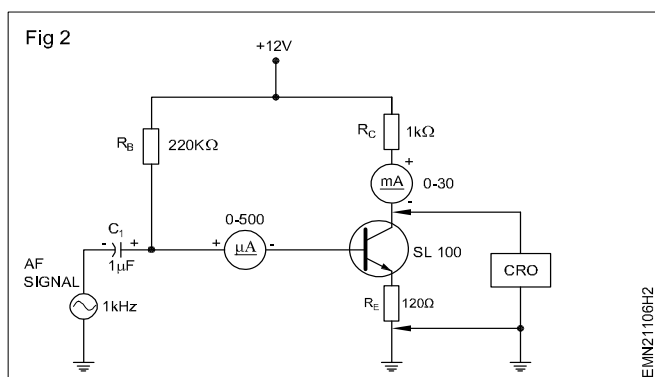

- Calculate the values of I_B , I_C , β_{dc} and V_{CE} by using the formulae given in the note and record the values in Table 2.
- Switch ON the 12V DC supply and AF signal generator input to the circuit assembled and measure base current I_B , collector current I_C , V_{BE} (forward bias of transistor) and the voltage drops across base resistor R_B , the emitter resistor R_E , collector resistor R_C and V_{CE} record the observed values in Table 3.

Table 2

Calculated Observed values	Collector Current I_C	Base current I_B	V_{CE}	Current gain $A_i (\beta_{dc})$	Volatage gain A_v
Calculated values					
Observed values					

- Prepeare CRO for measurements, connect and observe the peak-to-peak AC signal input from AF signal generators at CH1 and amplified AC signal output of the emitter feedback bias amplifier circuit at CH-2 and record the readings.
- Increase the input A/C signal voltage applied to emitter feedback amplifier gradually and repeat the observations of the parameters given in step 3.
- Note that the collector current ' I_C ' remains stable to maintain constant 'Q' - operating point of the amplifier.
- Get the values checked by the Instructor.
- Calculate and record the I_C (sat) of the emitter-bias circuit
- Get the values checked by the Instructor

Note:

- Emitter bias is also refered to as emitter feedback back bias (i.e) a portion of the output is given back to the input as feedback.
- In this circuit, the voltage across resistor ' R_E ' is used to offset changes is β_{dc} .
- This type of biasing compensates for the variation in β_{dc} and keeps the 'Q' point fairly stable.
- If β_{dc} increases, the collector current increases, which in turn increases the voltage at the emitter.
- This increased emitter voltage (plus the V_{BE} drop of transistor) decreases the voltage across the base-resistor.

- 6 There fore base current reduces, and hence collector current reduces. This prevents I_C from action varying continuously.

$$I_B = \frac{V_{CC} - (V_{BE} + V_E)}{R_B}$$

- 7 It partially offsets the original increase in I_C due to increased β_{dc} . Due to feedback only the output ' I_C ' could change the input I_B this maintain stable Q point.

- 8 In emitter-bias, the current ' I_C ' will be

$$I_C - \beta_{IB} \text{ (i.e) } I_C = \beta$$

$$\frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} \text{ \& } I_B = \frac{V_{CC} - V_{BE} - I_E R_E}{R_B}$$

Assuming $I_E \approx I_C$; $V_{CE} = (R_C + R_E) I_C$

Table 3

AF Signal Generator - AC input = Sinewave 1kHz/20mV

Value/ signal condition	Base Current I_B	Collector current I_C	Current gain $\beta = \frac{I_C}{I_B}$	V_{BE}	V_{CE}	DRB	Drop across R_E	Drop across R_C
Calculated Value								
Measured Values								
Without Signal								
With signal								

TASK 3 : Construction and testing of voltage divider biased transistor CE amplifier

- 1 Check all the components and assemble the circuit as shown in Fig 3.
- 2 Get the assembled circuit checked by the Instructor.
- 3 Measure and record I_B and I_C in Table 4, calculate current gain β_{dc} and record it.

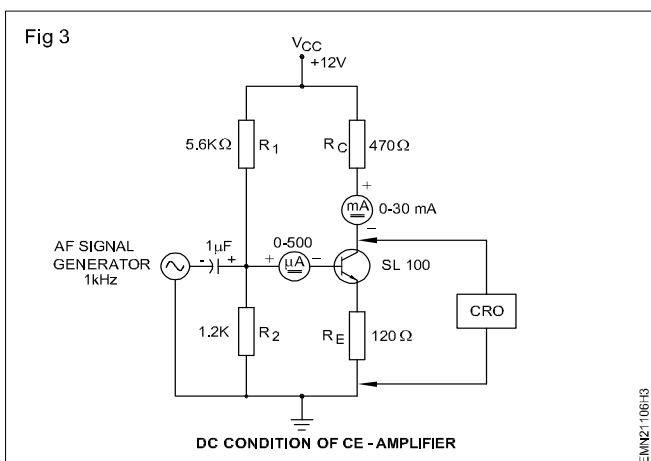


Table 4

Collector current I_C	Base current I_B	Current gain A_i β_{dc}

- 4 Apply AC input signal of 1 kHz, 20 mV from AF signal generator to the voltage divider biased CE amplifier.
- 5 Prepare the CRO for measurements connect CRO to observe/measure AC signal input to amplifier from AF signal generator to CH-1 and amplified AC signal output of voltage divider bias to CH-2.
- 6 Measure and record the observed values as required in Table 5. Calculate & record A_i and A_v of the amplifier observe and record the Input/Output waveforms available on the CRO.

Note:

- In this circuit note that the base of the transistor is biased by voltage divider network made up of R_1 & R_2 .
- Q point of this circuit lies half way along the transistor's load line.
- $V_{CE} = V_{CC} - I_C (R_C + R_E)$ and $I_C = \beta I_B$
- $R_B \ll (\beta + 1) R_E$ and $R_B = R_1 // R_2$.

Table 5

Signal Condition	Base current I_B	Collector current I_C	β_{dc}	Voltage drop Across				V_{BE}	V_{CE}	Voltage gain $A_v = \frac{V_{Load}}{V_{in}}$
				R_1	R_2	R_C	R_E			
Without signal										
With signal										

- 7 Get the work checked by the Instructor.

Construct and test a CE amplifier with and without emitter bypass capacitors

Objectives: At the end of this exercise you shall be able to

- construction and find the effect of emitter bypass capacitor on amplifier gain and input impedance
- plot the frequency response of CE amplifier with by pass capacitor.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- CRO, 20 MHz Dual trace - 1 No
- AF Signal generator - 1 No
- Regulated DC power supply, 30V/2A - 1 No
- Digital multimeter with probes - 1 No


Materials/Components

- Hook-up wires - as reqd
- Breadboard - as reqd
- Resistor/ $\frac{1}{4}$ W/CR25
1k Ω , 1.2 k Ω , 5.6 k Ω
120 Ω , 470 Ω - 1 No each
- Capacitors
25 μ F/25V - 2 Nos
4.7 μ F/25V - 1 No
100 μ F/25V - 1 No
470 μ F/25V - 1 No

PROCEDURE

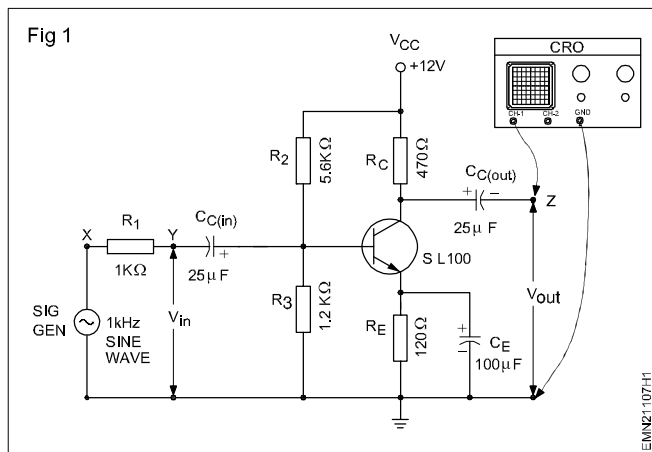TASK 1 : Construction and testing of the effect of bypass capacitor in CE amplifier

- 1 Collect all the components, test them assemble the circuit as shown in Fig 1 on breadboard. Capacitor C_E is the emitter by pass capacitor.





- 5 Find the input impedance Z_{in} and output impedance Z_{out} of the amplifier using the same procedure as followed for Task 2 of Ex. 2.1.106; Record values in Table 1.
- 6 Measure and record the AC and DC voltages at various points of the amplifier in Fig 2 and Fig 3.
- 7 Switch off DC supply to the circuit. Disconnect 100 μ F capacitor connected across the 120 Ω emitter resistor.

Now the input V_{in} may show higher value due to increased Z_{in} without the bypass capacitor. Do not alter the output level / frequency of the signal generator.

- 2 Get the circuit connections checked by the Instructor.
- 3 Preprepare the CRO for measurements and switch 'ON' 12V DC supply to the circuit, adjust the output of the signal generator at 1kHz such that V_{out} is large enough and undistorted.
- 4 Record the peak to peak values of input V_{in} and output V_{out} in Table 1; Calculate and record the voltage gain A_v of the amplifier.
- 8 Switch 'ON' DC supply to the circuit, repeat steps 4 and record readings in Table 1.
- 9 Measure and record the AC and DC levels at various points of the amplifier without the bypass capacitor in Fig 3.
- 10 Switch-OFF DC supply to the circuit and from the recorded readings, complete the sentences given in record sheet.
- 11 Get the work checked by the Instructor.

Table - 1

Condition	$V_{in(\text{peak-to-peak})}$	$V_{out(\text{peak-to-peak})}$	A_v	Z_{in}	Z_{out}
With bypass capacitor C_E connected across R_E					
Without bypass capacitor C_E					

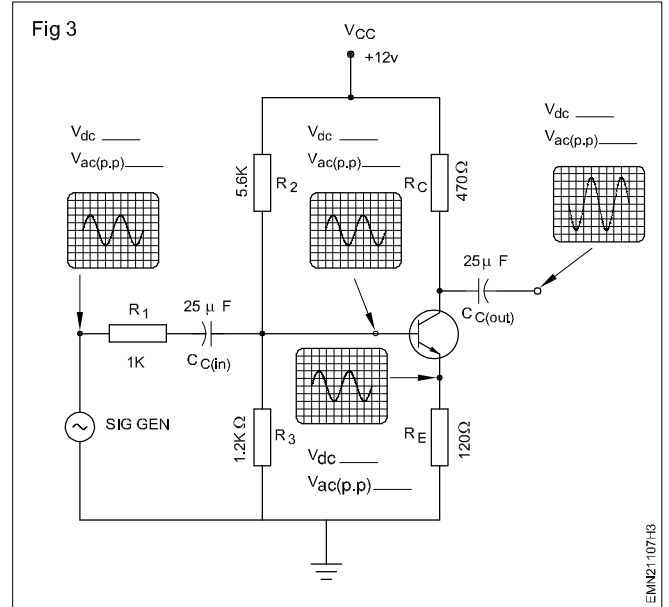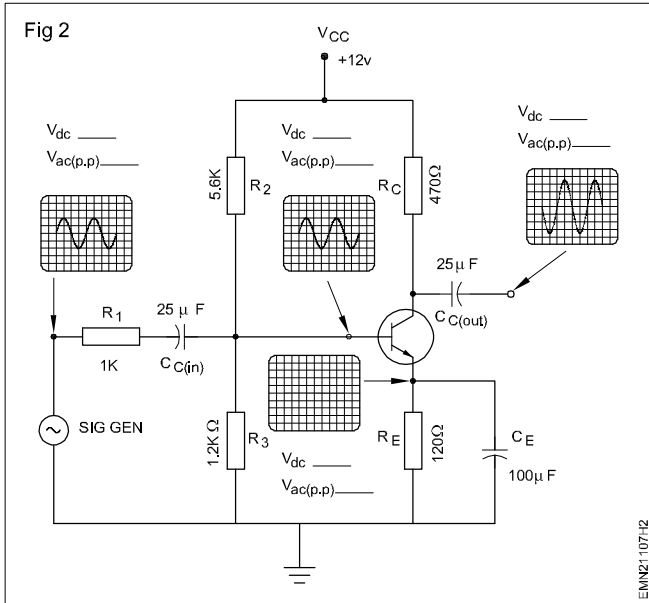


12 Complete the sentences given below with the readings recorded in Table 1.

When the emitter bypass capacitor was removed

- the voltage gain of the amplifier decreased by _____ %.
- the input impedance of the amplifier _____ by _____ %.

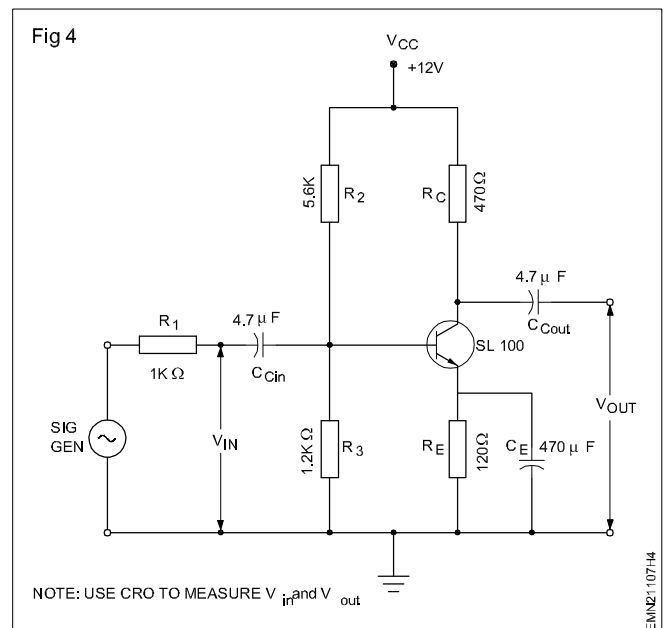TASK 2 : Plotting the frequency response of CE amplifier

- Modify the circuit to confirm to the schematic diagram as given in Fig 4.
- Set the output of the signal generator to sine wave, 1 KHz. Adjust the input voltage to the transistor $V_{in} = 200\text{mV}$.
- Record the set input level V_{in} and corresponding value of output V_{out} of the amplifier in the appropriate row of the Table 2.
- Vary the output frequency of the signal generator above and below the set frequency of 1 kHz in steps as given in Table 2. At each step record the output of amplifier, V_{out} .
- Calculate and record the voltage gain A_v of the amplifier at different frequencies.
- Change the value of $C_{C(in)}$ to $4.7\mu\text{F}$ and repeat steps 2 to 5.



- 7 Plot the graph of frequency (f_{in}) versus voltage gain A_v for the readings taken with the capacitor values of 0.047 and 4.7 μF in Table 2. Find and mark the low frequency cut off/half power point on the graph.

The cut off/half power point is 0.707 A_v at the mid-band gain.

- 8 Switch OFF DC supply to the circuit; change the value of the input coupling capacitor $C_{C(in)}$ to 100 μF .

$C_{C(in)}$ is made 100 μF to eliminate the effect of the coupling capacitor while finding the effect of C_E on the frequency response.

- 9 Change value of the bypass capacitor C_E to 0.47 μF and repeat steps 2 to 5, record readings in Table 3.
- 10 Change the value of the bypass capacitor C_E back to 470 μF and repeat steps 2 to 5.
- 11 Find the dominant lower cut off frequency of the amplifier with $C_{C(in)} = 4.7 \mu F$ and $C_E = 470 \mu F$.

The effect of $C_{C(out)}$ on the amplifier frequency response is not given in the procedure as the effect of $C_{C(out)}$ is almost same as that of $C_{C(in)}$.

Table - 2

Frequency response for different C_{cin}

Set value of $V_{in} = \underline{\hspace{2cm}}$ at $f_{in} = 1 \text{ kHz}$ $C_E = 470 \mu F$ $C_{Cout} = 4.7 \mu F$				
frequency f_{in} H_z	$C_{Cin} = 0.047 \mu F$		$C_{Cin} = 4.7 \mu F$	
	V_{out}	A_v	V_{out}	A_v
10				
20				
30				
100				
200				
400				
800				
1000				
1200				
1400				
1600				
2000				
3000				

Table - 3


Frequency response for different C_E

Set value of $V_{in} = \underline{\hspace{2cm}}$ at $f_{in} = 1 \text{ kHz}$ $C_{Cin} = 100 \mu F$ $C_{Cout} = 4.7 \mu F$				
frequency f_{in} H_z	$C_E = 0.47 \mu F$		$C_E = 470 \mu F$	
	V_{out}	A_v	V_{out}	A_v
10				
20				
30				
100				
200				
400				
800				
1000				
1200				
1400				
1600				
2000				
3000				

- 12 Get the work checked by the Instructor.


Graph 1

Frequency response with $C_{cin} = 0.047$ capacitor

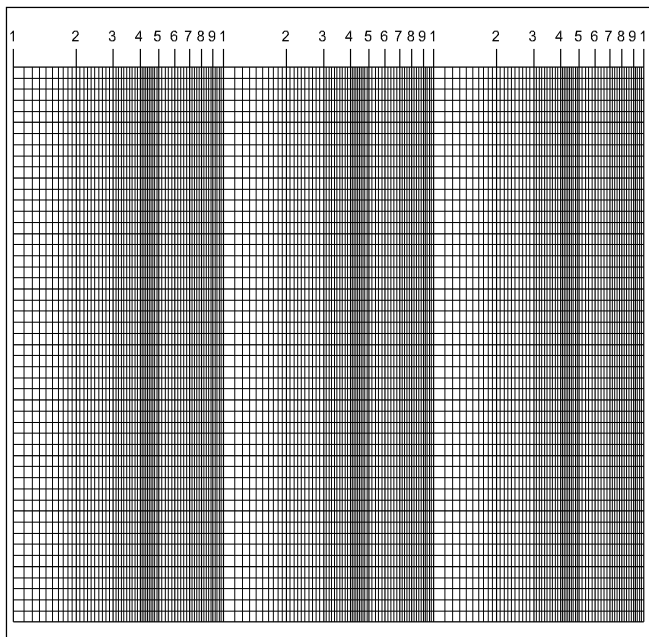

Graph 2

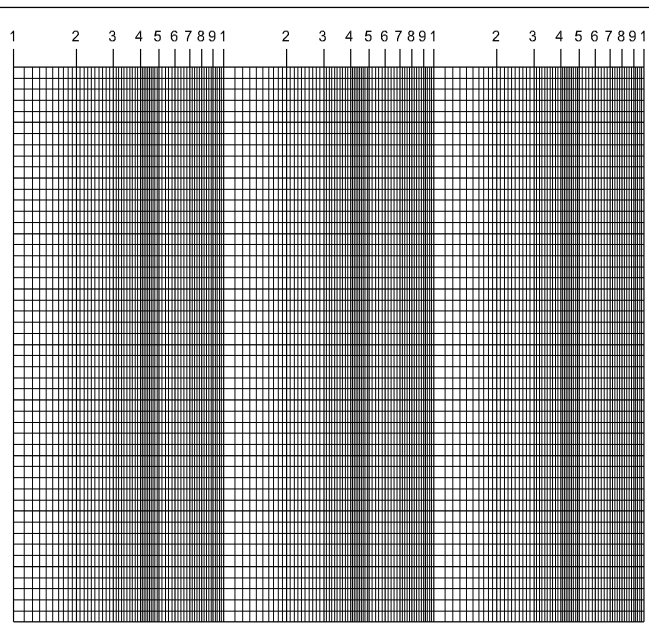Frequency response with $C_{cin} = 4.7\mu F$



Construct and test a Common Base amplifier

Objectives: At the end of this exercise you shall be able to

- construct a common base amplifier and measure,
 - current gain, of the amplifier
 - voltage gain of the amplifier
 - input-impedance of the amplifier
 - output-impedance of the amplifier
 - power gain of the amplifier
- compare the phase relationship between Input and Output of common base amplifier.

Requirements

Tools/Equipments/Components

- Trainees tool kit - 1 Set
- DC milliammeter, 0-10mA - 1 No
- Regulated DC power supply 0-30V/2A - 1 No
- CRO, 20 MHz Dual trace - 1 No
- AF signal generator - 1 No
- Multimeter /DMM with probes - 1 No


Materials/Components

- Breadboard - 1 No
- Transistor, SL 100 - 1 No
- Resistors/¼ W/CR25
 - 1kΩ - 1 No
 - 1.2kΩ - 1 No
 - 2.2kΩ - 1 No
 - 3.3kΩ - 1 No
 - 6.8kΩ - 1 No
 - 10kΩ - 1 No
- Capacitors
 - 25 µF/25V - 2 Nos
 - 100 µF/25V - 1 No

PROCEDURE

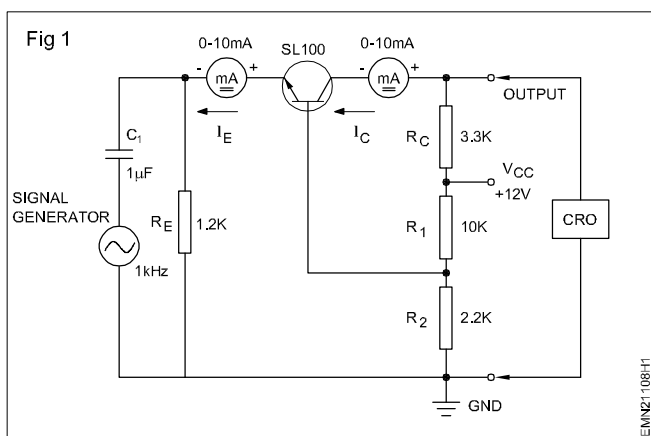TASK 1: Construction and measurement of A_i , A_v , Z_{in} and Z_{out} in CB amplifier

- 1 Collect all the required components, test and assemble the common base amplifier as shown in Fig 1.



- 2 Get the assembled circuit checked by the Instructor.
- 3 Switch ON 12V DC supply to the circuit, measure and record the dc voltage levels of V_{RE} , V_{BE} , V_{CB} and V_{CE} .

From the readings, conclude whether the transistor is working or not.


Record the values of input current I_E and output current I_C . Calculate and record the current gain A_i of the common base amplifier in Table 1 using the formula

$$A_i = \frac{I_C}{I_E}$$

- 4 Calculate and record values of, input impedance Z_{in} , output impedance Z_{out} , voltage gain A_v in Table 2.

Use the value of A_i found in step 3. Find the value of r'_e using the formula, $r'_e = 25\text{mV}/I_E$.

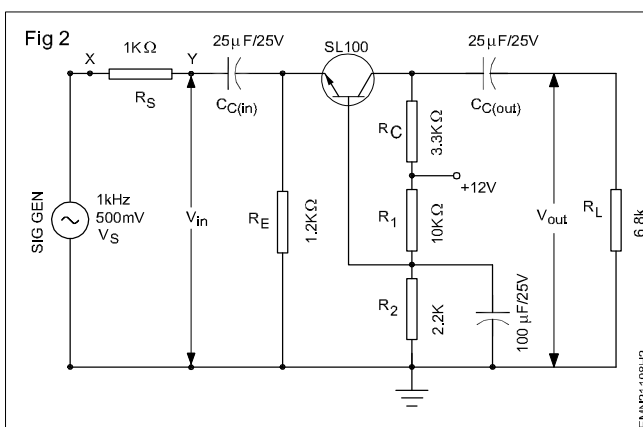- 5 Modify the circuit as shown in Fig 2 and prepare the CRO for measurements.



- 6 Set the output of the Signal generator to Sine wave, 1kHz at 500mV. Measure and record V_{in} and V_{out} of the amplifier. Calculate and record the voltage gain A_v of the amplifier in Table 3; draw the input and output waveforms in the graph sheets.
- 7 Measure and record the input impedance Z_{in} and output impedance Z_{out} of the common base amplifier in the same way as found in common emitter amplifiers Ex.No. 2.1.107.
- 8 Calculate and record the power gain of the common base amplifier using the above readings.
- 9 Compare the calculated readings at step 4 and the actual values measured.
- 10 Get the work checked by the Instructor.

Table 1
Current gain A_i of CB amplifier

V_{BG}	V_{BE}	V_{CB}	V_{CE}	Condition of transistor	I_E	I_C	Current gain A_i (or) a

Table 2
Calculated values using given circuit component values

r'_e	Z_{in}	Z_{out}	A_v	A_p



Table 3

Frequency set to 1 kHz , sine wave

V_{in}	V_{out}	Voltage gain A_v	Input impedance Z_{in}	Output Impedance Z_{out}	Power gain A_p

Graph of Input/output phase relationship

Note: *Make rough sketches of wave-forms using pencil.*

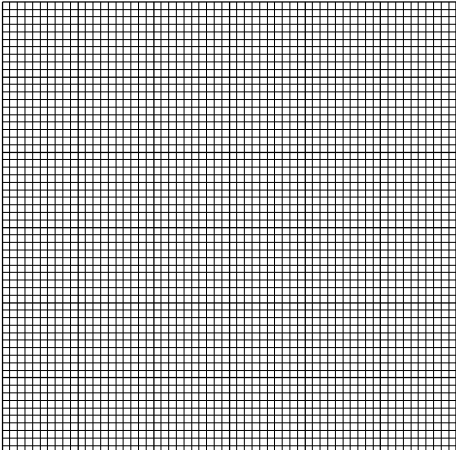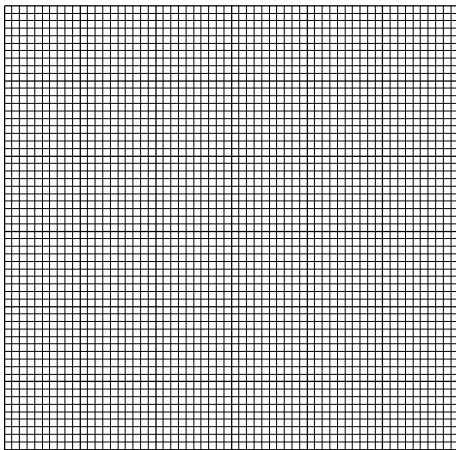Amplifiers input waveform	Amplifiers output waveform	Remarks on input-output phase relationship
		

TASK 2: Comparison of phase relationship between input and output

- 1 Adjust the signal generator output for maximum undistorted V_{out} .
- 2 Prepare the CRO for measurement and connect Ch-1 of CRO at input point (across signal generator) and Ch-2 at the output point (across R_L).
- 3 Switch 'ON' 12V DC supply to the circuit, observe and sketch the waveform in graph sheet as in Table 4.
- 4 Record the remarks on the phase relationship between input and output waveforms. (Inphase/out of phase)
- 5 Get the work checked by the Instructor.

Construct and test a Common Collector/Emitter Follower amplifier

Objectives: At the end of this exercise you shall be able to


- construct a common collector/Emitter Follower amplifier and measure current gain, voltage gain of Emitter Follower amplifier
- Compare input - output phase relationship of Emitter Follower amplifier
- measure input impedance Z_{in} , output impedance Z_{out} and power gain of Emitter Follower amplifier.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
• Trainees tool kit	- 1 Set	• Breadboard	
• DC microammeter 0-500 μA	- 1 No	• Transistor, SL100 or equivalent	- 1 No
• DC milliammeter 0-1 mA	- 1 No	• Resistors ¼ W/CR25	
• Regulated DC power supply 0-30V/2A	- 1 No	120Ω	- 1 No
• A.F Signal generator	- 1 No	100kΩ	- 1 No
• CRO, 20MHz-Dual trace	- 1 No	1kΩ	- 1 No
• Multimeter / DMM with probes	- 1 No	• Preset, 470Ω	- 1 No
		• Capacitors, 0.47 μF/25V	- 2 Nos

PROCEDURE

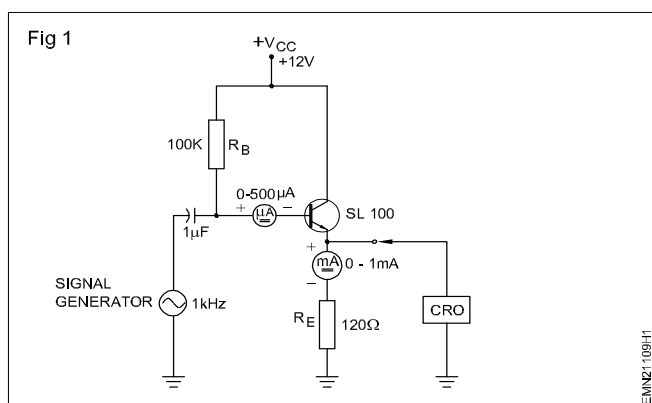TASK 1: Construction and measurement of current gain and voltage gain of emitter follower

- 1 Collect all the components, test and assemble the emitter follower circuit as shown in Fig 1, on breadboard.



- 2 Get the assembled circuit checked by the Instructor.
- 3 Measure and record the values of I_B and I_E in Table 1. Assuming $I_C \approx I_E$, calculate and record the β of the transistor using the formula in Table 1.


$$\beta \approx \frac{I_E}{I_B} \approx \frac{I_C}{I_B}$$

- 4 Calculate and record the theoretical values of voltage gain A_v , input impedance Z_{in} , output impedance Z_{out} and current gain A_i of the amplifier in Table 2.

[To calculate the value of r'_e use the formula,

$$r'_e = \frac{25\text{mV}}{I_E}]$$

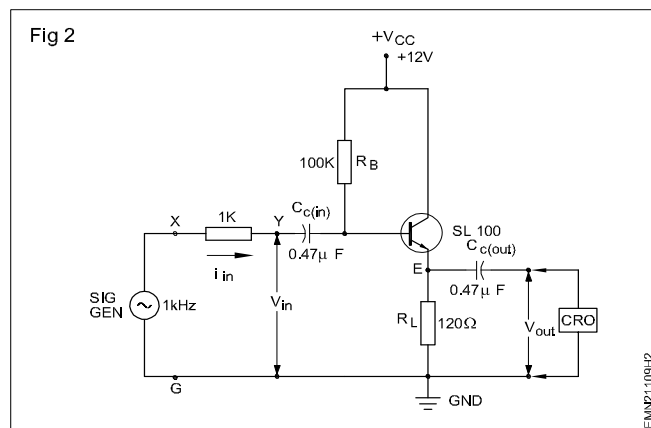- 5 Modify the assembled circuit as shown in Fig 2. Get the correctness of the assembled circuit checked by the Instructor.



- 6 Connect the signal generator to the input of the emitter follower amplifier. Set the signal generator output to sine wave, 1 kHz.
- 7 Adjust the signal generator output level such that the AC input $V_{in(p-p)} = 500$ mV. Measure and record the corresponding output $V_{out(p-p)}$ of amplifier in record sheet Table 3.
- 8 From the measured values of V_{in} and V_{out} , calculate and record the voltage gain A_v of the circuit.
- 9 Compare the values of calculated voltage gain A_v of the amplifier in step 4 and that found in step 8. Record the difference in Table 3.

Table - 1

I_B	I_E	Current gain $A_i = I_E/I_B \approx \beta$

Table - 2

Values calculated using circuit component values

A_v	Z_{in}	Z_{out}	A_i	r'_e

TASK 2: Measure input and output impedance of emitter follower

- Set the output of the signal generator to sine wave, 1 kHz, 500 mV_(p-p) in Fig. 2 and record V_{in} and V_{out} levels in Table 4.
- Measure voltages V_{XG} and V_{YG} on either side of the 1K Ω resistor. Record readings in the record sheet at Table 4.
- From the recorded values of V_{XG} and V_{YG} , calculate the input signal current I_{in} to the amplifier using Ohms law as given below,

$$I_{in} = \frac{V_{XG} - V_{YG}}{1k\Omega}$$

- From the values V_{in} and I_{in} , calculate and record the input impedance Z_{in} using the formula

$$Z_{in} = \frac{V_{in}}{I_{in}}$$

- Connect a 470 Ω preset across the output of the amplifier as shown in Fig 3. Keep the preset in the maximum resistance position before switching ON DC supply to the circuit.

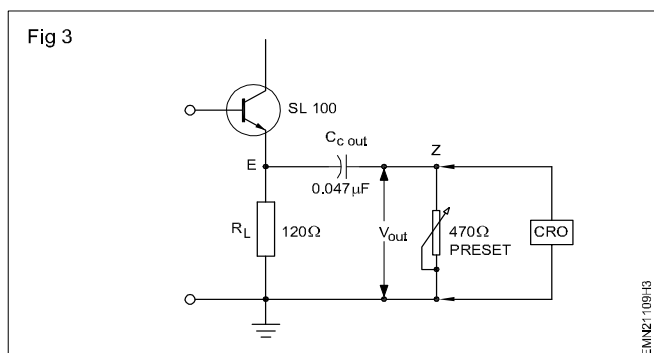


Table 3

(a) Measured value of A_v

Frequency set to 1 KHz

$V_{in(p-p)}$	$V_{out(p-p)}$	A_v
500 mv		

10 Get the work checked by the Instructor.

- (b) Difference between calculated (at step-4) and measured value of A_v (at step-8):-

Precaution: Since there is no limiting resistor in the collector, if the preset is set at zero or low resistance heavy current may damage the transistor.

- Adjust the preset until V_{out} is half the value measured at Step 1 and record the input & output waveforms in graph sheet

Do not adjust the output level of signal generator set at step 1 of this task.

- Switch OFF DC supply to the circuit. Take out the preset from the circuit without disturbing its adjusted position.
- Measure the adjusted resistance value of the preset and record it as the amplifier's output impedance Z_{out} in Table 4.
- From the values recorded, calculate and record, current gain A_i , and power gain A_p of the amplifier, using the formulae

$$A_i = A_v \frac{Z_{in}}{R_E}$$

$$P_{in} = \frac{V_{in}^2}{Z_{in}}$$

$$P_{out} = \frac{V_{out}^2}{R_{out}}$$

$$\text{Power gain of amplifier } A_p = \frac{P_{out}}{P_{in}}$$

$$\text{Power gain } A_p \text{ in decibel} = 10 \log \frac{P_{out}}{P_{in}}$$

Table - 4

Frequency set to 1kHz

$V_{in(p-p)}$	$V_{out(p-p)}$	V_{XG}	V_{YG}	I_{in}	Input impedance Z_{in} of amplifier	Output impedance Z_{out} of amplifier
500 mV						

2 Current gain A_i using the formula $A_i = A_v(Z_{in}/R_E)$: _____

3 Power gain A_e of emitter follower/CC amplifier : _____

4 Power gain A_p of emitter follower/CC amplifier in dB : _____

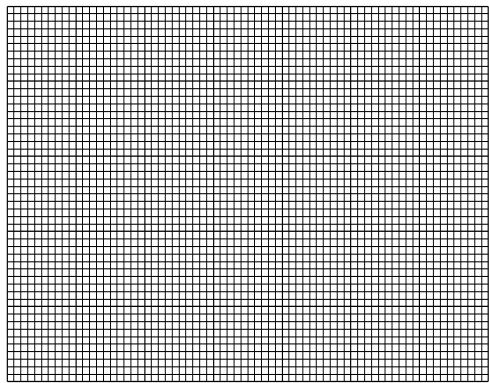
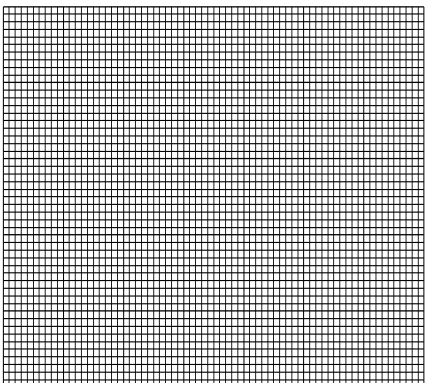
10 Get the work checked by the Instructor.

TASK 3: Comparison of phase relationship between
the input and output of emitter follower amplifier.

- 1 Find the phase relationship between the input and output of the emitter follower in the same way as done for common emitter amplifier in Exercise 2.1.107 or Ex. No. 2.1.108

Graph of Input and output phase relationship.

- 2 Get the work done by the Instructor.

Amplifiers input wave-form	Amplifiers output wave-form	Remarks on input-output phase relationship
		

Construct and test a Darlington amplifier

Objectives: At the end of this exercise you shall be able to

- construct Darlington amplifier and measure current gain and voltage gain
- Compare the input - output phase relationship
- measure input and output impedance and calculate power gain of darlington amplifier
- compare the phase relationship.

Requirements

Tools/Equipments/Instruments


- Trainees tool kit - 1 Set
- DC microammeter 0-100 μ A - 1 No
- DC milliammeter 0-1mA - 1 No
- Regulated DC power supply, 0-30V/2A - 1 No
- AF Signal generator - 1 No./batch
- CRO, 20 MHz- Dual trace - 1 No./batch
- Multimeter/DMM with probes - 1 No

Materials/Components

- Breadboard - 1 No
- Transistor, SL100 or equivalent - 2 Nos
- Resistors/1/4 W/CR25
 - 120 Ω - 1 No
 - 150k Ω , 10k Ω , 1k Ω - 2 Nos
- POT, 470 Ω , 1/2W - 1 No
- Capacitors, 0.47 μ F/25V - 2 Nos
- 1 μ F/25V - 1 No

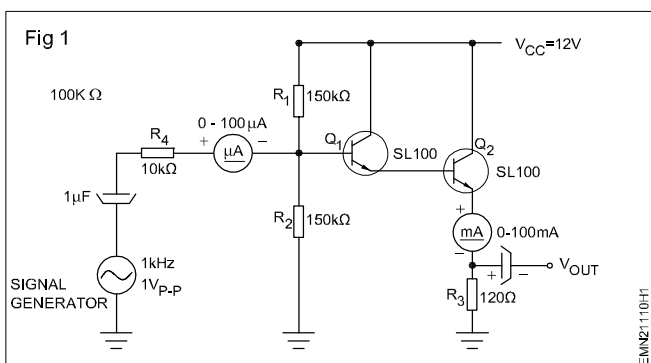TASK 1(a): Measurement of current gain and voltage gain

- 1 Collect all the components, test them and assemble the Darlington amplifier circuit as shown in Fig 1.




- 2 Get the assembled circuit checked by the Instructor.

- 3 Measure and record the values of I_B at base and I_E at Emitter of transistor-Q1 and I_E , at emitter of transistor-Q2 in Table 1. Assuming $I_C \approx I_E$, calculate and record the current gain of the transistor using the formula,

$$\text{current gain} = \frac{\beta_{dc} I_{E2}}{I_{B1}}$$

- 4 Using the value of I_E and current gain from step 3, calculate and record the theoretical values of voltage gain A_v , input impedance Z_{in} , output impedance Z_{out} and current gain A_i of the amplifier in Table 2.

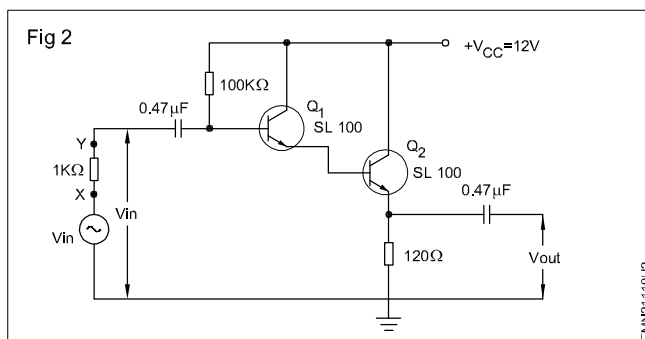- 5 Modify the assembled circuit as shown in Fig 2. Get the correctness of the wired circuit checked by the instructor.



- 6 Connect the signal generator to the input of transistor Q1 and set the signal generator output to sine wave, 1kHz.
- 7 Adjust the signal generator output level such that the AC input $V_{in(p-p)} = 500 \text{ mV}$. Measure and record the corresponding output $V_{out(p-p)}$ of amplifier in Table 3.
- 8 From the measured values of V_{in} and V_{out} , calculate and record the voltage gain A_v of the circuit in Table 3.
- 9 Compare the values of calculated voltage gain A_v of the amplifier in step 3 and that found in step 8. Record the difference in the space provided.

1 Table - 1

$Q_1 I_{B1}$	$Q_1 I_{E1}$	$Q_2 I_{E2}$	Current gain $A_1 = I_{E2}/I_{B1} \approx \beta$

a) Observation to obtain A_v the darlington amplifier practically

Frequency set to 1 KHz

$V_{in(p-p)}$	$V_{out(p-p)}$	A_v
500 mv		

- (b) Difference between calculated (at step-3) and measured value of A_v (at step-7):
-

TASK 1(b) : Measurement of input and output impedance and calculation of power gain for darlington amplifier

- Set the output of the signal generator to sine wave, 1 kHz, 500 mV $V_{in(p-p)}$ in Fig. 2 and record V_{in} and V_{out} levels in Table 4.
- Measure voltages V_{XG} and V_{YG} on either side of the 1K resistor. Record readings in Table 4.
- From the recorded values of V_{XG} and V_{YG} , calculate the input signal current I_{in} to the amplifier using Ohms law as given below,

$$I_{in} = \frac{V_{XG} - V_{YG}}{1k\Omega}$$

- From the values V_{in} and I_{in} , calculate and record the input impedance Z_{in} using the formula

$$Z_{in} = \frac{V_{in}}{I_{in}}$$

- Connect a 470Ω preset across the output of the amplifier as shown in Fig 3. Keep the preset in the maximum resistance position before switching ON DC supply to the circuit.

Since there is no limiting resistor in the collector, if the preset is set at zero or low resistance heavy current may damage the transistor.

- Adjust the preset until V_{out} is half the value measured at Step 1.

Do not adjust the output level of sig. gen. set at step 1 of this task.

- Switch OFF DC supply to the circuit. Take out the preset from the circuit without disturbing its adjusted value.


Table - 2

Values calculated using circuit component values

A_v	Z_{in}	Z_{out}	A_1	r'_e

- Get the work checked by the Instructor.

Fig 3

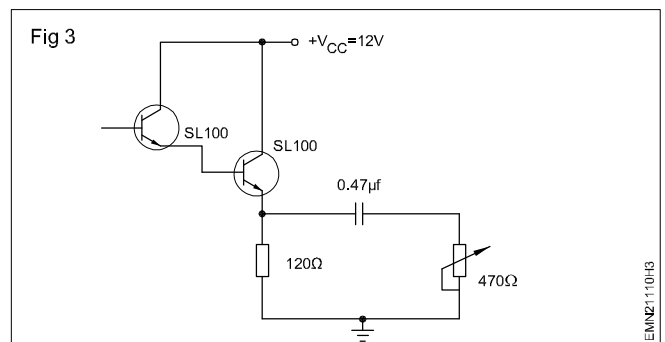

- Measure the adjusted value of the preset and record it as the amplifier's output impedance Z_{out} in Table 4.
- From the values recorded calculate and record, current gain A_1 , and power gain A_p of the amplifier, using the formulae

$$A_1 = A_v \frac{Z_{in}}{R_E}$$

$$P_{in} = \frac{V_{in}^2}{Z_{in}}$$

$$P_{out} = \frac{V_{out}^2}{R_{out}}$$

$$\text{Power gain of amplifier } A_p = \frac{P_{out}}{P_{in}}$$

$$\text{Power gain } A_p \text{ in decibel} = 10 \log \frac{P_{out}}{P_{in}}$$

Table - 4



Frequency set to 1 kHz

$V_{in(p-p)}$	$V_{out(p-p)}$	V_{XG}	V_{YG}	I_{in}	Input impedance Z_{in} of amplifier	Output impedance Z_{out} of amplifier
500 mV						

10 Get the work checked by the Instructor.

TASK 2 : Compare the phase relationship between input and output of darlington amplifier

- 1 Draw the sketch of input & output waveform on graph sheet.
- 2 Find the phase relationship between the input and output of the emitter follower in the same way as done for common emitter amplifier in Exercise 2.1.106.
- 3 Write remark on input and output phase relationship.

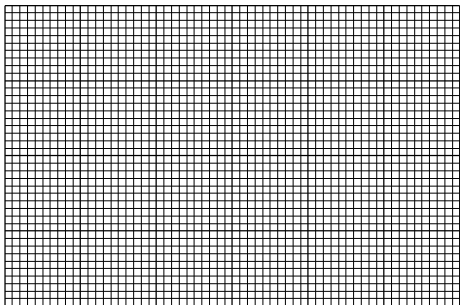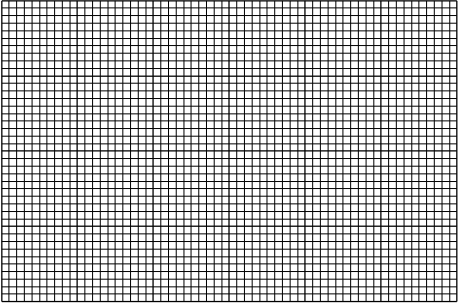Amplifiers input wave-form	Amplifiers output wave-form	Remarks on input-output phase relationship
		

4 Get the work checked by the Instructor.

Construct and a two stage test RC-coupled Amplifier

Objectives: At the end of this exercise you shall be able to

- construct and test two stage amplifier using RC coupling
- observe the frequency response of RC coupled amplifier.

Requirements

Tools/Equipments/Instruments

- | | |
|--------------------------------------|-----------|
| • Trainees tool kit | - 1 Set |
| • CRO, 20 MHz Dual trace | - 1 No |
| • AF Signal generator | - 1 No |
| • Regulated DC power supply 0-30V/2A | - 1 No |
| • Semiconductor data manual | - as reqd |


Materials/Components

- | | |
|---------------------|-------------|
| • Breadboard | - 1 No |
| • Transistor SL 100 | - 2 Nos |
| • Resistor ¼ W/CR25 | |
| 5.6 kΩ | - 2 Nos |
| 1kΩ | - 2 Nos |
| 3.3 kΩ, 22 kΩ | - 1 No each |
| 15 kΩ, 2.5 kΩ | - 1 No each |
| • Capacitor | |
| 1 μF/25V | - 3 Nos |
| 100 μF/25V | - 2 Nos |
| • Hook up wire | - as reqd |
| • Patch cords | - as reqd |

PROCEDURE

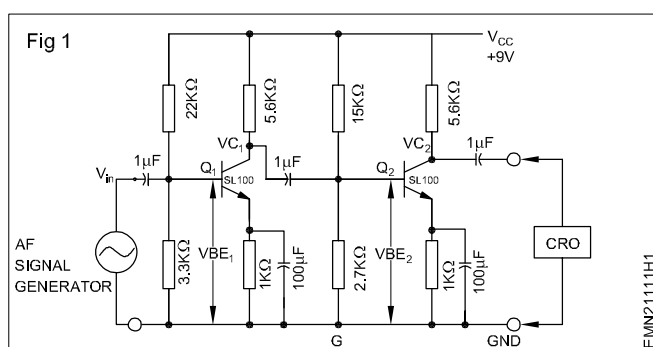TASK 1: Construction and testing of 2 stage RC coupled amplifier

- 1 Collect all the components, identify the base, emitter and collector pins of given transistors and test for their good working condition.
- 2 Assemble the RC coupled amplifier on breadboard as shown in Fig 1.



- 3 Get the assembled circuit checked by the Instructor.

- 4 Switch ON 9 VDC supply to the assembled circuit, measure the DC levels at different test points V_{BE1} , V_{CE1} , V_{BE2} , V_{CE2} (of both transistors) shown in Fig 1; record the measured voltages in Table 1.
- 5 Connect the A.F. signal generator at the input of the assembled amplifier; set the output of the signal generator at 20 mV, 1 kHz, sinewave.
- 6 Preapre the CRO for measurements, measure and record the output of each stage in Table 2.
- 7 From the recorded readings find and record the gain of each stage and the overall voltage gain of the cascaded amplifier.
- 8 Vary the output frequency of the signal generator between 20 Hz to 20 kHz in steps as given in Table 3 and record overall gain of the amplifier at different frequency settings in Table 3.
- 9 Plot the graph of frequency versus voltage gain and mark the low frequency cut-off (f_{LC}) and high frequency cut-off (f_{HC}) points on the graph.

Table 1
V_{in} = 9V DC

Transistor Q ₁ (DC levels)		Transistor Q ₂ (DC levels)		Transistor Condition
V _{BE1}	V _{CE1}	V _{BE2}	V _{CE2}	ON/OFF

Table 2
V_{in} = 20 mV, F = 1kHz, sinewave

Amplifier-1 stage output Voltage	Amplifier-2 stage output Voltage	Amplifier output waveform on CRO
V _{C1} - Gnd	V _{C2} - Gnd	

Table 3

V_{in} = 20mV Observation of frequency response of RC coupled amplifier

Sl No.	Input frequency	V _o	Voltage Gain = $\frac{V_o}{V_{in}} = A_v$
1	10Hz		
2	50Hz		
3	100Hz		
4	200kHz		
5	500kHz		
6	1kHz		
7	2kHz		
8	5kHz		
9	10kHz		
10	15kHz		
11	20MHz		

10 Get the working of the circuit and the recorded readings checked by the Instructor.

Construct and test class-B complementary push-pull amplifier

Objectives: At the end of this exercise you shall be able to

- **construct and test a Class B complementary-symmetry push-pull amplifier circuit**
- **test the amplifier with AF signal input and loudspeaker output.**

Requirements			
Tools/Equipments/Instruments			
• Trainees tool kit	- 1 Set	• General purpose PCB	- 1 No
• CRO, 20 MHz - Dual trace	- 1 No	• Capacitors 25VDC wkg	
• AF signal generator	- 1 No	1000 μ F	- 1 No
• Regulated DC power supply 0-30V/2A	- 1 No	22 KpF	- 1 No
• Multimeter /DMM with probes	- 1 No	1 μ F	- 1 No
• Ammeter 0-500 mA MC panel type	- 1 No	• Resistors ¼ W/CR25	
• Soldering iron 25W/230V	- 1 No	100 k Ω	- 1 No
		1k Ω	- 1 No
		120 Ω	- 1 No
Materials/Components		• Potentiometer 10k Ω , LOG	- 1 No
• Transistors 100N or 100P		8.2 k Ω	- 1 No
orequivalent	- 1 No each	• Loudspeaker - 8 Ω /5W	- 1 No
• BC 148B	- 1 No	• Rosin cored solder	- as reqd
• Transistor data sheet	- as reqd	• Hook up wire/connecting wires	- as reqd

PROCEDURE

TASK 1 : Construction and testing of a class-B complementary symmetry push-pull audio amplifier

- 1 Collect all the components, identify the base emitter and collector leads of given transistors and test them.
- 2 Plan the layout of components and assemble the complementary push pull amplifier as shown in Fig 1 on the general purpose PCB.
- 3 Connect a 0-500mA DC current meter in series with the 9 V regulated DC supply to the assembled circuit as shown in Fig 1. Switch ON DC supply to the circuit.

If current meter shows more than 50mA, switch-off DC supply and consult your instructor.

- 4 Measure the current drawn and the dc voltage levels at different test points of the circuit in Table 2.
- 5 From the recorded readings, calculate the DC current drawn by each stage. Get it checked by Instructor.
- 6 Feed a 100 mV, 1 kHz sine wave from AF signal generator to the input of the amplifier.

If the output of speaker is feeble, increase the input signal level suitably by adjusting the volume control.

- 7 Prepare the CRO for measurements and verify the input and output at each transistor to confirm amplification.
- 8 Measure and record the ac voltage levels (peak-to-peak) at the output of each stage using CRO in Table 3.
- 9 From the recorded readings calculate the overall voltage gain, efficiency of the amplifier and output power.
- 10 Vary the output frequency of the signal generator between 20 Hz and 20kHz and record the 3dB low frequency cut off(f_{LC}) and high frequency cut-off(f_{HC}) on a graph sheet.
Check the audibility of loud speaker.
- 11 Get the working of the amplifier and the recorded readings checked by the Instructor.

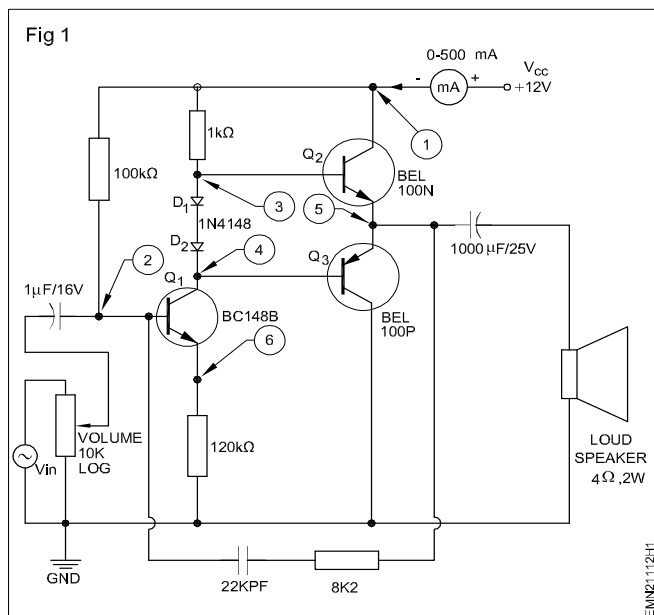


Table 1 Transistor specifications

Transistor type number	NPN or PNP	Package type	Leads diagram	β_{dc} Typ	V_{dc} Max	I_c Max	P_D	Application
BC 100P								
BC 100N								
BC 148B								

Table 2

Current drawn by the circuit		DC voltage levels at test points					
Without signal	With max signal	Supply V_{cc}	V_{B1}	V_{B2}	V_{B3}	V_{E1}	V_{E2}

Table 3 Total circuit current drawn by the cascaded amplifiers with input ac signal: _____

AC voltage levels (p-p) at,					Overall voltage gain $A_V = \frac{V_{out}}{V_{in}}$
Input	Collector of Q_1	Emitter of Q_2	Emitter of Q_3	Speaker	

Efficiency calculation :-

Input current (I_1) = _____

DC power (P_o) = $V_{cc} \times I_1$ = _____

Voltage across speaker (V_o) = _____

Resistance of speaker (R_L) = _____

Output power (P_o) = $\frac{V_o^2}{R_L}$

Efficiency = $\frac{P_o}{P_{DC}} \times 100$

Construct and test Class C Tuned Amplifier

Objectives: At the end of this exercise you shall be able to

- construct and test a Tuned Amplifier and plot the frequency response.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
• Function generator (1Hz to 1 MHz)	- 1 No	• Transistor BF 494	- 1 No
• CRO 0-20 MHz Dual channel	- 1 No	• Resistors ¼ W/CR25 10kΩ,12kΩ,1kΩ	- 1 No each
• Trainees tool kit	- 1 Set	• Inductor, 1mH	- 1 No
• Multimeter / DMM with probes	- 1 No	• Capacitor 0.1µF/25V	- 4s Nos
• Regulated DC power supply 0-30V/2A	- 1 No	• Capacitor 1 nF	- 1 No
		• Breadboard	- 1 No
		• Hookup wires	- as reqd

PROCEDURE

- 1 Collect the required components , check them and assemble the components on breadboard as shown in Figure 1.
- 2 Measure V_B, V_C, V_E of the transistor and record in Table 1.
- 3 Connect the FG at the input terminals and CRO in the output terminals.
- 4 Prepare CRO for measurements, connect one channel to FG/AF generator and other channel to O/P of amplifier as shown in Fig 1.
- 5 Apply 1 kHz -20 mV, sinewave to the input of the circuit and measure the output voltage (P-P) and record in Table 2.
- 6 Vary the frequency in steps and keep the input voltage constant and record the readings in Table 2.
- 7 Repeat the above steps till the output amplitude increases and falls below the 70.7% of the maximum value.
- 8 Plot the graph by taking frequency in X axis & gain in Y axis as shown in Fig 2.
- 9 Mark the 3 dB lower and higher cut-off frequencies on the graph.


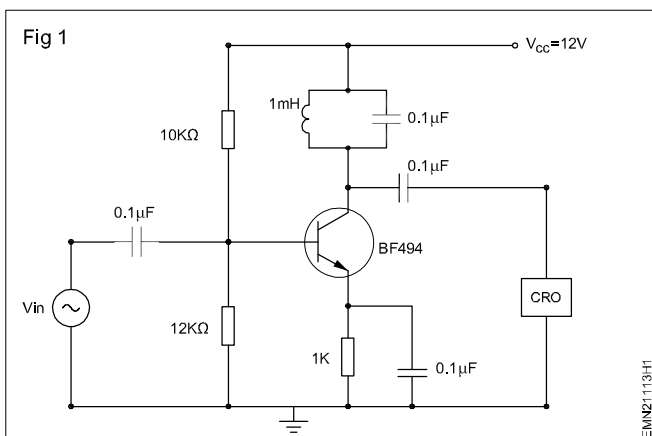


Table 1
DC voltage levels

V_B	V_C	V_E

Table 2

Sl.No	Freq in kHz	V _{out}	V _{in}	Gain = $\frac{V_{out}}{V_{in}}$

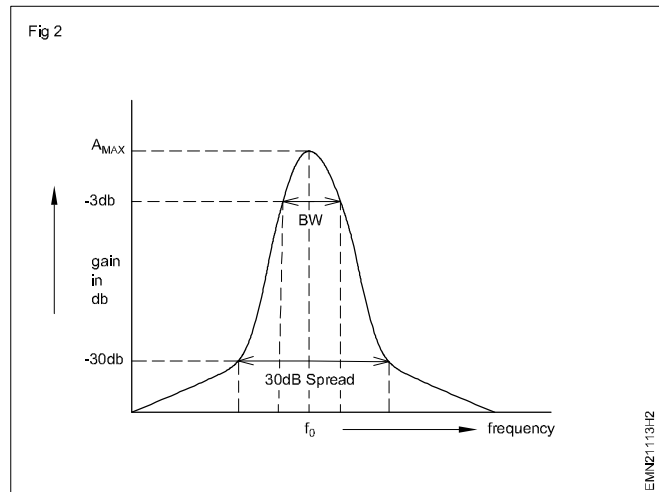

10 Get the work checked by the Instructor.

3dB Lower cut-off frequency = ----- kHz

3dB Higher cut-off frequency = ----- kHz

Demonstrate Colpitt's oscillator, Hartley oscillator circuits and compare the output frequency of the oscillator by CRO

Objectives : At the end of this exercise you shall be able to

- construct and test a Colpitts oscillator
- construct and test a Hartley oscillator
- compare the measured output frequency with calculated frequency.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- CRO 20 MHz -Dual trace - 1 No
- Regulated DC power supply 0-30V/2A - 1 No
- Digital multimeter with probes - 1 No
- Soldering iron 25W/230V - 1 No
- Soldering iron stand - 1 No

Materials/Components

- Transistor BF 195 - 1 No
- MW oscillator coil - 1 No
- Breadboard - 1 No
- Resistor $\frac{1}{4}$ W/CR25
18k Ω , 390 Ω , 82k Ω , 3K9 - 2 Nos each
- Capacitor
0.1 μ F - 1 No
0.01 μ F - 2 Nos
- 2J gang capacitor - 1 No
- Hook up wires - as reqd
- Rosin cored solder - as reqd

PROCEDURE

TASK 1 : Construction and testing of a Colpitts oscillator

- 1 Collect all the required components for assembling/collect trainer kit & test the component for working condition.
- 2 Plan the layout and assemble the circuit on the breadboard as shown in Fig 1.
- 3 Get the assembled circuit checked by the Instructor.
- 4 Prepare the CRO for measuring the output of oscillator.
- 5 Switch ON the 12VDC supply to the circuit connect the CRO at the output terminal of the oscillator circuit and measure the waveform.
- 6 Adjust the gang capacitor to get the desired frequency on CRO.

Note: If the trainer kit on oscillator is not available, the instructor can use assembled oscillator for demonstration.

Note: The operating range of Colpitts oscillator using medium wave oscillator coil is from 1000 kHz to 2055 kHz Frequency of Colpitts oscillator can be determined therotically by using Formula:

$$F = \frac{1}{2\pi\sqrt{LC}}$$

Where 'C' is the capacitance of 2J gang and L is the inductance of the oscillator coil in the tank circuit.

- 7 Repeat the above step, by changing the position of the gang capacitor and record the readings in Table 1.
- 8 Draw waveform observed at 3 positions of gang capacitor and note down the frequencies.
- 9 Compare the calculated value with observed value of frequencies.

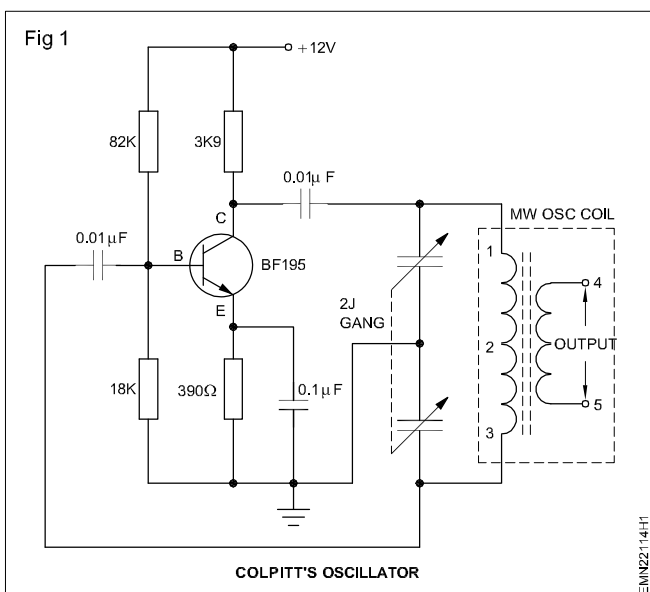



Table 1
Colpitts oscillator Observation

Position of gang capacitor	Amplitude in volts	Conventional circuit	
		Calculated	Observed
Gang capacitor at one extreme end			
Gang capacitor at other extreme end			
Gang capacitor at approximately mid-position			

10 Get the work checked by the Instructor.

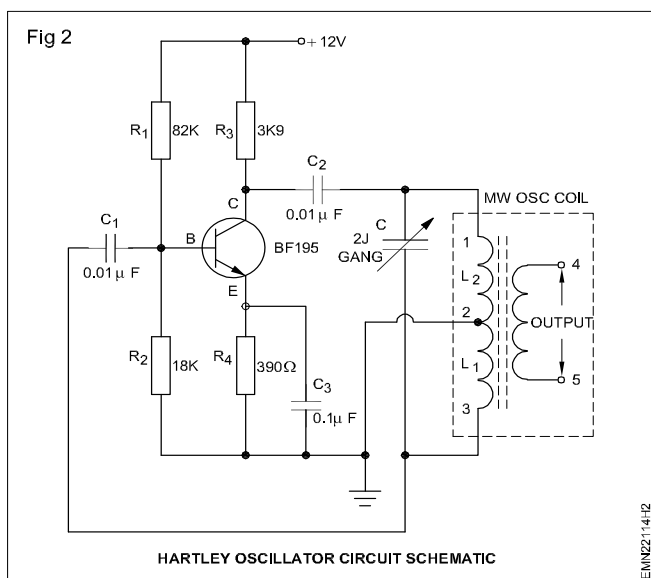TASK 2 : Construction and testing of a Hartley oscillator

- 1 Use trainer kit (or) assemble the components as shown in Fig 2 on breadboard.
- 2 Connect the DC supply and set for 12V



- 3 Switch on the supply
- 4 Switch on the CRO and adjust to get horizontal trace.
- 5 Connect the CRO in the O/P terminal of the circuit.
- 6 Observe the output of the circuit in the CRO, adjust the time/div, V/div knobs to get stable wave form.
- 7 Measure the time period & calculate the frequency of

oscillator using the formula $F = \frac{1}{T}$ practically.

Note: Frequency of Hartley oscillator can be determined theoretically by using formula

$$F = \frac{1}{2\pi\sqrt{LC}}$$

Where 'C' is the capacitance of the capacitor C1 in tank circuit and L = L1 + L2 the effective series inductances of tank circuit.

- 8 Repeat the above steps by changing the position of the gang capacitor and record the readings in Table 2.
- 9 Draw waveform observed at different settings of gauged capacitor and note down the frequencies as given in Table 2.

Table 2

Position of gang capacitor	Conventional circuit	
	Amplitude in volts	Frequency in Hz
Gang capacitor at one extreme end		
Gang capacitor at other extreme end		
Gang capacitor at approximately mid-position		

10 Get the work checked by the Instructor.

Construct and test RC phase-shift oscillator circuits

Objectives: At the end of this exercise you shall be able to


- construct and test RC phase shift oscillator circuit using transistor and vary the output frequency of the oscillator.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
• Trainees tool kit	- 1 Set	• Breadboard	- 1 No
• Regulated DC power supply, 0-30V/2A	- 1 No	• Resistor $\frac{1}{4}$ W/CR25	- 1 No each
• CRO, 20 MHz - Dual channel	- 1 No	10k Ω , 2k Ω , 680 Ω , 47k Ω	- 1 No each
• Digital frequency counter	- 1 No	• Resistor 4.7k Ω / $\frac{1}{4}$ W/CR25	- 2 Nos
• Soldering Iron 25W/230V with stand	- 1 No	• Capacitor 25VDC working	- 3 Nos
• Digital multimeter with probes	- 1 No	0.01 μ F	- 1 No each
		1 μ F, 22 μ F	- 1 No each
		• Transistor BC 107	- 1 No
		• POT 4.7k Ω	- 1 No
		• Hookup wire	- as reqd

PROCEDURE

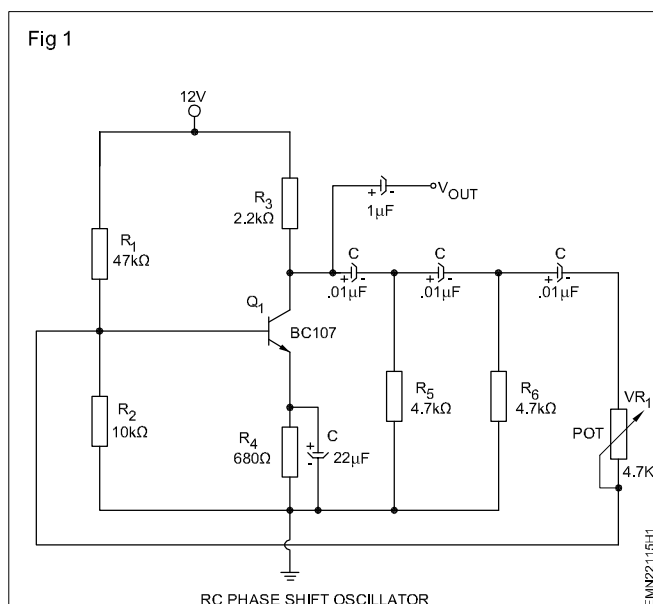TASK 1 : Construction and testing of RC phase shift oscillator circuit using transistor

- 1 Collect all the components from instructor and test them.
- 2 Assemble the RC phase-shift oscillator as shown in Fig 1 on the breadboard.



- 3 Get the assembled circuit checked by the Instructor.
- 4 Prepare the CRO for measurements and connect it across the output terminals.
- 5 Switch ON the 12VDC supply to the RC phase shift oscillator circuit and measure the output waveform using CRO.

If there is no output, adjust the value of POT to get the output; even after adjusting the POT no output is available consult the instructor.

- 6 Keep the preset VR₁ at maximum resistance position adjust the preset pot and observe the change in frequency/waveform on CRO.
- 7 Measure and record the oscillator output frequency in Table 1.
- 8 Measure the output using frequency counter also and record the readings in Table 1.
- 9 Adjust POT suitably and find the minimum and maximum frequency of oscillations of the circuit. Record the observations in Table.
- 10 Compare the calculated and measured frequency of the oscillator.
- 11 Get the work checked by the Instructor.

Table 1

Output frequency at different positions of R_3 preset Calculated frequency _____ Hz

Sl. No.	Position of preset VR_1	Frequency measured using CRO	Frequency measured using freq counter	$\left. \begin{array}{l} \text{Calculated} \\ \text{Frequency} \end{array} \right\} F = \frac{1}{2\pi RC\sqrt{6}}$
1	Minimum			
2	Middle			
3	Maximum			

Construct and test a crystal oscillator circuit

Objectives : At the end of this exercise you shall be able to

- **construct and test a Crystal oscillator using transistor.**

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Oscilloscope, 20 MHz Dual trace - 1 No
- Regulated DC power supply 0-30V/2A - 1 No
- Digital multimeter with probes - 1 No

Materials/Components


- Breadboard - 1 No
- Hook up wires - as reqd

- 8.44 MHz Crystal with holder - 1 No
- Capacitors - 25V DC wkg
 - 680pF - 1 No
 - 330pF - 1 No
- Capacitor 0.1μF - 2 Nos
- Transistor BF195 - 1 No
- Resistors ¼ W/CR25
 - 82kΩ, 18kΩ, 3.9kΩ, 390Ω - 1 No each

PROCEDURE

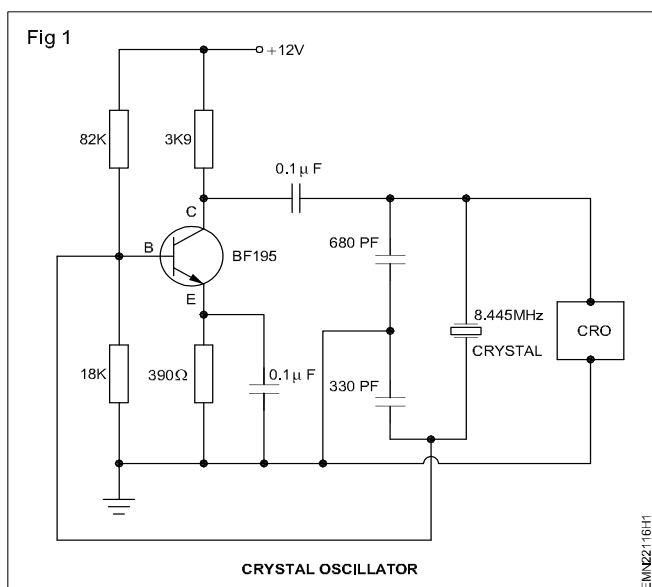TASK 1 : Construction and testing of crystal controlled Pierce oscillator

- 1 Record the frequency marked on the crystal.
- 2 Collect all the required components, test and assemble pierce crystal controlled oscillator circuit on breadboard as shown in Fig 1.
- 3 Connect 12V DC supply to the oscillator circuit.
- 4 Prepare the CRO for measurement and connect it across the output of the oscillator.
- 5 Adjust the CRO time-base to get a clear sinusoidal waveform on the screen. Measure and record the amplitude and frequency of oscillations.



If oscillations are not seen, the crystal may be bad. Consult your instructor.

- 6 Decrease the supply voltage to find and record the minimum V_{CC} voltage at which the crystal oscillator oscillates satisfactorily.
- 7 Get the working of the circuit and the recorded readings checked by the instructor.

TASK 2 : Construct and test a Pierce Crystal oscillator

- 1 Frequency marked on crystal : _____
- 2 (a) Amplitude of oscillations : _____
 (b) Frequency of oscillations : _____
- 3 (a) Minimum V_{CC} at which crystal oscillator work satisfactorily : _____
 (b) Output frequency : _____
 (c) Output amplitude : _____

Demonstrate Astable, Monostable and Bistable multivibrator circuits using transistors

Objectives : At the end of this exercise you shall be able to

- construct and test an astable multivibrator using transistors
- construct and test a monostable multivibrator using transistors
- construct and test a bistable multivibrator using transistors.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Oscilloscope 20 MHz Dual trace - 1 No
- Digital multimeter with probes - 1 No
- Regulated DC power supply 0-30V/2A - 1 No

Materials/Components

- Breadboard - 1 No
- Transistor BC 148 B - 2 Nos
- LED 5mm, Red and Green - 1 No each

- Resistors/1/4 W/CR25

- 100 k Ω - 2 Nos
- 1k Ω - 4 Nos
- 10 k Ω - 2 Nos
- 33 k Ω - 1 Nos
- 150 k Ω - 1 No


- Capacitors 25 V DC wkg

- 0.1 μ F - 2 Nos
- Diode- 1N4001 - 2 Nos
- Push button Switch (push-to-ON) - 2 Nos
- Hook up wires - as reqd

PROCEDURE

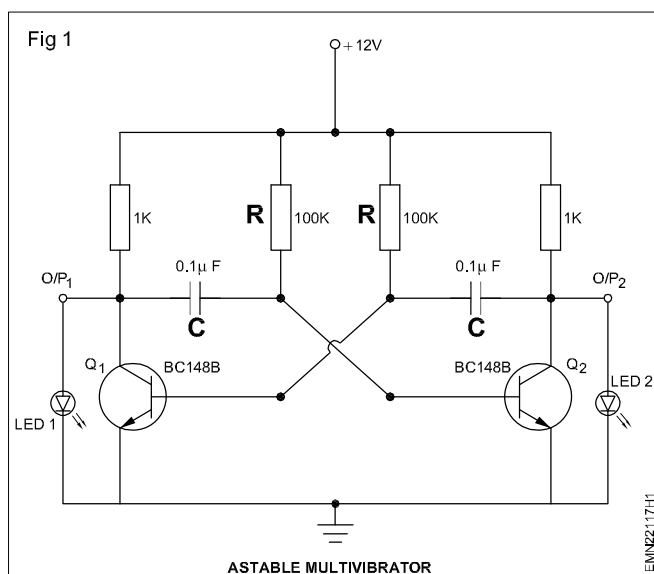TASK 1 : Construction and testing of astable multivibrator using transistors

- 1 Collect the required components, test and assemble the astable multivibrator on breadboard as shown in Fig 1.



- 2 Connect 12 V DC supply and switch ON the circuit.

1 (a) Calculated ON-time (t_{ON}) : (0.69 RC): _____

(b) Calculated OFF-time (t_{OFF}) : (0.69 RC) : _____

2 (a) Measured ON-time (t_{ON}) : _____

(b) Measured OFF-time (t_{OFF}) : _____

- 3 Prepare the CRO for measurements and connect it across any one of the collector of the transistor and ground.
- 4 Observe the waveform, measure the frequency of oscillation and record it in Table 1.
- 5 Calculate the ON time OFF time, PRF and record the values.
- 6 Observe the of LEDs and record in Table 1.


Table 1

Value of		Wave form at		Calculated frequency (PRF)	Measured frequency (PRF)	Status of LEDs	Remarks
R	C	Base	Collector				

7 Get the work checked by the Instructor.

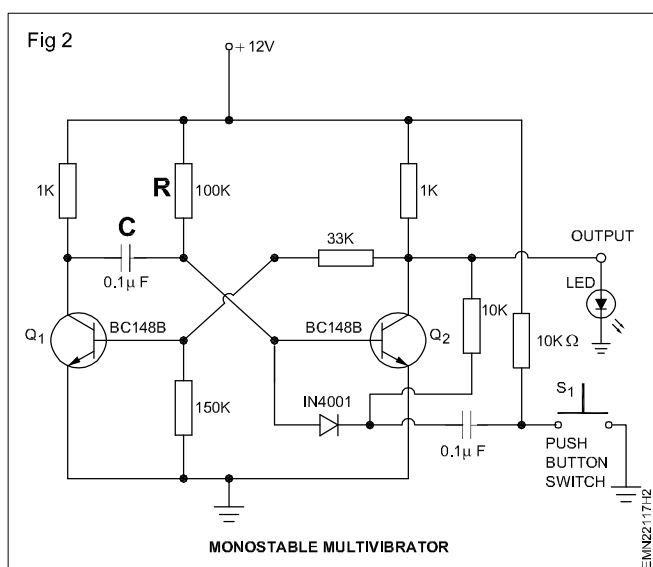TASK 2 : Construction and testing of monostable / One shot multivibrator using transistors

- 1 Assemble the monostable multivibrator as shown in Fig 2.



- Calculate and record the ON time of the monostable multivibrator.
- Get the circuit and calculated values checked by the Instructor.
- Switch ON 12 VDC supply to the circuit, connect the CRO probe at the collector of Q_1 with reference to ground.

1	Calculated ON time	:	_____
2	Measured ON time of the output pulse (t_{ON}) with $C = 100\mu F$:	_____
3	Calculated ON time	:	_____
	Measured ON time	:	_____


- Press switch S_1 and observe the LED and one single pulse output on CRO. Repeat this step for adjusting the CRO controls such that the pulse can be clearly seen on CRO.
- Press S_1 repeatedly such that the pulse keep appearing on the screen repeatedly. Measure and record the ON time of the pulse.

If the CRO used has storage option, use this option to measure the ON time more conveniently. Take the help of the instructor to use the storage option on the DSO.

- Change the value of the capacitor C from $0.1\mu F$ to $100\mu F$. Calculate and record the new ON-time of the pulse.
- Switch ON DC supply to the circuit. Press switch S_1 and observe the LED glowing. Try to find the approximate glow time using a stop watch record the glowing time of the LED.
- Get the working of the circuit checked by the Instructor.

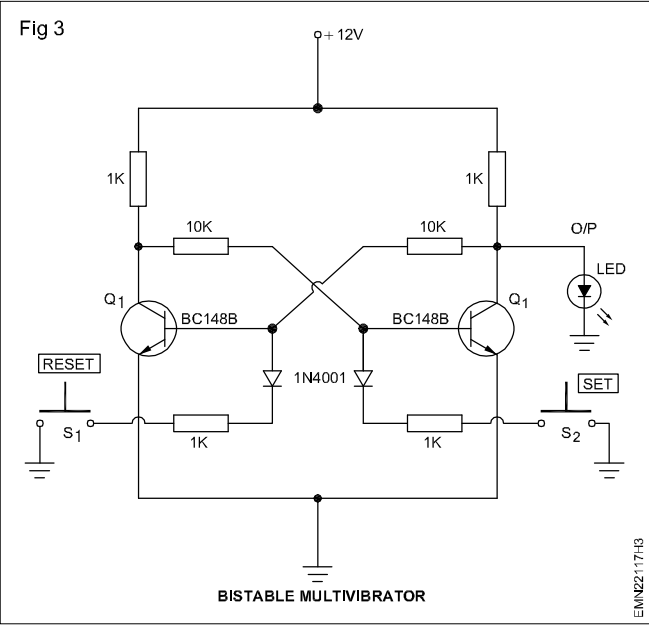TASK 3 : Construction and testing of Bistable multivibrator using transistors

1 Assemble the bistable multivibrator as shown in Fig 3.



- 2 Connect the 12VDC supply to the circuit and switch ON.
- 3 Press switch S_1 , observe the condition of LED.
- 4 Press switch S_2 , observe the condition of LED.
- 5 Record the observations in Table 1.

Table 1

Sl. No.	Switch to press	Output condition	
		(HIGH/LOW)	(Glow / No Glow)
	Set		
	Reset		

6 Get the work checked by the Instructor.

Construct and test shunt clipper

Objectives : At the end of this exercise you shall be able to

- construct and test the positive shunt clipper circuit using discrete components
- construct and test the shunt negative clipper circuit.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Function Generator - 1 No
- Oscilloscope 20 MHz - Dual trace - 1 No
- Regulated DC power supply 0-30V/2A - 1 No
- Digital multimeter with probe - 1 No

Materials/Components

- Diode 1N4007 - 1 No
- Resistor 10 k Ω /¼ W/CR25 - 1 No
- Breadboard - 1 No
- Hook up wires - as reqd


PROCEDURE

TASK 1 : Construction and testing of positive shunt clipper circuit using discrete components

- 1 Collect the components identify the diode number and cathode terminal.
- 2 Carry out quick test to confirm good working condition of the given diode using multimeter
- 3 Construct the positive shunt clipper circuit as shown in Fig 1 and verify the circuit connection by the Instructor.
- 4 Switch on the 5 VDC power supply to the shunt clipper circuit.
- 5 Set the function generator to sinewave output with 1kHz 10 V_{p-p}.
- 6 Prepare the CRO for measurements.
- 7 Observe the input waveform, output clipped waveform and record them in Table 1.
- 8 Use DMM measure the input, output voltages and record the readings in Table 1.

Table - 1

Sl. No.	Voltage	Waveform	Voltage as per CRO	Voltage as per DMM	Remarks
1	Input voltage				
2	Output voltage				

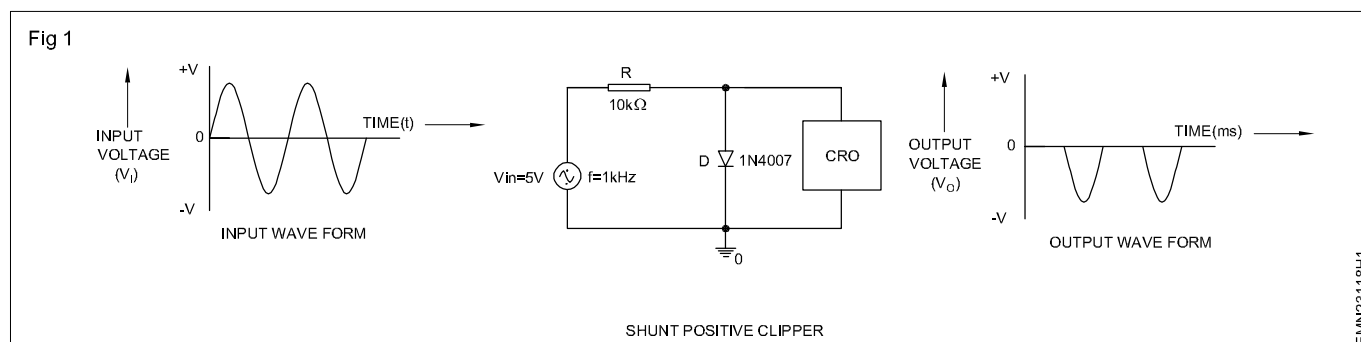


- 9 Get the work checked by the Instructor.

TASK 2 : Construction and testing of negative shunt clipper

- 1 Modify the polarities of the diode as shown in Fig 2 for negative shunt clipper circuit.
- 2 Repeat steps 4 to 8 of Task 1 and record the readings in Table 2

Table - 2

Sl. No.	Voltage	Waveform	Voltage as per CRO	Voltage as per DMM	Remarks
1	Input				
2	Output				

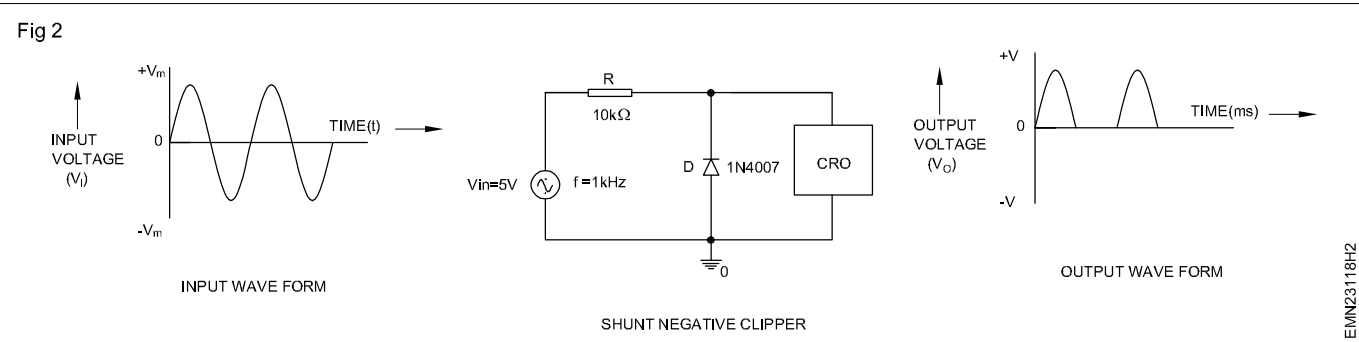

- 3 Ge the work checked by the Instructor.

Construct and test series and dual clipper circuit using diodes

Objectives : At the end of this exercise you shall be able to

- construct and test series negative clipper circuit using diode
- construct and test series positive clipper circuit using diode
- construct and test dual clipper circuit using diode.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Function Generator - 1 No
- CRO 20 MHz - Dual trace - 1 No
- Regulated DC power supply 0-30V/2A - 1 No
- Digital multimeter with probes - 1 No

Materials/Components

- Diode 1N4007 - 1 No
- Resistor 10 k Ω / $\frac{1}{4}$ W/CR25 - 1 No
- Breadboard - 1 No
- Hook up wires - as reqd

PROCEDURE


TASK 1 : Construction and testing of series negative clipper circuit using discrete components

- 1 Collect the components, identify the diode number and cathode terminal.
- 2 Carry out quick test to confirm good working condition of the given diode using multimeter.
- 3 Construct the series negative clipper circuit as shown in Fig 1 on breadboard and verify the circuit connection by the Instructor.
- 4 Switch ON the 5 VDC power supply to the series negative clipper circuit.
- 5 Set the function generator to sinewave output with 1kHz $10 V_{p-p}$.
- 6 Prepare the CRO for measurements.
- 7 Observe the input waveform, output clipped waveform and record them in Table 1.
- 8 Use DMM measure the input, output voltages and record the readings in Table 1.

Table - 1

Sl. No.	Voltage	Waveform	Voltage as per CRO	Voltage as per DMM	Remarks
1	Input				
2	Output				

Fig 1

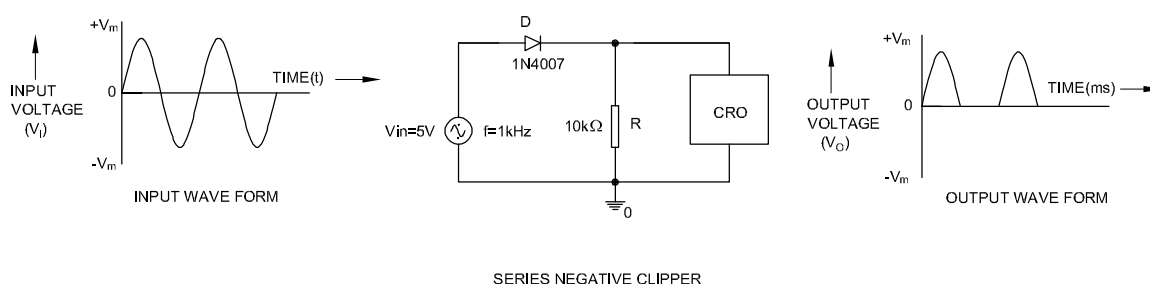


- 9 Get the work checked by the Instructor.

TASK 2 : Construction and testing of series positive clipper

- 1 Modify the polarities of the diode as shown in Fig 2 for series positive clipper.
- 2 Repeat steps 4 to 8 of Table 1 and record the readings in Table 2.

Table - 2

Sl. No.	Voltage	Waveform	Voltage as per CRO	Voltage as per DMM	Remarks
1	Input				
2	Output				

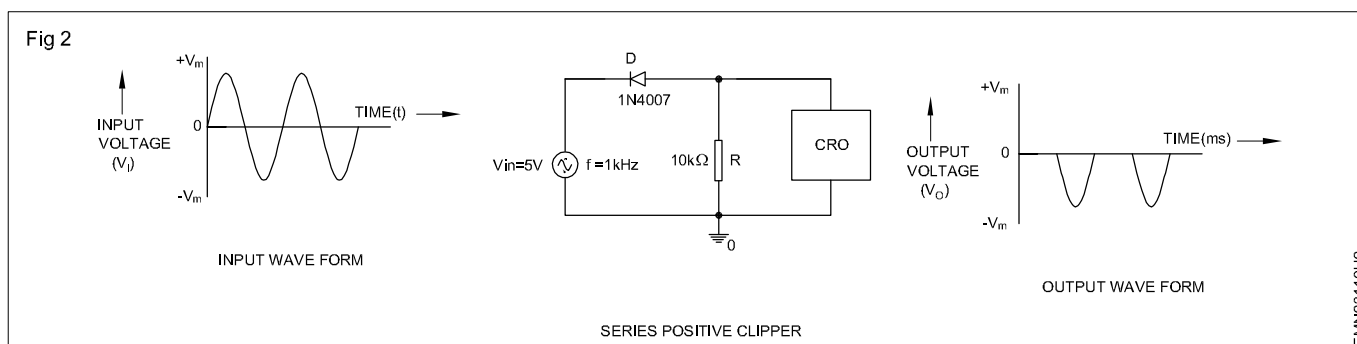


- 3 Get the work checked by the Instructor.

TASK 3 : Construction and testing of dual Clipper Circuit using discrete components

- 1 Collect the components, check them and assemble the dual clipper circuit on breadboard as shown in Fig 1.
- 2 Set 2V DC on both the sections of dual DC power supply and connect as V1 AND V2 as shown in the circuit.
- 3 Check and verify the circuit connection by the instructor.
- 4 Repeat steps 4 to 8 of Task 1 and record the readings in Table 3.

Table - 3

Sl. No.	Voltage	Waveform	Voltage as per CRO	Voltage as per DMM	Remarks
1	Input				
2	Output				

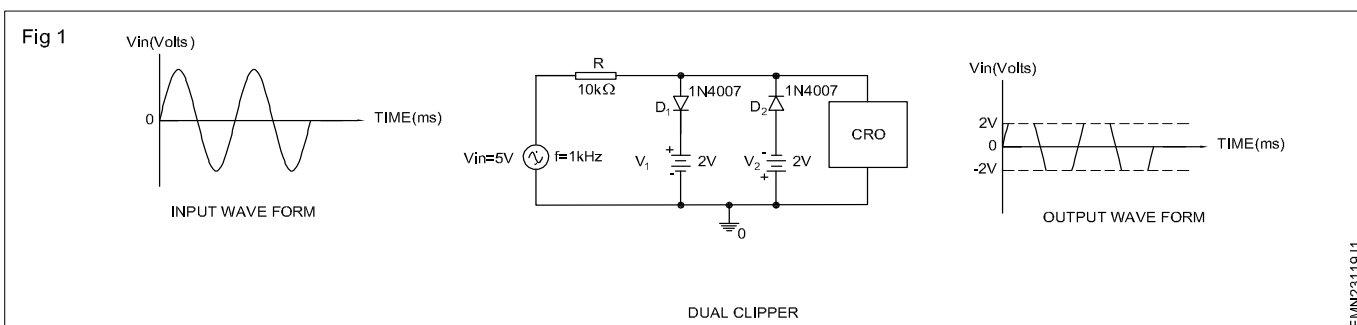

- 5 Ge the work checked by the Instructor.

Construct and test clamper circuit using diodes

Objectives : At the end of this exercise you shall be able to

- construct and test a positive clamper circuit using diode
- construct and test a negative clamper circuit using diode.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Function Generator 0-1 MHz - 1 No
- Oscilloscope 20 MHz - Dual trace - 1 No
- Regulated DC power supply 0-30V/2A - 1 No
- Digital multimeter with probes - 1 No

Materials/Components

- Diode 1N4007 - 1 No
- Resistor 10 k Ω / $\frac{1}{4}$ W/CR25 - 1 No
- Capacitor 0.1 μ F/25VDC - 1 Nos
- Breadboard - 1 No
- Connecting wires/Hook up wires - as reqd

PROCEDURE

TASK 1 : Construction and testing of positive clamper circuit using discrete components


- 1 Collect all the components required identify the diode number and cathode terminal.
- 2 Carryout quick test to confirm good working condition of the given diode using multimeter.
- 3 Construct the positive clamper circuit as shown in Fig 1 on breadboard.
- 4 Check and verify the circuit connection by the Instructor.
- 5 Switch ON the 5 VDC power supply to clamper circuit.
- 6 Set the Sinewave generator frequency to 1kHz and its output amplitude to 10 V_{p-p}.
- 7 Prepare the CRO for measurements.
- 8 Observe the output waveform on the CRO, and record the amplitude and time period from the waveforms in Table 1.
- 9 Measure the clamped voltage verify with the input voltage using DMM and record the observations in Table 1.

Safety precautions: Ensure the variable DC power supply control zero volt position.

Table - 1

Sl. No.	Voltage	Waveform	Voltage as per CRO	Voltage as per DMM	Remarks
1	Input				
2	Output				

Fig 1

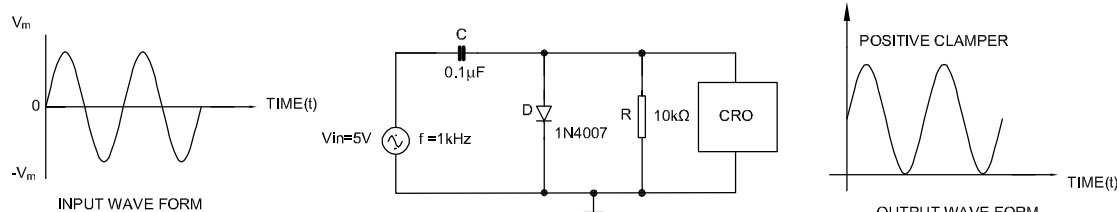


- 10 Get the work checked by the Instructor.

TASK 2 : Construction and testing of negative clamper circuit using discrete components

- 1 Modify the polarities of the diode as shown in Fig 2 for negative clamper circuit.
- 2 Repeat stpes 4 to 9 of Task 1 and record the observations in Table 2.

Table - 2

Sl. No.	Voltage	Waveform	Voltage as per CRO	Voltage as per DMM	Remarks
1	Input				
2	Output				

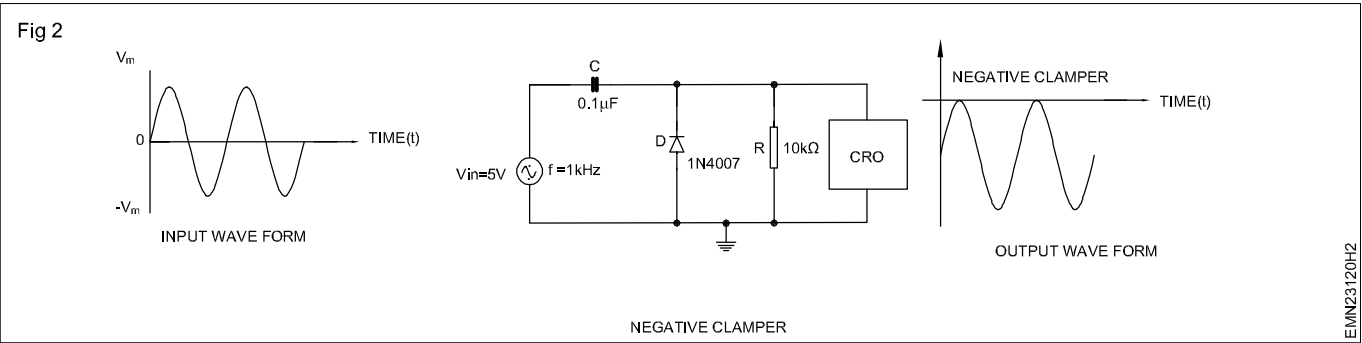

- 3 Get the work checked by the Instructor.

Construct and test zener diode as a peak clipper

Objectives : At the end of this exercise you shall be able to

- construct zener diode circuit as peak clipper
- test zener diode circuit.

Requirements

Tools/Equipments/Instruments

- | | |
|--------------------------------------|---------|
| • Trainees tool kit | - 1 Set |
| • Function Generator 0-1MHz | - 1 No |
| • Oscilloscope 20 MHz - Dual trace | - 1 No |
| • Regulated DC power supply 0-30V/2A | - 1 No |
| • Digital multimeter with probes | - 1 No |


Materials/Components

- | | |
|--|-----------|
| • Zener Diode BZX55 or equivalent | - 1 No |
| • Resistor 1k Ω 1/4 W/CR25 | - 1 No |
| • Breadboard | - 1 No |
| • Connecting wires/Hook up wires | - as reqd |
| Aids: Semiconductor data manual | - as reqd |

PROCEDURE

TASK 1 : Construction of peak clipper Circuit using Zener Diode

- 1 Collect the components and identify the Zener diode number and cathode terminal.
- 2 Carry out quick test to confirm good working condition of the given diode using multimeter.
- 3 Construct the peak clipper circuit as shown in Figure 1.
- 4 Check and verify the circuit connection by the Instructor.

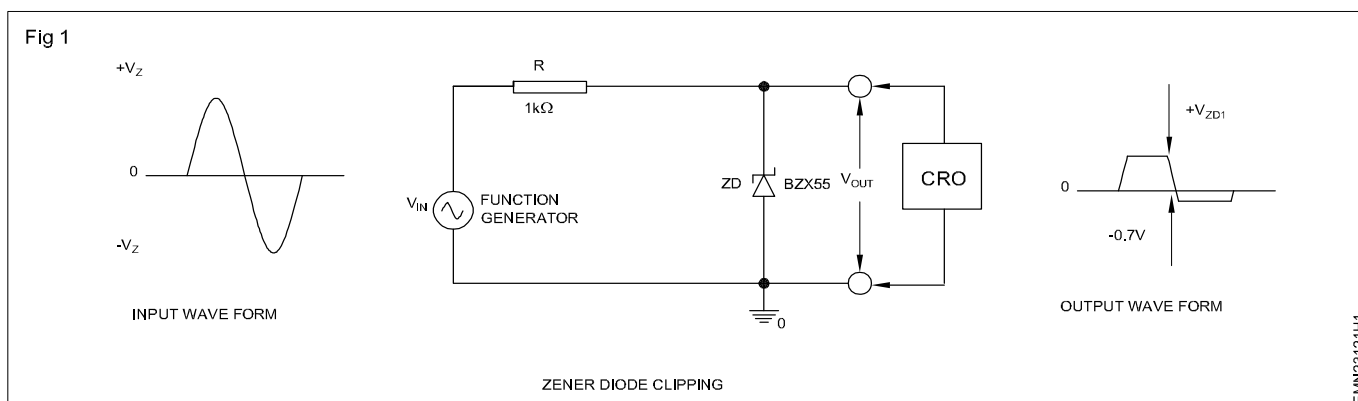

TASK 2 : Test the clipper circuit

- 1 Switch ON the 5 VDC power supply to the peak clipper circuit.
- 2 Switch ON the signal generator, apply Sinewave input amplitude greater than the clipping level of the zener diode.
- 3 Prepare the CRO for measurements.
- 4 Observe the output waveform on the CRO, record the amplitude and time period from the waveform in Table 1.
- 5 Measure the clipped voltage, verify with the input voltage using DMM and record the observations in Table 1.

Table - 1

Sl. No.	Voltage	Waveform	Voltage as per CRO	Voltage as per DMM	Remarks
1	Input				
2	Output				

- 6 Get the work checked by the Instructor.

Identify different power electronic components, their specification and terminals

Objectives : At the end of this exercise you shall be able to

- identify the terminals of FET, UJT and its specification using data manual
- identify the terminals of SCR, TRIAC, DIAC and its specification using data manual.

Requirements			
Tools/Equipments/Instruments		Material/Components	
• Trainees tool kit	- 1 Set	• Assorted types of N-Channel FET	- 3 Nos
• Semiconductor data manual for the active devices used for this exercise	- as reqd	• Assorted types of SCR	- 3 Nos
• Digital multimeter with probes	- 1 No	• Assorted types of UJT	- 2 Nos
Aids: Chart showing the pin out diagram of active devices used for this exercise	- as reqd	• Assorted types of TRIAC	- 2 Nos
		• Assorted types of DIAC	- 2 Nos
		• Plastic sleeves (2mm dia)-Red, Green, Yellow, Black	- 1 M each

Note: The instructor has to label the active devices used for this exercise

PROCEDURE

TASK 1 : Identification of leads of given FETs and its specifications using Data manual

- Collect the components and pick a labelled FET from the assorted lot record the code number of the FET and enter against its label number in Table 1.
 - Maximum forward gate current, I_G .
 - Pinch-off Voltage (at $I_D = 0$), V_P .
 - Maximum power dissipation, P_{max}
- Draw the pinout package diagram, refer to the chart/data manual/identify and record the following important specification of the FET based on its type Number, package type,
 - Polarity of the device (N-type/P-type)
 - Maximum drain-source Voltage, V_{DS}
 - Maximum gate-source Voltage, V_{GS}
 - Maximum drain current, I_D .
- Put sleeves of suitable length to the leads following the colour scheme given below.
 - Drain - Red
 - Source - Green
 - Gate - Yellow
 - Shield - Black
- Repeat steps 1 to 3 for the remaining labelled FETs.

Table 1

Sl. No.	Label	FET No.	Type	V_{DS}	V_{GS}	I_D	I_G	V_P	P_{max}	Package/ diagram pintout
1										
2										
3										

- Get the work checked by the Instructor.

TASK 2 : Identifications of UJT by its code number

- 1 Pick a labelled UJT, record the code number, refer to the data manual find and record the specification of the given UJTs in Table 2.
- 2 Draw the pinout/package diagram and mark the terminal.

Table 2

Sl.No	Type Label No.	Device code number	I_p	I_v	R_{BB}	h	Package pinout diagram
1							
2							

- 3 Get the work checked by the Instructor.

TASK 3 : Identification and specifications of SCR by its code number

- 1 Collect the components from the instructor and pick one of the labelled SCR from the assorted lot, note down the SCR label number and its Code number printed on the SCRI in Table 3.
- 2 Draw the package/pinout diagram of SCR identify the terminals of SCR referring to the data manual, and record the specifications in Table 3.

In some power SCRs, the metal case itself will act as anode. Mark "A" on the case using a pencil or put a RED colour dot using colour marker pen.

- 3 Repeat above steps for remaining labelled SCRs from the assorted lot.

Table 3

Sl. No.	Label No	Code number of SCR	V_{RRM}	$I_{T(RMS)}$	I_{TSM}	I_{GT}	V_{GT}	I_H	Package/ pinout diagram
1									
2									
3									

- 4 Get the work checked by the Instructor.

TASK 4 : Identification of leads of given TRIAC and its specifications using data manual

- 1 Pick a labelled TRIAC from the given lot, record the code number of the TRIAC against its label number in Table 4.
- 2 Draw the pinout/package diagram, refer to the chart/ data manual, identify and record the important specifications used on the code number in Table 4.
- 3 Repeat above steps for the remaining labelled TRIAC and record the observations in Table 4.

Table 4

Sl. No.	Label No.	Code number	Voltage off state	Current on-state (I_t)	Voltage gate trigger (V_{gt})	Current gate trigger (I_{gt})	Package pinout diagram
1							
2							

4 Get the work checked by the Instructor.

TASK 5 : Identification of leads of given DIAC and its specifications using data manual

- 1 Pick a labelled DIAC from the given lot, record the code number against its label number in Table 5.
- 2 Draw the package/terminal diagram, refer to the datasheet, identify and record the important specifications of the DIAC in Table 5.
- 3 Repeat above steps for the remaining labelled DIACs and record the observations in Table 5.

Table 5

Sl.No	Label No.	Code number	V_{BO}	I_{TRM}	T_j	Package pinout diagram
1						
2						

4 Get the work checked by the Instructor.

Construct and test a FET Amplifier

Objectives : At the end of this exercise you shall be able to

- construct a voltage amplifier using a JFET
- measure the gain of JFET amplifier with different input voltages
- calculate the gain of the amplifier at different frequencies.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Regulated DC power supply 0-30V/2A - 1 No
- Function generator - 1 No
- Soldering iron 25W/240VAC - 1 No
- Oscilloscope 0-20 MHz Dual trace - 1 No
- Digital multimeter with probes - 1 No

Materials/Components

- Assorted types of N-channel JFET - 4 Nos
- Plastic sleeves Red, Green, Yellow, Black - 4 Nos (each of 10mm length)

Aids: Semiconductor data manual/
data sheet of the FET

- as reqd

- Capacitors
5.6 nF/25V DC - 1 No
270 nF/25V DC - 1 No
6.8 μ F/25V - 1 No
- Resistors, $\frac{1}{4}$ W/CR25
10 k Ω - 1 No
12 k Ω - 1 No
47 k Ω - 1 No
1 M Ω - 1 No
- Solder, flux - as reqd
- Hook up wires - as reqd

One of the given JFET should be a BF 245B or BFW 10 or equivalent.

TASK 1 : Construction and testing of FET amplifier

- 1 Collect the required components, test and assemble the FET amplifier as shown in Fig 1.

Construct the circuit on a bread board or on a GPCB.

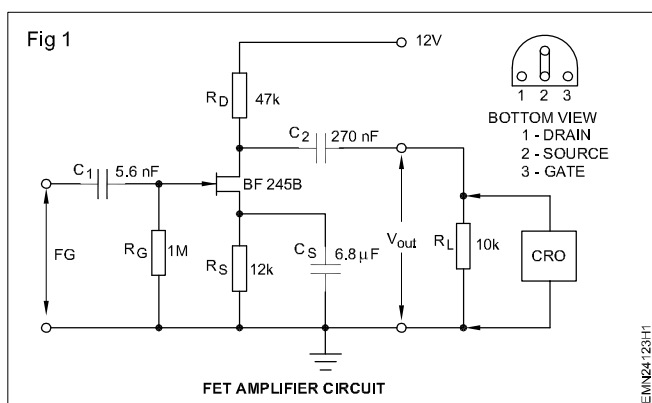


Table 1

Input frequency : 10 kHz			Gain= $\frac{\text{Output voltage}}{\text{Input voltage}}$
Sl. No.	Input voltage (mV)	O/P voltage	
1	100		
2	200		
3	300		
4	400		
5	500		
6	600		
7	700		
8	800		
9	900		
10	1000		

- 2 Get the assembled circuit checked by the instructor.
- 3 Switch ON the 12 VDC to the circuit.
- 4 Set the function generator output with sinewave at 10 kHz, 100 mV_{p-p} as the input to the FET amplifier.
- 5 Prepare the CRO for measurements and observe the output across the R_L .
- 6 Record the output reading in Table 1.

- 7 Increase the input voltage in steps of 100 mV upto 1V, record the observation in Table 1.
- 8 Calculate gain for each setting of input and record them.
- 9 Get the work checked by the Instructor.

TASK 2 : Measurement of gain of FET amplifier at different frequencies

- 1 Set the function generator output with sinewave at 20 kHz- 400 mV, switch ON the FET amplifier
- 2 Measure the output across R_L using CRO and record the readings in Table 2.
- 3 Increase the signal frequency from 20 kHz in steps of 20 kHz, measure the output voltage and record the readings in Table 2.
- 4 Calculate the gain for each setting of input and record them.
- 5 Get the work checked by the Instructor.

Table 2

Input volt 400mV		Gain = $\frac{\text{Output voltage}}{\text{Input voltage}}$
Frequency kHz	O/P Voltage	
40		
80		
100		
120		
150		

Construct and test a circuit of SCR using UJT triggering

Objectives : At the end of this exercise you shall be able to

- construct and test of SCR using UJT triggering.

Requirements				
Tools/Equipments/Instruments				
• Digital multimeter with probes	- 1 No	• Miniature toggle switch SPST	- 2 Nos	
• Trainees tool kit	- 1 Set	• SCR. Ty 6004	- 1 No	
• AC Power supply (0-250V)	- 1 No	• Variable Resistor pot 100 K	- 1 No	
• CRO, 0-20MHz-Dual channel	- 1 No	• Lamp 12V/5W with holder	- 1 Set	
		• Capacitor 100 μ F/25V, 10 μ F/25V	- 1 No each	
Materials/Components				
• Stepdown transformer		• Resistor		
230V/0-12V/500mA	- 1 No	100 Ω	- 2 Nos	
• Diode 1N4007	- 2 Nos	12 Ω	- 1 No	
• Zener diode 12V/1W	- 1 No	4.7 k Ω	- 1 No	
• LED-5mm/Red	- 1 No	3.3 k Ω	- 1 No	
• UJT 2N2646	- 1 No	560 Ω	- 1 No	
		1 k Ω	- 1 No	
Aids: Semiconductor data manual		• Gen purpose PCB	- 1 No	
data sheet of the LOT and SCR	- as reqd	• Rosin cored solder	- as reqd	
		• Hook up wire	- as reqd	

PROCEDURE

TASK 1 :


- 1 Collect all the components required, test them and confirm their working condition.
- 2 Plan the layout of components on the General purpose PCB, assemble the circuit as shown in Fig 1.
- 3 Verify the connections and get the assembled circuit checked by the Instructor.
- 4 Keep switch S2 open, switch ON mains supply to transformer, observe the LED is ON.
- 5 Measure the DC voltage at cathode of zener diode, B1 & B2 terminals of UJT and record the readings in Table 1.
- 6 Prepare CRO for measurements and observe the Pulse waveform at B2 terminal of UJT.
- 7 Close the switch S2 to allow AC supply to SCR, observe the Lamp is ON.
- 8 Measure the waveform across the Lamp and record the observations in Table 1.
- 9 Get the work checked by the Instructor.

Note: The Instructor has to adjust the preset slightly and observe the pulse frequency waveform, explain the reasons to trainees.

Table 1

Voltage across			Waveform across	
Zener diode	UJT B1	B2	B2	Lamp

Fig 1

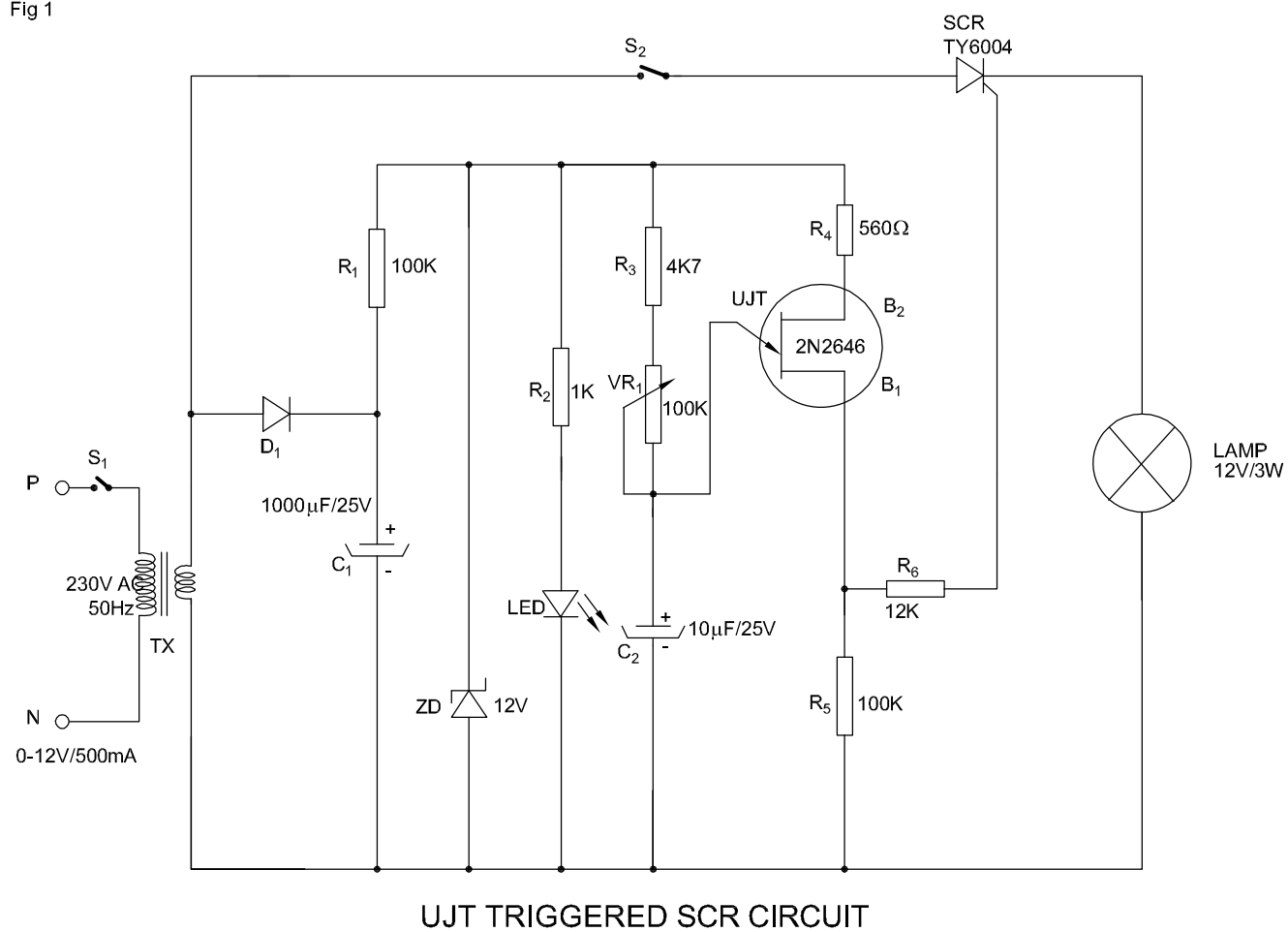

E:\MN24\124\H1

Identify different heatsinks used in SCRs

Objective : At the end of this exercise you shall be able to

- to identify different shapes and sizes of heatsinks used for SCRs.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
• Trainees tool kit	- 1 Set	• SCR with assorted rating (T0-3, T0-3P, T0-92, T0-220, T0-220AB, T0-126, T0-208AC, T0-247, T0-65, T0-32)	- 10 Nos
• International SCR data book	- 1 No	• Heat sinks for given SCR packages	- 10 Nos
• Data sheets of SCRs	- as reqd		
• Chart showing all types of heatsinks used for SCRs	- 1 No		

Note:

- 1 The Instructor has to provide minimum one SCR in each package type with label for all ratings of voltage/current and physical sizes.
- 2 Label all the heatsinks provided for this exercise with different method of coding.

PROCEDURE

- 1 Pick one of the labelled SCR, refer to data book identify the ratings package type etc., record those parameters in Table 1.
- 2 Repeat the above steps for all the labelled SCRs.
- 3 Identify the heat sink required for given SCR according to SCR current rating/Junction temperature with reference to the Chart 1.
- 4 Repeat the above step for the labelled items.

Table 1




Sl.No	SCR Label	Code number on SCR	Package type	Voltage rating	Current rating	V_{GT}	I_{GT}	T_J Junction temperature	Remarks
1									
2									
3									
4									
5									
6									
7									
8									
9									
10									

Table 2

Sl. No.	Heatsink Label No.	Suitable for SCR type Package No.	Remarks

- 5 Get the work checked by the Instructor.

Chart 1

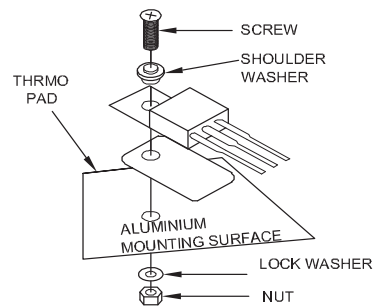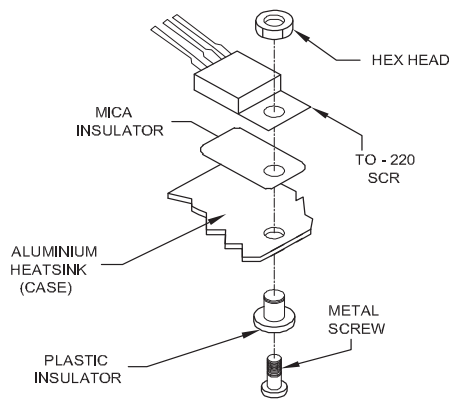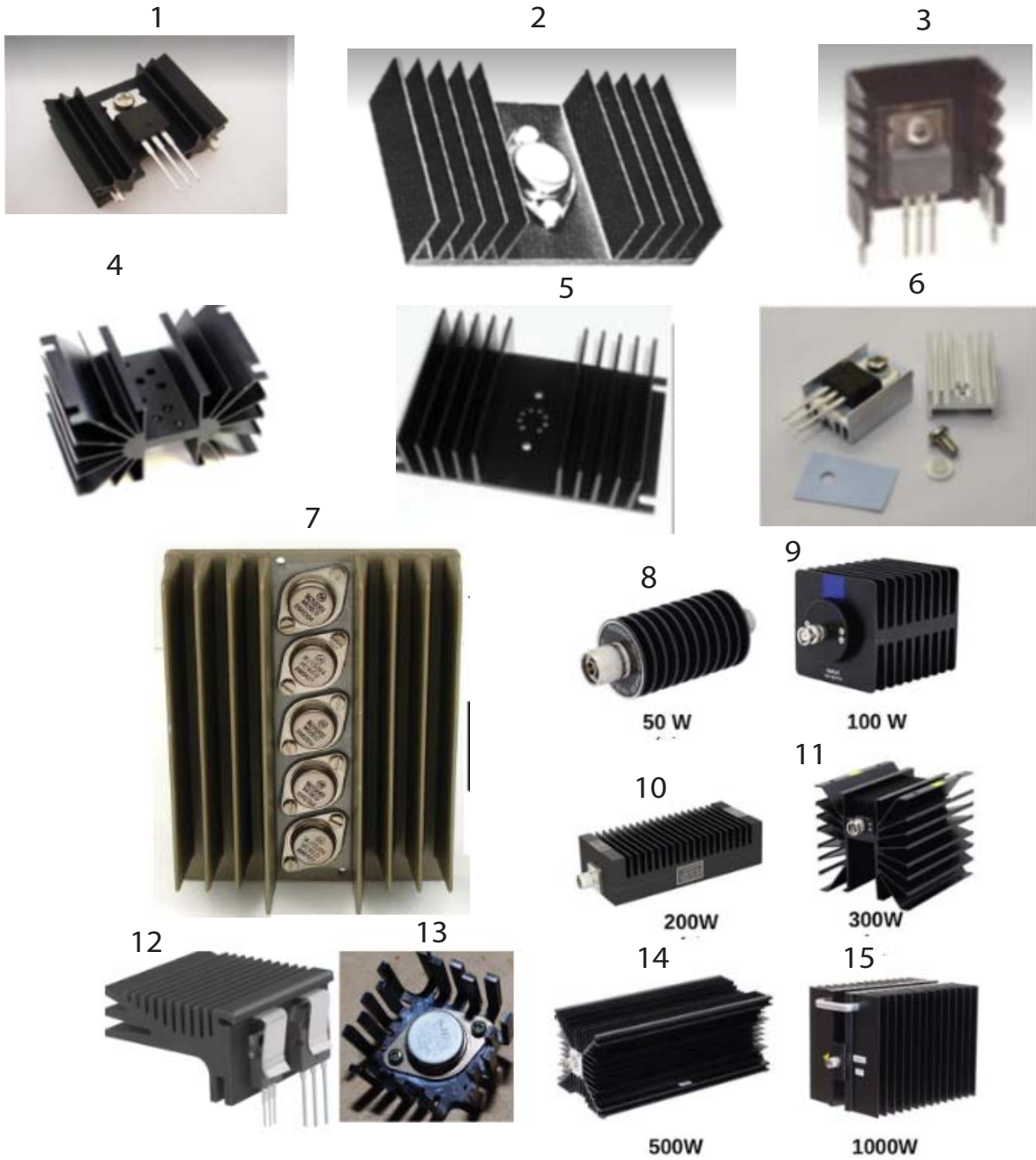

MOUNTING METHODS OF MOSFET ON HEATSINK

Construct a snubber circuit for protecting SCR use freewheeling diode to reduce back emf

Objective : At the end of this exercise you shall be able to

- construct a snubber circuit for protecting SCR and use free wheeling diode to reduce back emf.
- measure the waveform of gate trigger pulse and across the load.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Variac (0-260 VAC/5A) - 1 No
- Digital multimeter with probes - 1 No
- CRO, 0-20MHz Dual channel - 1 No
- Pulse generator/Function generator - 1 No

Materials/Components


- General purpose printed circuit Board - 1 No
- Resistors
120Ω, 100Ω/1W - 1 No each
- 30 VDC motor/2A - 1 No
- SCRTY6004 - 2 Nos
- Capacitor 680pF/1KV - 1 No
- DPST Switch - 1 No

Note: The instructor may use the assembled circuit of previous Ex.No.2.4.124 for this task with necessary additional components for snubber circuit across the SCR.

PROCEDURE

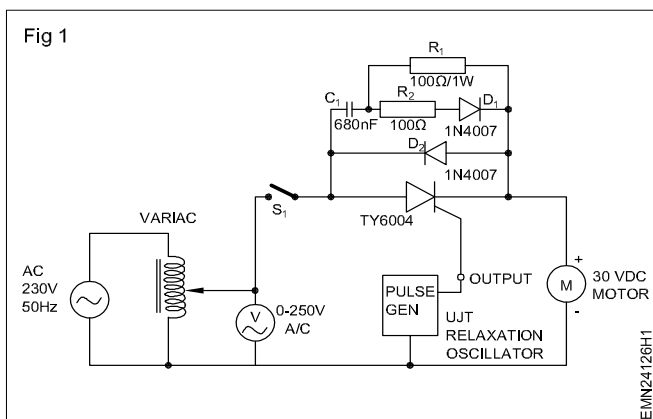TASK 1 : Construction snubber circuit for protecting SCR with free wheeling diode

- 1 Collect all the components, check them plan the layout of the circuit shown in Fig 1 on the general purpose PCB.



- 2 Fix the component as per the layout assemble the snubber circuit for SCR.
- 3 Get the assembled snubber circuit checked by the Instructor.
- 4 Connect the load (DC motor) and the pulse generator to the SCR circuit.
- 5 Keep the variac in zero volt position and connect to the AC mains supply.

- 6 Switch ON and adjust prepare the CRO for measurements.
- 7 Switch ON the AC mains supply, adjust /set the output of variac at 30 VAC to the circuit.
- 8 Switch ON the pulse generator and apply the gate triggering pulse to the SCR.
- 9 Measure the waveform at gate terminal across the load, and across the SCR.
- 10 Record the observation in Table 1.

Table 1

Sl. No	Test point	Waveform measured	Remarks
1	Gate terminal		
2	Across load		
3	Across SCR		

- 11 Get the work checked by the Instructor.

Construct a jig circuit to test DIAC

Objectives : At the end of this exercise you shall be able to

- construct the test jig circuit for DIAC
- test the DIAC in both directions.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Regulated DC power supply 0-30V/2A - 1 No
- Ammeter 0-5 mA (MC) - 1 No
- Voltmeter 0-50V DC (MC) - 1 No
- Digital multimeter with probes - 1 No
- Aids:** Semiconductor data manual /data sheet of the DIAC - as reqd


Materials/Components

- DIAC DB3 or equivalent - 1 No
- Resistor 5k Ω /5W - 1 No
- Breadboard - 1 No
- Hook up wires - as reqd

PROCEDURE

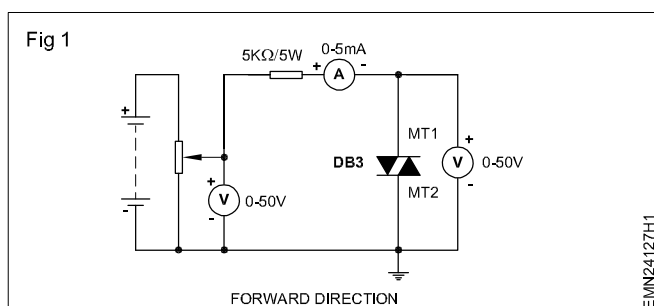TASK 1 : Testing the DIAC in one direction

- 1 Collect the DIAC and identify the terminals with reference to the Data sheet, note down the rating of the DIAC V_{BO} - I_{BO} .
- 2 Assemble the circuit on breadboard as shown in Fig 1.



- 3 Switch ON the DC power supply unit, increase the voltage to 5V.
- 4 Observe the ammeter, measure the voltage across DIAC and record the readings in Table 1.
- 5 Increase the DC voltage in steps of 5V upto 25V, record the readings.

Note: After reached 25V DC, carefully increase the voltage and observe the breakover of the DIAC.

- 6 Slowly increase the voltage in steps of 2V upto 30V and record the readings.


Table 1

Sl. No.	Applied Voltage	Current	Voltage across DIAC	Remarks
1	5V			
2	10V			
3	15V			
4	20V			
5	25V			
6	27V			
7	29V			
8	30V			

- 7 Get the work checked by the Instructor.

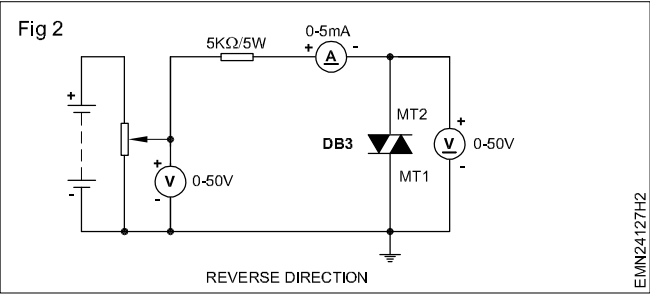TASK 2: Testing the DIAC in opposite direction

- 1 Reverse the polarity of the DIAC and connect the circuit as shown in Fig 2.



- 2 Repeat steps 3 to 6 and record the readings in Table 2.

Table 2

Sl. No.	Applied Voltage	Current	Voltage across DIAC	Remarks
1	5V			
2	10V			
3	15V			
4	20V			
5	25V			
6	27V			
7	29V			
8	30V			

- 3 Get the work checked by the Instructor.

Construct a simple dimmer circuit using TRIAC

Objectives: At the end of this exercise you shall be able to

- assemble and test a lamp dimmer circuit using TRIAC and DIAC
- test the lamp dimmer circuit using domestic fan.

Requirements

Tools/Equipments/Instruments

- Soldering iron 25W/230V - 1 No
- Trainees tool kit - 1 Set
- Lamp load (60 watts 230V) with holder - 1 No
- Digital multimeter with probes - 1 No

Materials/Components


- Printed circuit Board, (as Fig 2) - 1 No
- Resistors 180 ohms 1W, carbon film - 1 No
- 4.7 k Ω , ½ W - 1 No
- 470 k Ω , ½ W - 1 No

- Potentiometer 250k Ω , 16 mm plastic shaft - 1 No
- Capacitor 0.1 μ F 400 volts - 3 Nos
- TRIAC BT136 or equivalent - 1 No
- DIAC D3202 or equivalent - 1 No
- Inductor / Choke (25 SWG, 40 turns on 10mm ferrite rod with former made of leatheroid paper) - 1 No
- SPST switch flush type, 5 amps, 240V - 1 No
- Knob (for potentiometer) - 1 No
- 2 core mains cord, 240V/5 amps - 1 No
- Solder and Flux - as reqd
- Fuse 500 mA - 1 No
- Connecting wires - as reqd
- 2 core twisted pair flexible wire - 1 No

PROCEDURE

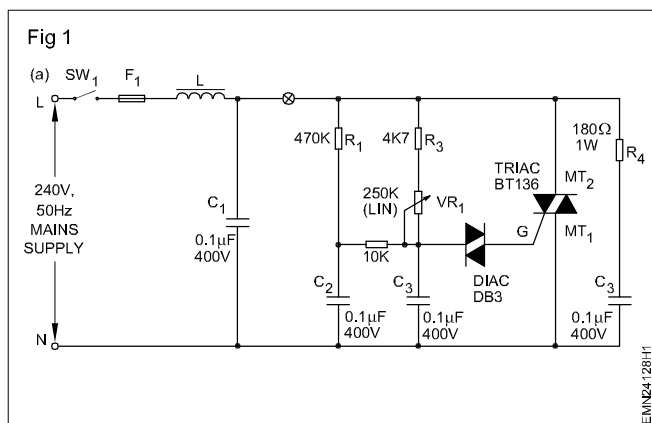TASK 1: Construction and testing of lamp dimmer using TRIAC and DIAC


- 1 Collect all the required components to assemble the circuit as shown in Fig 1



- 2 Plan the layout of components on the Gen.purpose PCB.

Use the dimmer circuit PCB if available as shown

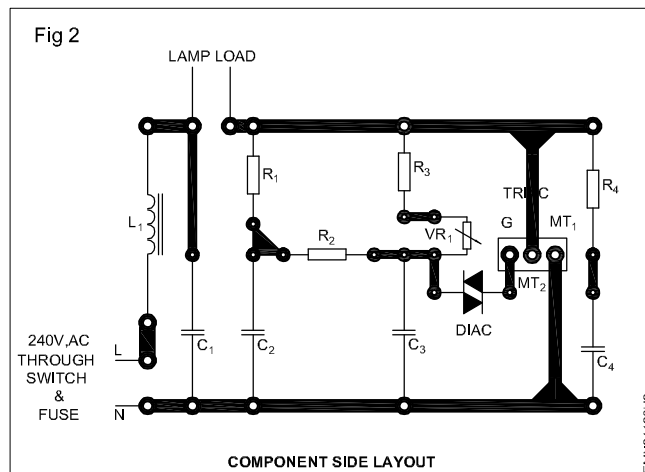- 3 Assemble the lamp dimmer circuit reference to the schematic diagram shown in Fig 1 & PCB layout diagram shown in Fig 2.



- 4 Get the wired circuit checked by the Instructor.
- 5 Connect the load and keep the lamp on a safe place to avoid heating nearby items.
- 6 Switch ON AC mains supply to the circuit, observe the lamp and increase the potentiometer position to the maximum brightness
- 7 Gradually decrease lamp brightness, and record the observations in Table - 2 (as dim, bright, very bright).
- 8 Get the work checked by the Instructor.

TASK 2 : Testing the lamp dimmer circuit to control the speed of domestic Fan

- 1 Remove the lamp load and connect the domestic fan across the terminals.
- 2 Keep the potentiometer at minimum position, switch ON AC mains supply to the circuit, gradually increase to maximum observing the rotation of fan speed.
- 3 Gradually decrease the speed and record the observations in Table 2 (as slow, medium, or fast).
- 4 Get the work checked by the instructor.

Table 1

Sl. No.	Potentiometer position	Fan speed	Remarks
1	Minimum		
2	Middle		
3	Maximum		

Construct UJT based free running oscillator and change its frequency

Objectives: At the end of this exercise you shall be able to

- construct and test free running oscillator
- measure time period and frequency.

Requirements			
Tools/Equipments/Instruments			
• Trainees tool kit	- 1 Set	• $10\Omega/1/4\text{ W}$	- 1 No
• CRO dual trace 20MHz	- 1 No	• Resistor $330\text{ Ohm}/1/4\text{ W}$	- 1 No
• Regulated DC power supply 0-30V/2A	- 1 No	• Preset $47\text{k}\Omega$	- 1 No
• Digital multimeter with probes	- 1 No	• Capacitor $0.1\mu\text{F}$	- 2 Nos
Materials/Components		• Hookup wires	- 1 No
• UJT 2646	- 1 No	• Breadboard	- 1 No
• Resistor $47\text{ ohm } 1/4\text{W}$	- 1 No	• Miniature toggle switch SPST	- 1 No

PROCEDURE

- 1 Collect all the components, test them to confirm their working condition.
- 2 Assemble the circuit on the breadboard as shown in Fig 1
- 3 Get the assembled circuit checked by the instructor.
- 4 Switch ON 12VDC power supply to the circuit
- 5 Prepare CRO for measurements, observe keeping preset value maximum
- 6 Observe the waveform across resistor R3 and record them in Table - 1
- 7 Measure time period & frequency of waveform compare with calculated values and record it.
- 8 Adjust the preset, change the value of VR measure the resistance value and record in Table - 1.
- 9 Repeat steps 6&7
- 10 Close switch S_1 to increase the value of 'c' and repeat steps 6&7

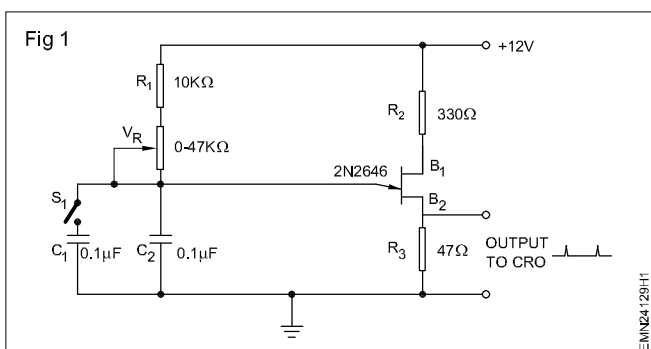


Table 1

Sl. No	Value of R	Value of C	Calculated frequency	Mesured frequency


Wave form

Across R_1

Across C

Table 2

UJT No.	Resistance						Conclusion
	B ₁ & B ₂		B ₁ & G		B ₂ & G		
	Forward	Reverse	Forward	Reverse	Forward	Reverse	

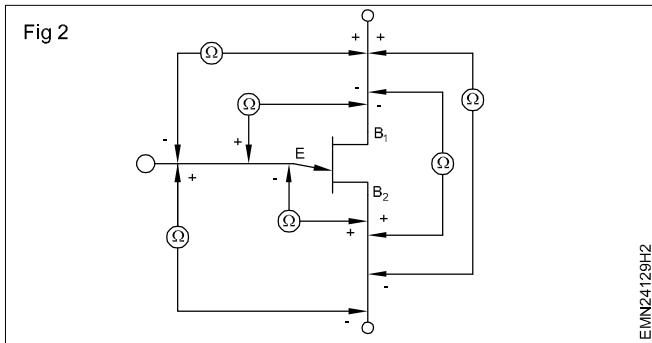

11 Get the work checked by the Instructor.

Identify various power MOSFETs by its number and test by using multimeter

Objectives: At the end of this exercise you shall be able to

- identify given MOSFET type by its number and test MOSFET using multimeter.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Digital multimeter with probes - 1 No
- MOSFET Data book - 1 No

Materials/Components

- MOSFET IRF 540 - 1 No
- IRFZ44 - 1 No
- IRF840 - 1 No


PROCEDURE

TASK 1: Identification of the given MOSFET by its number and testing with a multimeter

MOSFET is easily destroyed with static electricity, always ground yourself before working with one.

- 1 Note down the number, specification & type of given MOSFET by using MOSFET data book.
- 2 Identify which pins of the MOSFET are its source, gate and drain leads. Look up the device's part number in the MOSFET data book to verify its leads layout.
- 3 For testing the MOSFET using multimeter, hold the MOSFET by the case or the tab but don't touch the metal parts of the test probes with any of the other MOSFET'S terminals until needed. Do not allow a MOSFET to come in contact with your clothes, plastic or plastic products, etc. because of the high static voltages it can generate.

Fig 1

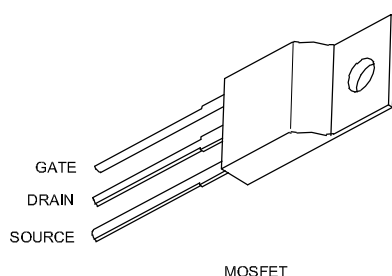

- 4 First, touch the multimeter positive lead onto the MOSFET'S 'Gate' and negative lead onto the source.

This testing procedure is for use with a digital multimeter in the diode test-range with a minimum of 3.3 volt over diode-under-test. If your multi-meter battery is less than that it will not do the test. Check your meter for the specification.

Table 1

Sl. No.	MOSFET No.	V_{GD}	V_{DS}	V_{GS}	Condition of MOSFET

- 5 Now move the positive probe to the 'Drain'. You should get a 'low' reading. The MOSFET'S internal capacitance on the gate has now been charged up by the meter and the device is 'turned-ON'.
- 6 With the meter positive still connected to the drain, touch a finger between source and gate (and drain if you like, it does not matter at this stage). The gate will be discharged through your finger and the meter reading should go high, indicating a non-conductive device/high resistance condition.

The above test means that, actually testing the cut-off voltage, which is basically the highest voltage put on the gate without making it conduct.

- 7 If the meter reading is low on both sides of V_{GS} (or) V_{DS} , then MOSFET is short circuited/defective.
- 8 Get the work checked by the Instructor.

Identify different heatsinks used with various power MOSFET devices

Objective: At the end of this exercise you shall be able to

- identify different shapes and sizes of heatsinks used for power MOSFETs.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
• Trainees tool kit	- 1 Set	• MOSFET with assorted rating (T0-3P, T0-220, T0-220AB, T0-247, T0-247 plus)	- 5 Nos
• Semiconductor data manual	- 1 No	• Heat sinks for given MOSFET	- 5 Nos
		• MOSFET Data book	- 1 No

Note:

- 1 The Instructor has to provide minimum on MOSFET in each package type with label for each one.
- 2 Label all the heat sinks provided with label numbers.

PROCEDURE

- 1 Pick one of the labelled MOSFET, identify the rating current capacity & junction to case thermal resistance of given MOSFET from data sheet record the parameters in Table 1.
- 2 Identify the heat sink required for given MOSFET according to current capacity of MOSFET with reference to the chart 1.
- 3 Draw the pictorial diagram & note down the specification of heat sink selected in Table 2.
- 4 Repeat the above steps for all the labelled items in Table 1 & 2.

Typically an aluminum heatsink, with fins to increase the surface area, is used to dissipate this energy to air. Higher current capacity controllers use a fan to force the air to pass through the fins in order to increase heat dissipation. Water cooled heatsinks are used on MOSFET with very high current ratings.



Table 1

Sl. No.	Label No.	Code no on MOSFET	package type	Voltage rating	Current rating	Junction temperature	Remarks
1							
2							
3							
4							
5							

Table 2

Sl. No.	Heatsink label no.	Suitable for MOSFET number	Package type number	Heatsink outline diagram
1				
2				
3				
4				
5				

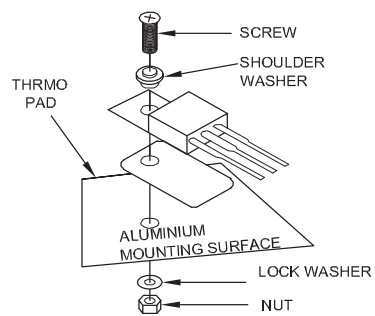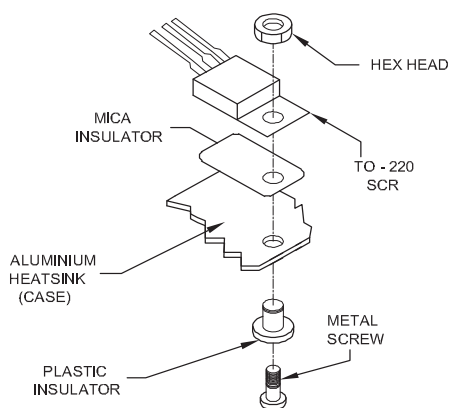- 5 Get the work checked by the Instructor.



MOUNTING METHODS OF MOSFET ON HEATSINK

Construct MOSFET test circuit with a small load

Objectives: At the end of this exercise you shall be able to

- to construct MOSFET test circuit with a small load.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Regulated DC power supply 0-30V/2A - 1 No
- Multimeter with probes - 1 No

Materials/Components


- MOSFET (assorted number) - 5 Nos
- Resistor 1k Ω , ¼ W/CR25 - 1 No

- Resistor 100 Ohm/ ¼ W/CR25 - 1 No
- Resistor 68k Ω /¼ W/CR25 - 1 No
- ON/OFF Switch - 2 Nos
- Socket for MOSFET - 1 No
- 12V lamp - 1 No
- Hook up wires - as reqd
- Solder flux - as reqd
- Connecting wires - as reqd
- PCB/Bread board - 1 No

PROCEDURE

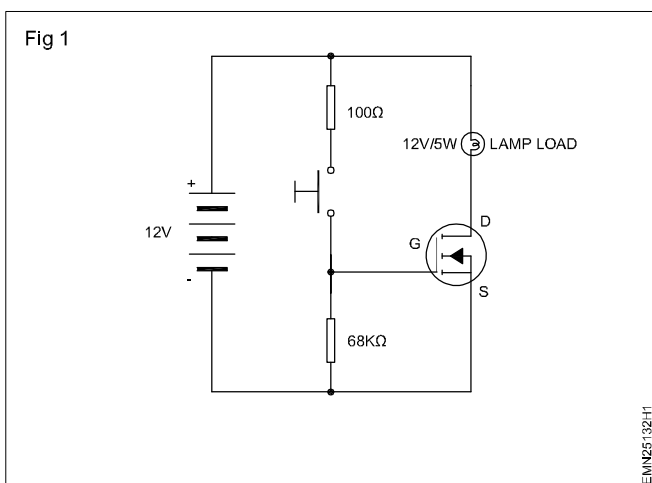TASK 1 :

- 1 Check the working condition of all given components with multimeter.
- 2 Assemble the circuit on bread board as shown in the circuit Fig 1.



- 3 Insert MOSFET (to be checked) in socket.
- 4 Power on the supply, Press switch S and observe that lamp glows. This means MOSFET is turned ON. Note down the status of lamp in Table 1.
- 5 Thus MOSFET act as open switch if gate voltage is zero. If gate voltage is applied then the MOSFET will act as closed switch then the working condition of MOSFET is good/ON.
- 6 If the MOSFET is P-channel then reverse the polarity of power supply and lamp load then check the condition of lamp load.

Table 1

Sl. No.	MOSFET No.	Type	Status of lamp ON/OFF	MOSFET Condition

- 7 Get the work checked by the Instructor.

Identify IGBTs by their numbers and test by using multimeter

Objectives: At the end of this exercise you shall be able to

- identify IGBT by its number, specification, pin configuration type and application
- test IGBT by using multimeter.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
• Trainees tool kit	- 1 Set	• IGBT with assorted rating	- 5 Nos
• Multimeter with probes	- 1 No	• IGBT data book	- 1 No

PROCEDURE

TASK 1 : Identification of IGBTs by their number, pin configuration of type

- 1 Note down the number printed on given device.
- 2 Identify the number in data book and note IGBT type.
- 3 Record the specification like voltage & current rating of given IGBT in Table 1.
- 4 Identify the terminals gate, emitter & collector with the help of the data book.

Table

Sl.No.	IGBT No.	Specifications							
		VR (Voltage Rating)	CR (Current Rating)	ID (Gate Input Drive)	II (Input Impedence)	OI (Output Impedence)	SS (Switching Speed)	Pin confi- guration	Application

TASK 2 : Testing of IGBT using multimeter

- 1 To test IGBT with multimeter use meter in diode checking mode with battery voltage of less than 20 V.
- 2 To test collector emitter junction remove the conductive foam and short the gate to the emitter
- 3 As the multimeter is in diode check mode, the collector to emitter should give a normal diode reading with positive on the collector and negative on the emitter.
- 4 The multimeter should read open or infinite with collector negative and emitter positive.
- 5 If IGBT is damaged it may test as shorted in both positive and negative directions, open in both directions, or low resistive in both directions.
- 6 For gate oxide test keep the meter in resistance mode, where the resistance from gate to collector and gate to emitter should be infinite on a good device
- 7 If it is a damaged device it appears shorted or have leakage resistance from gate to collector and/ or emitter.
- 8 Get the work checked by the Instructor.

Note: The input section of IGBT junctions like a MOSFET and the output section of IGBT functions like a bipolar junction transistor.

Construct IGBT test circuit with a small load

Objectives: At the end of this exercise you shall be able to

- to determine the working condition of IGBT by using test circuit.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Regulated DC power supply 0-30V/2A - 1 No
- Multimeter with probes - 1 No

Materials/Components


- IGBT (5SMV 86M1731) - 5 Nos
- Resistor $1k\Omega/1/4$ W - 1 No
- Resistor $2.2k\Omega/1/4$ W - 2 Nos
- ON/OFF Switch - 2 Nos
- Socket for IGBT - 1 No
- Breadboard - 1 No
- 12V lamp - 1 No

PROCEDURE

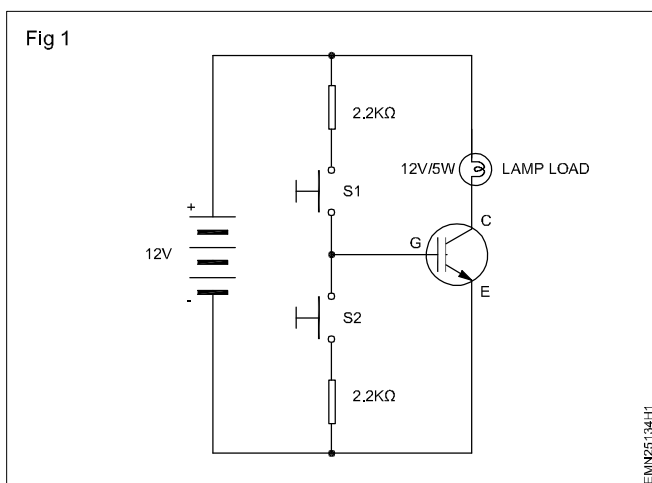TASK 1 : Construction and testing of IGBT test circuit

- 1 Collect and check the working condition of all the given components by multimeter.
- 2 Assemble the circuit on breadboard as shown in Fig 1.
- 5 Switch OFF S_1 and press switch S_2 observe that lamp will turn OFF this means IGBT is turned OFF.

Thus IGBT act as open switch if gate voltage is not provided. If positive gate voltage is applied then the IGBT will act as closed switch then the working condition of IGBT is good.



- 3 Insert IGBT (to be checked) in socket.
- 4 Power ON the supply & Press switch S_1 and observe that lamp load will glow this means IGBT is turned ON.

- 7 Test all given IGBT by using above procedure.
- 8 Note down the readings on Table 1.

Table 1

Sl. No.	IGBT No.	S_1 Position	S_2 Position	Lamp ON/OFF	IGBT Condition
1		Closed	Open		
		Open	Closed		
2		Closed	Open		
		Open	Closed		
3		Closed	Open		
		Open	Closed		

- 9 Get the work checked by the Instructor.

Test LEDs with DC supply and measure voltage drop and current using multimeter

Objectives: At the end of this exercise you shall be able to


- measure voltage drop and current using multimeter by testing LED.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
• Trainees tool kit	- 1 Set	• LED (assorted colour, Type & size)	- 10 Nos
• Digital multimeter with probes	- 1 No		
• Ammeter (0-50) mA	- 1 No		

PROCEDURE

- 1 Note down the type of LED by physical identification. (ie. Single colour 5mm LED, Miniature, flashing LED, Bi-colour or tri-colour) and for details look-into the data sheet.
- 2 Determine the Anode and Cathode terminals of the LED.

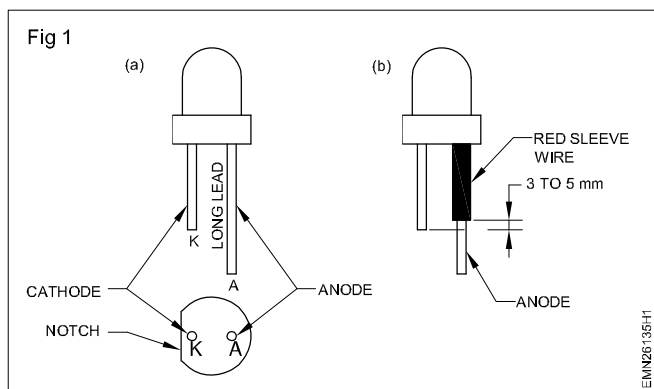If it is a new LED, the long leg should be the anode(+) and the short leg is the cathode(-). You can also look inside the LED and the larger electrode is cathode and the smaller electrode is the anode (+).



- 3 Turn digital multimeter ON and set it to diode mode testing position will be marked by a diode symbol.

Note: In diode mode and resistance mode of testing using multimeter, the battery of the multimeter is engaged for providing DC bias (or) DC supply voltage required for testing.

- 4 Clip the positive(+) of meter to the predetermined anode(+) of the LED and the negative(-) to the cathode (-). The LED should glow and shows bias in display.
- 5 If the connection is correct and the LED does not light up then LED is bad.
- 6 Connect ammeter in series with the LED and measure current.

Note: Max forward voltage that can be applied to a 5mm LED can draw is only 20 ma. SO always use a current limiting resistor in series with an LED (for using in the circuits)

- 7 Record it in Table 1.
- 8 Repeat the procedure for testing other LEDs.

Table 1

Sl. No.	Type of LED	LED ON/OFF	Voltage drop	I when LED is ON

- 9 Get the work checked by the Instructor.

Construct a circuit to test photo voltaic cell

Objectives: At the end of this exercise you shall be able to


- construct a simple photovoltaic (PV) system, using a PV cell(s) and a DC ammeter
- learn how the amount and wavelength of light affect the generation of electricity.

Requirements		
Tools/Equipments/Instruments		Materials/Components
<ul style="list-style-type: none"> • Trainees tool kit • DC ammeter 0-500 mA • DC volt meter 0-24V • Multimeter/DMM with probes 	<ul style="list-style-type: none"> - 1 Set - 1 No - 1 No - 1 No 	<ul style="list-style-type: none"> • Small PV cells • Sheets of colored transparency film in different colors • Two electrical leads with crocodile clips • Source of bright light or access to direct sunlight (desk lamp or flashlight could be substituted) • Goggles/gloves
		<ul style="list-style-type: none"> - as reqd - 1 Set

PROCEDURE

TASK 1: Constructing the Photovoltaic Energy System for Light Source Changes

- 1 If your PV cell mini panel does not have wires already attached to it, you should attach 15 cm of wire to each node of the PV cell. The cell should have either clips or hooks around which you can manually twist the wire.
- 2 Follow the Instructor safety instructions and attach the red wire from the PV cell to the red lead of the volt meter and ammeter (either clip or connect the wires together).
- 3 Similarly, connect the black wires from the PV cell to the negative terminal black lead of the voltmeter.
- 4 Connect the 6V/4.5Ah battery between negative terminal of Ammeter and negative terminal of solar panel.
- 4 Use the direct light/other source on the PV cell to see if you are getting a current reading. If the ammeter shows no current, check the wire connections.
- 5 Check DC voltage across battery.

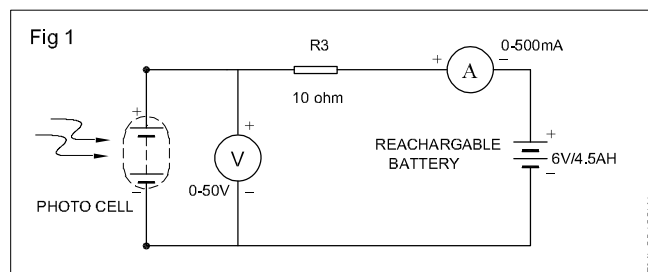

TASK 2: Performing the Activity for Light

- 1 Keeping the sunlight constant (or the light source at constant distance), cover the PV cell(s) with a piece of coloured transparency film. Repeat with the other colours of transparency film and then use just direct sunlight alone (or light substitute). Record the current generated for all colours tested and for direct light in Data Table 1.

Note that different colours (wave lengths) of light on the solar panel produces different voltage. It is concluded that the wave length of light affects the electricity.

Table 1 Effect of Colour (Wavelength) on Cell Current

Color of Filter	Current	Remarks
Red		
Green		
Blue		
Yellow		
No filter		

- 2 With just 1 PV cell in the circuit, shade 1/4 of the PV cell with a piece of cardboard or paper and take a reading. Shade 1/2, 3/4 and then all of the photovoltaic cell. Record the readings in Data Table 2.

Table 2 Effect of Shading on Cell Current

Amount of Shade Current	Current
No shade	
1/4 covered	
1/2 covered	
3/4 covered	
All covered	

Note:-

Safety Precautions to be followed while handling photo-voltaic cells.

- 1 Do not press (or) apply pressure on PV cell (a) panel, they may break (or) cause injury or damage to the solar panel.**
- 2 Make sure you entire PV system is properly and safely earth grounded to prevent electrical shock and injury.**
- 3 When the solar panel is exposed to sunlight, do not touch any electrical lubricant (or) wiring with bare hands. Wear goggles to protect eyes from bright-light.**

- 3 Get the work checked by the Instructor.

Construct a circuit to switch a lamp load using photo diode

Objectives: At the end of this exercise you shall be able to

- construct a circuit to switch a lamp using photo diode and test the working of photo diode.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- DC Power Supply 0-30V/2A - 1 No
- Multimeter with probes - 1 No

Materials/Components

- Photo diode BPW 34 - 1 No
- POT 4.7k Ω /1W, linear - 1 No
- Relay (SPST) 12V - 1 No
- Transistor BC548 - 1 No
- Lamp 12V - 1 No
- Diode 1N4007 - 1 No
- Breadboard - 1 No

PROCEDURE

- 1 Check all given component using multimeter for good working condition.
- 2 Assemble the circuit on bread board as shown in diagram, connect a lamp to relay contact.
- 3 Switch on DC power supply, cover photo diode with card board. & observe the position of relay & load lamp. At this position relay will be activated and the lamp will produce light as shown in Fig 1.
- 4 Expose the photo diode with a light (gran IR LED or with torch light) & note down the position of relay and lamp condition. Lamp will not produce output.
- 5 Record the observation in the Table 1.

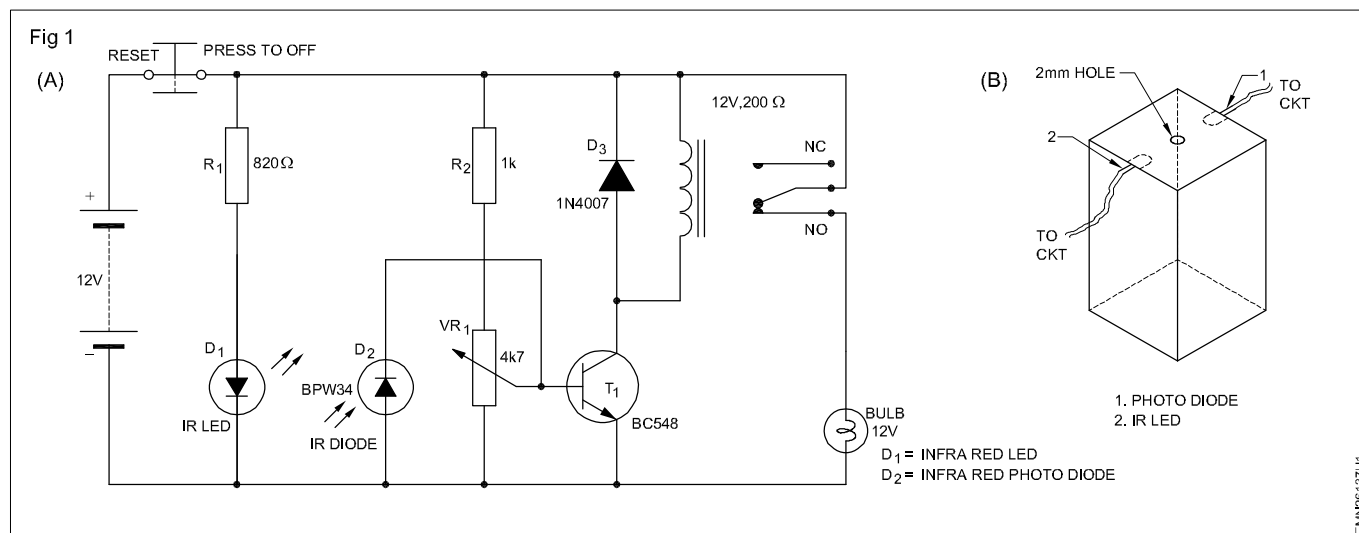


Table 1

Sl. No	Light falling on photo diode	Relay position	Lamp condition
1	Darkness		
2	Exposed to Lamp light		

- 6 Get the work checked by the Instructor.

Construct a circuit to switch a lamp load using photo transistor

Objectives: At the end of this exercise you shall be able to

- construct a circuit to switch a lamp using photo transistor and test the working of photo transistor.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
<ul style="list-style-type: none">• Trainees tool kit• DC Power Supply, 0-30V/2A• Multimeter DMM with probes	- 1 Set	• Photo transistor PT 1504-6B	- 1 No
	- 1 No	• POT 100kΩ/1W, linear	- 1 No
	- 1 No	• Transistor 2N2222	- 1 No
		• Relay 6 V	- 1 No
		• Lamp - Green, Red 12V/5W	- 1 No each
		• Breadboard	- 1 No

PROCEDURE

TASK 1: Construction and testing of photo transistor using a switch and lamp load

- 1 Test all given component on multimeter for good working condition.

2 Assemble the circuit on bread board as shown in fig 1.

3 Cover photo transistor with card board & switch on the DC & AC power supply.

4 Relay will be OFF hence lamp L₂ will turn ON & L₁ will remain OFF.
- 5 Now remove card board & expose phototransistor to light Lamp of 10W & again observe position of relay. Now relay will be activated & Lamp L₁ will turn ON & Lamp L₂ will turn OFF.

6 Note down position of phototransistor, Relay & Lamp in observation Table 1.

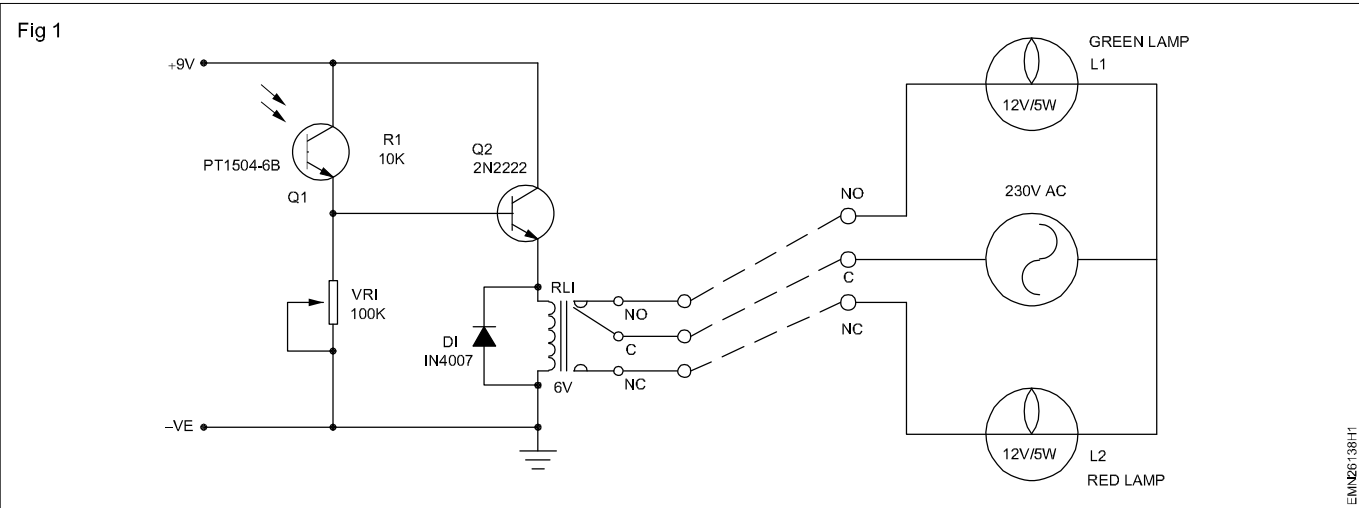


Table 1				
SI . No	Light falling on photo transistor	Relay position	Lamp L ₁	Lamp L ₂
1	Darkness			
2	Exposed to Lamp light			

- 7 Get the work checked by the Instructor.

Identify Opto coupler input and output terminals and measure the quantum of Isolation between input/output terminals and operate a relay by connecting a switch

Objectives: At the end of this exercise you shall be able to

- identify the input & output terminal by referring data manual and measure the quantum of isolation between I/O terminals
- operate a relay by using opto-coupler.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- DC Power Supply 0-30V/2A - 1 No
- DC Power Supply 0-5V/2A - 1 No

Materials/Components

- Opto coupler IC - 4N25 (opto transistor) - 1 No
- Opto-TRIAC IC - MOC3011 - 1 No
- Opto-SCR-H11C4 - 1 No
- Relay 12 V - 1 No
- Diode 1N4007 - 1 No
- Lamp 40W - 1 No

PROCEDURE

TASK 1: Identification of the terminals of Opto-coupler

- 1 Collect the components and note down the number & type of opto-coupler from data book.
- 2 Identify the terminal 1 by Index mark on IC.
- 3 Identify other terminals by using data book & note down the observation in Table 1 for all given opto-coupler ICs.

Fig 1

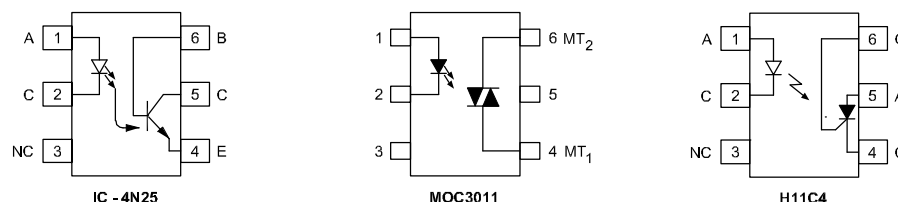


Table 1

Sl. No	Opto coupler type No.	Input Voltage to Opto-coupler	O/P resistance/Bias across terminal					
			B	C	E	G	A	K

- 1 Assemble the circuit on bread board as shown in Fig 2.
- 2 Switch ON 12V DC supply and AC mains.
- 3 Note down the position of relay & load lamp.
- 4 Now apply 5V DC supply at the input terminal of opto-coupler & observe the position of relay & load lamp.
- 5 Note down the observation in Table-2.
- 6 Get the work checked by the Instructor.

Identify different logic gates (AND, OR, NAND, NOR, EX-OR, EX-NOR, NOT ICs) by the number printed on them

Objectives: At the end of this exercise you shall be able to

- identify different logic gates by the IC number printed on them
- identify various ICs and their specifications using data sheet/semiconductor data manual.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
• Trainees tool kit	- 1 Set	• Breadboard	- 1 No
• Logic Gates (IC) trainer Kit	- 1 No	• Connecting Patch Cords	- as reqd
• Digital multimeter with probes	- 1 No	• IC 7400, IC 7408, IC 7432	
• Data sheet of ICs used	- as reqd	IC 74266, IC 7402, IC 7404	
		IC 7486	- 1 No each

PROCEDURE

Note: The Instructor has to provide/ensure ICs with their number printed on them is clearly visible and all the ICs are inserted on a bread board safely.

Safety precaution: Do not touch the pins of the ICs with fingers.

- 1 Pick one of the ICs note down the number in Table -1
- 2 Refer to the data sheet/semiconductor data manual, find the logic gate function, draw the pin out diagram, mark the input, output and supply pin numbers.
- 3 Repeat the steps for remaining ICs and record the observations in Table-1.

Table 1

Sl.No.	IC number	Logic gate	Symbol	Pin out diagram
1	IC 7408			
2	IC 7432			
3	IC 7404			
4	IC 7400			
5	IC 7402			
6	IC 7486			
7	IC 74266			

- 4 Get the work checked by the Instructor.

Verify the truth tables of all logic gate ICs by connecting switches and LEDs

Objectives: At the end of this exercise you shall be able to

- construct AND, OR, NOT, NAND, NOR and EX-OR gates using ICs
- verify truth tables of AND, OR, NOT, NAND, NOR and EX-OR gates using switches and LEDs.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Regulated DC power supply 0-30V/2A - 1 No
- Digital multimeter with probes - 1 No

Materials/Components

- Breadboard - 1 No
- IC 7408 - 1 No
- IC - 7432 - 1 No

- IC-7486 - 1 No
- IC-7400 - 1 No
- SPDT Switches (Miniature Toggle) - 2 Nos
- IC 7404 - 1 No
- Hook up wire, red and black - as reqd
- Flexible wires - as reqd
- Resistor/¼ W/CR25 - 1 No
- 330Ω - 1 No
- LED 5mm, Red - 1 No
- Data sheets of ICs used - as reqd

PROCEDURE

TASK 1 : Construction and AND gate using IC 7408 and verification of its truth table

- 1 Collect all the components, check them, refer to the data sheet of the IC 7408, assemble the AND gate as shown in Fig 1 on the bread board.

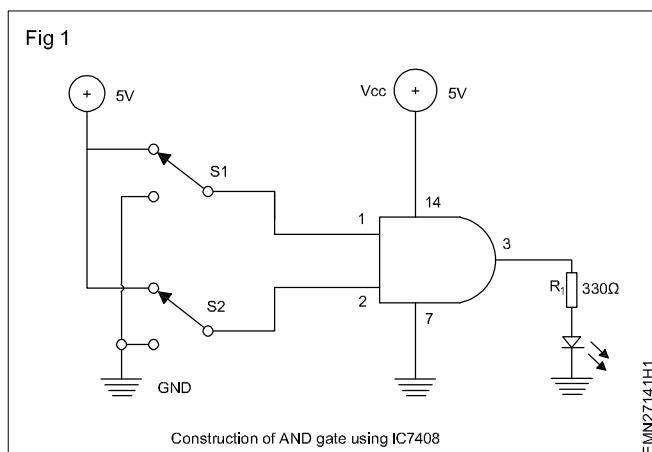


Table 1

Sl.No.	Input		Output LED status
	A	B	
1			
2			
3			
4			

AND gate Truth table


Sl.No.	Input		Output Y=A.B
	A	B	
1	0	0	0
2	0	1	0
3	1	0	0
4	1	1	1

- 2 Use toggle switches S_1 as input A and switch S_2 as input B.
- 3 Get the assemble circuit checked by the Instructor.
- 4 Switch ON 5VDC supply and operate switches S_1 & S_2 for different levels either in 5V position or zero volt (GND) position as shown in Table 1.
- 5 Observe the status of LED for each step of combinations, record the observations in Table 1.

- 6 Verify the readings with the truth table of AND gate.
- 7 Get the work checked by the Instructor.

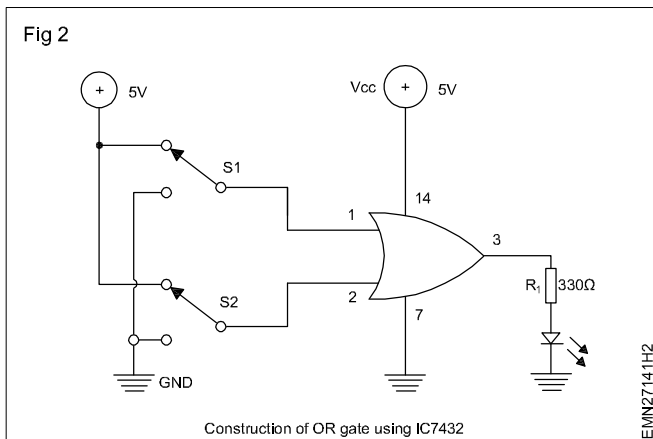TASK 2 : Construction of OR gate using IC 7432 and verification of its Truth table

- 1 Collect all the components, check them, refer to the data sheet of the IC 7432, assemble the OR gate as shown in Fig 2 on the bread board.



- 2 Repeat steps 2 to 5 of Task 1 and record the observations in Table 2.
- 3 Verify the readings with the truth table of OR gate.
- 4 Get the work checked by the Instructor.

Table 2


Sl.No.	Input		Output LED status
	A	B	
1			
2			
3			
4			

OR gate Truth table

Sl.No.	Input		Output Y=A+B
	A	B	
1	0	0	0
2	0	1	1
3	1	0	1
4	1	1	1

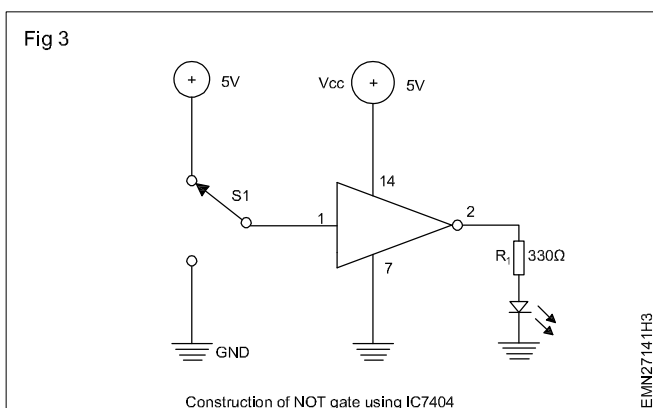TASK 3 : Construction of NOT gate using IC 7404 and verification of its Truth table

- 1 Collect all the components, check them, refer to the data sheet of the IC 7404, assemble the NOT gate as shown in Fig 3 on the bread board.



- 2 Use toggle switches S_1 as input A.
- 3 Repeat steps 3 to 5 of Task 1 and record the observations in Table 3.
- 4 Verify the readings with the truth table of NOT gate.
- 5 Get the work checked by the Instructor.

Table 3


Sl.No.	Input	Output LED status
	A	
1		
2		

NOT gate Truth table

Sl.No.	Input	Output Y= \bar{A}
	A	
1	0	1
2	1	0

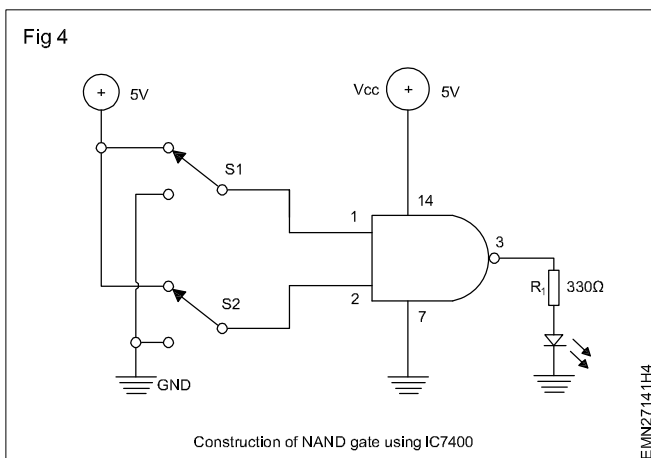TASK 4 : Construction of NAND gate using IC 7400 and verification of its Truth table

- 1 Collect all the components, check them, refer to the data sheet of the IC 7400, assemble the AND gate as shown in Fig 4 on the bread board.



- 2 Repeat steps 2 to 5 of Task 1 and record the observations in Table 4.
- 3 Verify the readings with the truth table of NAND gate.
- 4 Get the work checked by the Instructor.

Table 4


Sl.No.	Input		Output LED status
	A	B	
1			
2			
3			
4			

NAND gate Truth table

Sl.No.	Input		Output $Y=A.B$
	A	B	
1	0	0	1
2	0	1	1
3	1	0	1
4	1	1	0

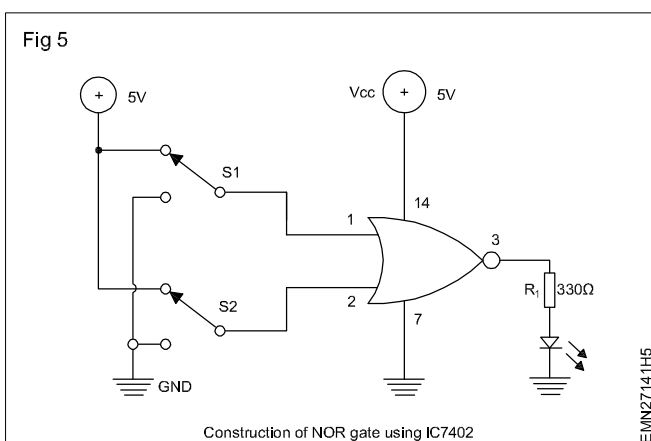TASK 5 : Construction of NOR gate using IC 7402 and verification of its Truth table

- 1 Collect all the components, check them, refer to the data sheet of the IC 7402, assemble the NOR gate as shown in Fig 5 on the bread board.



- 2 Repeat steps 2 to 5 of Task 1 and record the observations in Table 5.
- 3 Verify the readings with the truth table of NOR gate.
- 4 Get the work checked by the Instructor.

Table 5


Sl.No.	Input		Output LED status
	A	B	
1			
2			
3			
4			

NOR gate Truth table

Sl.No.	Input		Output $Y=A+B$
	A	B	
1	0	0	1
2	0	1	0
3	1	0	0
4	1	1	0

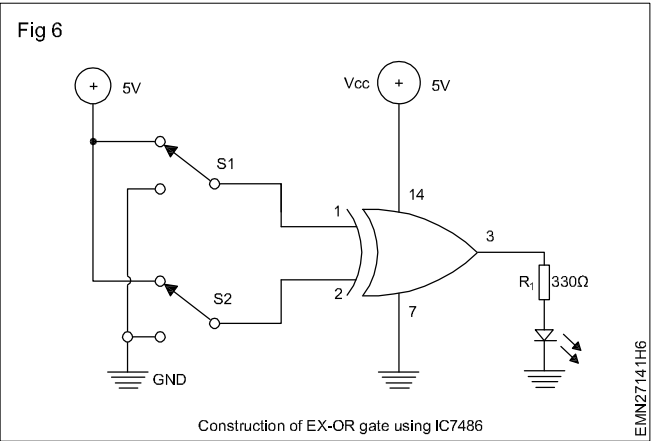TASK 5 : Construction of EX-OR gate using IC 7486 and verification of its Truth table

- 1 Collect all the components, check them, refer to the data sheet of the IC 7486, assemble the EX-OR gate as shown in Fig 6 on the bread board.



- 2 Repeat steps 2 to 5 of Task 1 and record the observations in Table 6.
- 3 Verify the readings with the truth table of EX-OR gate.
- 4 Get the work checked by the Instructor.

Table 6

Sl.No.	Input		Output LED status
	A	B	
1			
2			
3			
4			

EX-OR gate Truth table

Sl.No.	Input		Output $Y=A\oplus B$
	A	B	
1	0	0	0
2	0	1	1
3	1	0	1
4	1	1	0

Construct and verify the truth table of all the gates using NAND and NOR gates

Objectives : At the end of this exercise you shall be able to

- construct AND, OR, NOT, NOR, EX-OR and EX-NOR gates using NAND gate
- construct AND, OR, NOT, NAND, EX-OR and EX-NOR gates using NOR gates.

Requirements

Tools/Equipments/Instruments/Data Manuals

- Logic probe - 1 No
- Trainees tool kit - 1 Set
- Regulated DC power supply 0-30V/2A - 1 No
- Digital multimeter with probes - 1 No

Materials/Components

- Digital IC data manual - 1 No
- IC 7400 - 2 Nos

- IC 7402 - 2 Nos
- Hook up wires - as reqd
- 14 pin IC base - 4 Nos
- Toggle switches miniature type SPDT - 2 Nos
- Bread board - 1 No
- LED 5mm, Red - 1 No
- Resistor - 330Ω/1/4W - 1 No

Note:

- 1 The Instructor has to guide the trainees to record 5VDC given to gate input as logic high (1) and GND (zero volt) as logic low (0)
- 2 The condition of LED ON as Logic '1' and OFF as logic '0'.

PROCEDURE

TASK 1 : Construction of AND gate circuit using NAND gate IC 7400 and verification of its truth table

- 1 Collect all the components, check them, refer to the data sheet of the IC 7400, assemble the AND gate as shown in Fig 1 on the bread board.
- 5 Observe the LED for each step of combinations, record the observations in Table 1.


AND gate Truth table

Sl.No.	Input		Output Y=A.B
	A S ₁	B S ₂	
1	0	0	0
2	0	1	0
3	1	0	0
4	1	1	1

Table 1

Sl.No.	Input		Output LED Condition
	A S ₁	B S ₂	
1			
2			
3			
4			

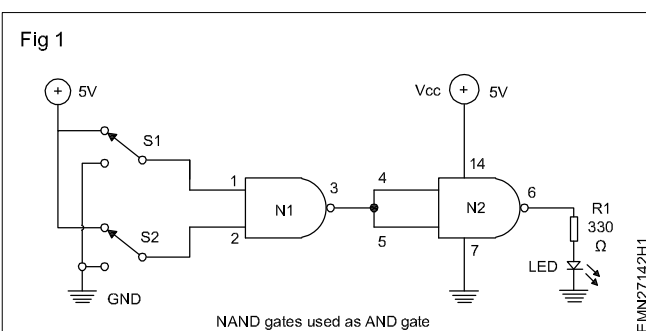
- 6 Get the work checked by the Instructor.



- 2 Use toggle switches S₁ as input A and switch S₂ as input B.
- 3 Get the assembled circuit checked by the Instructor.
- 4 Switch ON 5VDC supply and operate switches S₁ & S₂ for different logic levels either in 5V position or zero volt position as shown in Table 1.

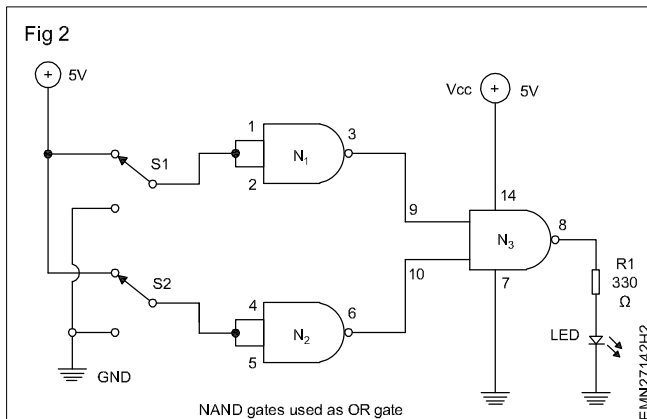TASK 2 : Construction of OR gate circuit using NAND gate and verification of its truth table

- 1 Rearrange the connections and assemble the OR gate circuit using NAND gates as shown in Fig 2 on bread board.



- 2 Repeat steps 2 to 5 of Task 1 and record the observations in Table 2.
- 3 Verify the readings with the truth table of OR gate.
- 4 Get the work checked by the Instructor.

Note: Use logic probe to check the status of each pin to confirm the functioning of each gate.

OR gate Truth table


Sl.No.	Input		Output $Y=A+B$
	A	B	
1	0	0	0
2	0	1	1
3	1	0	1
4	1	1	1

Table 2

Sl.No.	Input		Output LED
	A	B	
1			
2			
3			
4			

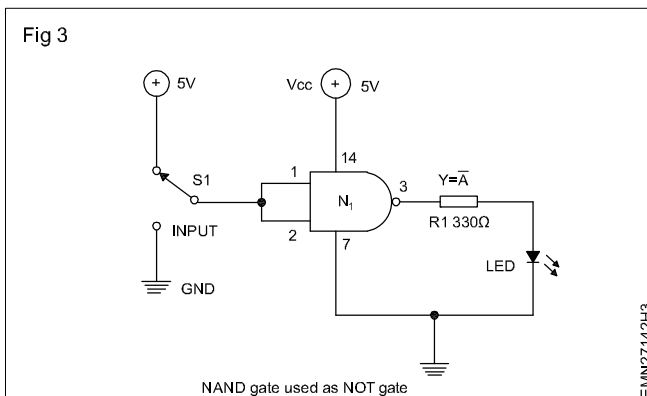TASK 3: Construction of NOT gate circuit using NAND gate and verification of its truth table

- 1 Rearrange the connections and assemble the NOT gate circuit using NAND gates as shown in Fig 3 on bread board.



- 2 Use toggle switch S_1 as input A.
- 3 Repeat steps 3 to 5 of Task 1 and record the observations in Table 3.
- 4 Get the work checked by the Instructor.

NOT gate Truth table


Sl.No.	Input	Output $Y=\overline{A}$
	A	
1	0	1
2	1	0

Table 3

Sl.No.	Input	Output LED
	A	
1	0	
2	1	

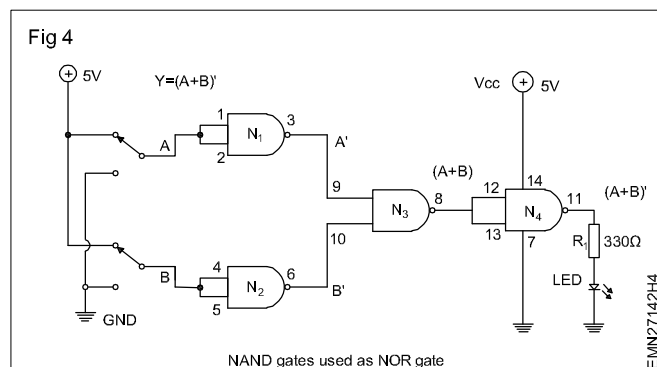TASK 4 : Construction of NOR gate circuit using NAND gate and verification of its truth table

- 1 Rearrange the connections and assemble the NOR gate circuit using NAND gates as shown in Fig 4 on breadboard.



- 2 Repeat steps 2 to 5 of Task 1, and record the observations in Table 4.
- 3 Verify the readings with the truth table of NOR gate.
- 4 Get the work checked by the Instructor.

Note: Use logic probe to check the status of each pin to confirm the functioning of each gate.

NOR gate Truth table


Sl.No.	Input		Output $Y = \overline{A+B}$
	A	B	
1	0	0	1
2	0	1	0
3	1	0	0
4	1	1	0

Table 4

Sl.No.	Input		Output LED
	A	B	
1			
2			
3			
4			

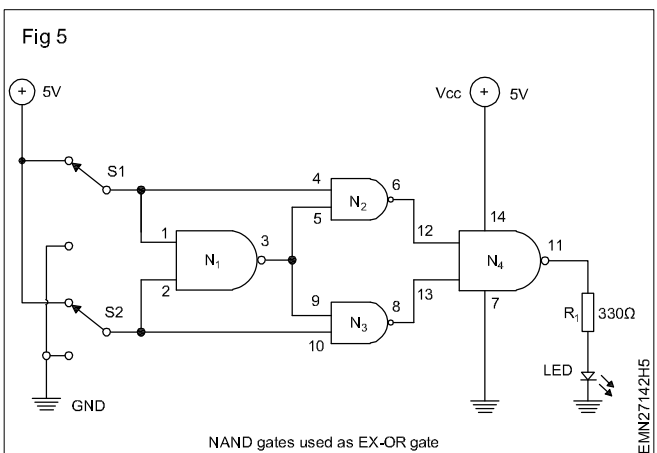TASK 5 : Construction of EX-OR gate circuit using NAND gate and verification of its truth table

- 1 Rearrange the connections and assemble the EX-OR gate circuit using NAND gates as shown in Fig 5 on breadboard.



- 2 Repeat steps 2 to 5 of Task 1, and record the observations in Table 5.
- 3 Verify the readings with the truth table of EX-OR gate.
- 4 Get the work checked by the Instructor.

Note: Use logic probe to check the status of each pin to confirm the functioning of each gate.

EX-OR gate Truth table


Sl.No.	Input		Output $Y = A \oplus B$
	A	B	
1	0	0	0
2	0	1	1
3	1	0	1
4	1	1	0

Table 5

Sl.No.	Input		Output LED
	A	B	
1			
2			
3			
4			

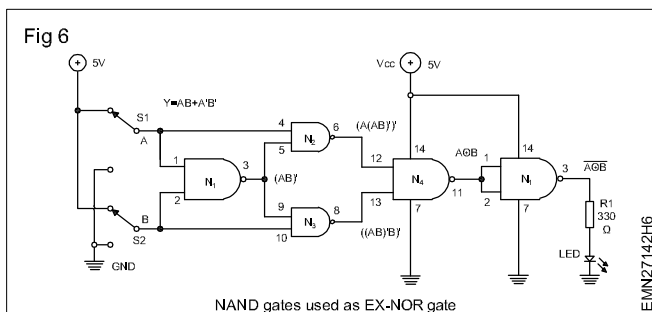TASK 6 : Construction of EX-NOR gate circuit using NAND gate and verification of its truth table

- 1 Rearrange the connections and assemble the EX-NOR gate circuit using NAND gates as shown in Fig 6 on breadboard.



EX-NOR gate Truth table

Sl.No.	Input		Output $Y=A\oplus B$
	A	B	
1	0	0	
2	0	1	
3	1	0	
4	1	1	

Table 6


- 2 Repeat steps 2 to 5 of Task 1, and record the observations in Table 6.
- 3 Verify the readings with the truth table of EX-NOR gate.
- 4 Get the work checked by the Instructor.

Note: Use logic probe to check the status of each pin to confirm the functioning of each gate.

Sl.No.	Input		Output LED
	A	B	
1			
2			
3			
4			

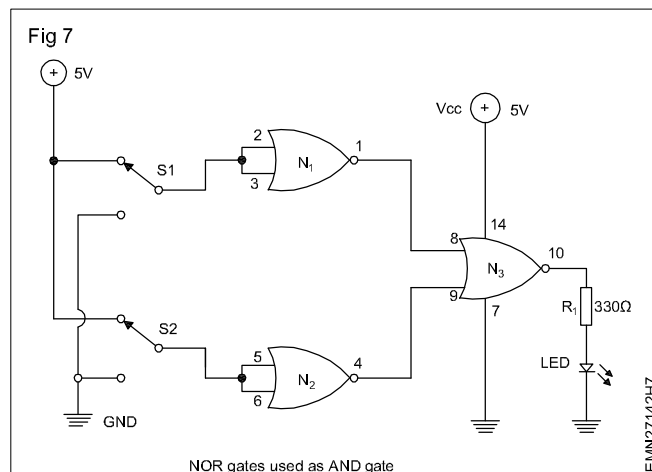TASK 7 : Construction of AND gate using NOR gate IC 7402 and verification of its truth table

- 1 Collect all the components, check them, refer to the data sheet of the IC 7402, assemble the AND gate as shown in Fig 7 on the bread board.



AND gate Truth table

Sl.No.	Input		Output $Y=A.B$
	A	B	
1	0	0	0
2	0	1	0
3	1	0	0
4	1	1	1

Table 7


- 2 Repeat steps 2 to 5 of Task 1, and record the observations in Table 7.
- 3 Verify the readings with the truth table of AND gate.
- 4 Get the work checked by the Instructor.

Note: Use logic probe to check the status of each pin to confirm the functioning of each gate.

Sl.No.	Input		Output LED
	A	B	
1			
2			
3			
4			

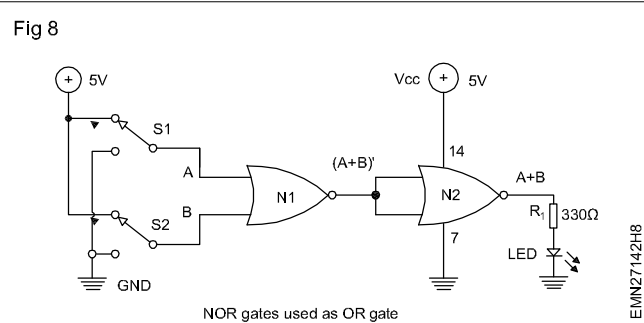TASK 8 : Construction of OR gate using NOR gate IC 7402 and verification of its truth table

- 1 Collect all the components, check them, refer to the data sheet of the IC 7402, assemble the OR gate as shown in Fig 8 on the bread board.



- 2 Repeat steps 2 to 5 of Task 1, and record the observations in Table 8.
- 3 Verify the readings with the truth table of OR gate.
- 4 Get the work checked by the Instructor.

Note: Use logic probe to check the status of each pin to confirm the functioning of each gate.

OR gate Truth table


Sl.No.	Input		Output $Y=A+B$
	A	B	
1	0	0	0
2	0	1	1
3	1	0	1
4	1	1	1

Table 8

Sl.No.	Input		Output LED
	A	B	
1			
2			
3			
4			

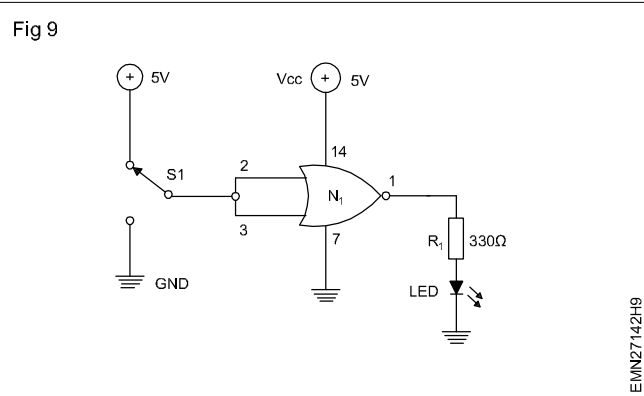TASK 9 : Construction of NOT gate using NOR gate IC 7402 and verification of its truth table

- 1 Collect all the components, check them, refer to the data sheet of the IC 7402, assemble the NOT gate as shown in Fig 9 on the bread board.



- 2 Repeat steps 2 to 5 of Task 9, and record the observations in Table 9.
- 3 Verify the readings with the truth table of NOT gate.
- 4 Get the work checked by the Instructor.

NOT gate Truth table


Sl.No.	Input	Output $Y=\overline{A}$
	A	
1	0	1
2	1	0

Table 9

Sl.No.	Input	Output LED
	A	
1		
2		

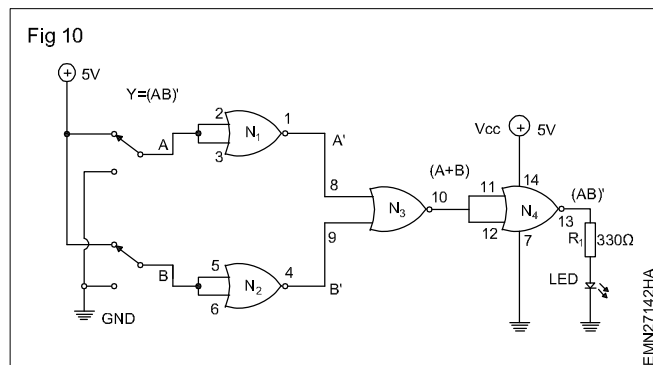TASK 10 : Construction of NAND gate using NOR gate IC 7402 and verification of its truth table

- 1 Collect all the components, check them, refer to the data sheet of the IC 7402, assemble the NAND gate as shown in Fig 10 on the bread board.



- 2 Repeat steps 2 to 5 of Task 9, and record the observations in Table 10.
- 3 Verify the readings with the truth table of NAND gate.
- 4 Get the work checked by the Instructor.

Note: Use logic probe to check the status of each pin to confirm the functioning of each gate.

NAND gate Truth table


Sl.No.	Input		Output $Y = \overline{A \cdot B}$
	A	B	
1	0	0	1
2	0	1	1
3	1	0	1
4	1	1	0

Table 10

Sl.No.	Input		Output LED
	A	B	
1			
2			
3			
4			

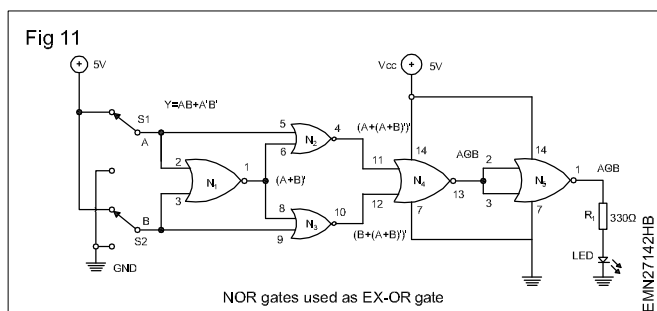TASK 11 : Construction of EX-OR gate using NOR gate IC 7402 and verification of its truth table

- 1 Collect all the components, check them, refer to the data sheet of the IC 7402, assemble the EX-OR gate as shown in Fig 11 on the bread board.



- 2 Repeat steps 2 to 5 of Task 9, and record the observations in Table 11.
- 3 Verify the readings with the truth table of EX-OR gate.
- 4 Get the work checked by the Instructor.

Note: Use logic probe to check the status of each pin to confirm the functioning of each gate.

EX-OR gate Truth table


Sl.No.	Input		Output $Y = A \oplus B$
	A	B	
1	0	0	0
2	0	1	1
3	1	0	1
4	1	1	0

Table 11

Sl.No.	Input		Output LED
	A	B	
1			
2			
3			
4			

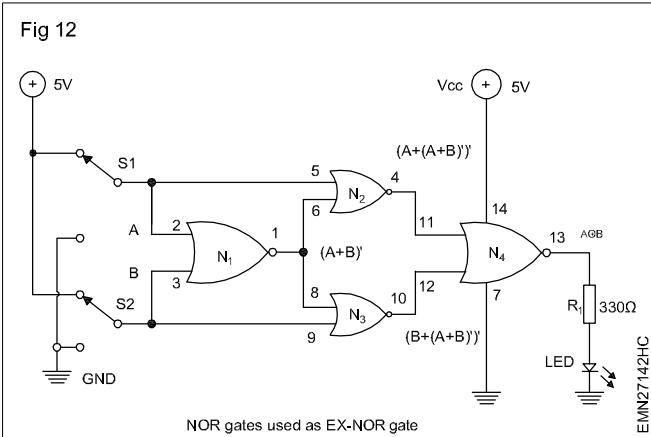TASK 12 : Construction of EX-NOR gate using NOR gate IC 7402 and verification of its truth table

- 1 Collect all the components, check them, refer to the data sheet of the IC 7402, assemble the EX-NOR gate as shown in Fig 12 on the bread board.



- 2 Repeat steps 2 to 5 of Task 9, and record the observations in Table 12.
- 3 Verify the readings with the truth table of EX-NOR gate.
- 4 Get the work checked by the Instructor.

Note: Use logic probe to check the status of each pin to confirm the functioning of each gate.

EX-NOR gate Truth table

Sl.No.	Input		Output $Y=A\oplus B$
	A	B	
1	0	0	1
2	0	1	0
3	1	0	0
4	1	1	1

Table 12

Sl.No.	Input		Output LED
	A	B	
1			
2			
3			
4			

Use digital IC tester to test various digital ICs (TTL and CMOS)

Objectives: At the end of this exercise you shall be able to

- identify the IC manufacturers' names from the logo given on the IC and manufacturers data
- identify IC code number printed on the given digital IC
- identify the type of package of the given digital IC (TTL and CMOS)
- identify the logic family of the given digital IC referring databook
- identify the pin numbers of the given Digital IC referring data book
- test the given IC using digital IC tester.

Requirements

Tools/Equipments/Instruments/Data manual

- Digital IC databook - 1 No
- Digital IC tester with manual - 1 No
- DMM with probes - 1 No

Materials/Components

- Assorted Digital ICs (both TTL and CMOS types) - 10 Nos
- Breadboard - 1 No
- Hook up wires - as reqd

Note: The Instructor has to label all the ICs serially

Keep a minimum of 20 numbers of assorted labeled TTL and CMOS ICs for this exercise. Instruct the trainees to pick one IC at a time and carryout the exercise.

Demonstrate setting the controls and testing ICs using digital IC tester. No detailed procedure for using IC tester is given as different IC testers used in different institutes may have different operating procedures and specification.

PROCEDURE

- 1 Identify operator controls, switches and IC socket on the digital IC tester as shown in Fig 1 with reference to the manual.
- 2 Pick one of the labeled IC from the assorted lot and record its label number.
- 3 Refer to the data manual interpret the manufacturer's logo given on the IC or alphabets used for the IC type identify and record the details in Table 1.
- 4 Identify and record the logic family supply voltage and function of the IC referring the data manual.
- 5 Count and record the number of pins on the IC.
- 6 As demonstrated by the instructor, test and record the condition of the IC using digital IC tester for atleast 10 different ICs both in TTL and CMOS types.
- 7 Get the recorded information checked by the instructor for 10 different ICs.

Note: Follow the procedure demonstrated by the instructor for setting the controls on digital IC tester while testing the IC.

TABLE 1

Sl. No.	Label No. IC	Code No. of IC	No.of pins	Logic family	Function	Package type	Maximum V_{cc} voltage	Condion of IC tested
1								
2								
3								
4								
5								
6								
7								
8								
9								
10								
11								
12								
13								
14								
15								
16								
17								
18								
19								
20								



Construct Half Adder circuit using ICs and verify the truth table

Objectives: At the end of this exercise you shall be able to

- construct the half adder circuit and verify the truth table.

Requirements

Tools/Equipments/Instruments

- Soldering iron 25W/230V - 1 No
- Logic probe - 1 No
- Trainees tool kit - 1 Set
- Regulated DC power supply 0-30V/2A - 1 No
- Digital multimeter with probes - 1 No

Materials/Components

- IC-7486 with base - 1 No
- IC-7400 with base - 1 No
- Data sheet of ICs used - 1 No each
- LED 5mm Red, Green - 2 Nos
- Resistor 330Ω/¼ W/CR25 - 2 Nos
- Miniature toggle switch SPDT - 3 Nos
- Breadboard - 1 No
- Solder, flux - as reqd
- Hook up wires - as reqd


PROCEDURE

TASK 1: Construction of Half Adder circuit and verification of truth table

- 1 Collect all the components, check them and assemble the Half adder circuit as shown in Fig 1 on breadboard.

- 6 Verify readings with truth table of Half Adder.

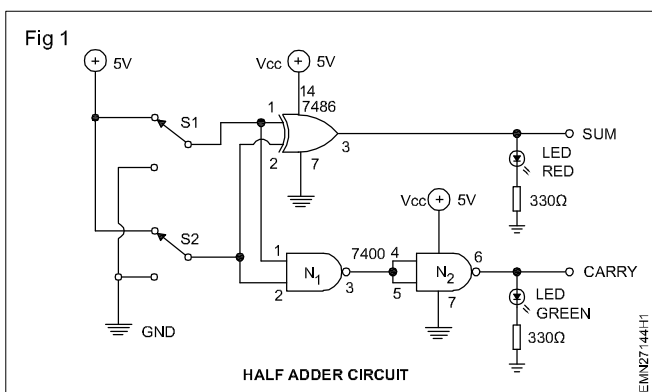Use logic probe to check the status of each pin to confirm the functioning of the gate.



Use 14 pin IC base on the bread board for this task.

- 2 Use toggle switch S_1 as input A and switch S_2 as input B.
- 3 Get the assembled circuit checked by the Instructor.
- 4 Switch ON 5VDC supply and operate switches S_1 & S_2 for different logic levels either in 5V position for zero volt (GND) position as shown in Table 1.
- 5 Observe the LEDs for each step of combinations, record your observations in Table 1.

Truth Table of Half Adder

Sl. No.	Input		Output	
	A	B	Sum	Carry
1	0	0	0	0
2	0	1	1	0
3	1	0	1	0
4	1	1	0	1

Table 1

Sl. No.	Input		Output LED	
	A	B	Red (Sum)	Green (carry)
1				
2				
3				
4				

- 7 Get the work checked by the instructor.

Construct Full adder with two Half adder circuit using ICs and verify the truth table

Objectives: At the end of this exercise you shall be able to

- construct and test full adder using half adder circuits.

Requirements

Tools/Equipments/Instruments

- Soldering iron 25W/230V - 1 No
- Logic probe - 1 No
- Trainees tool kit - 1 Set
- Regulated DC power supply 0-30V/2A - 1 No
- Digital multimeter with probes - 1 No


Materials/Components

- IC-7486 with base - 1 No
- IC-7400 with base - 1 No
- Data sheet of ICs used - as reqd
- LED 5mm Red, Green - 1 No each
- Resistor 330Ω/¼ W/CR25 - 2 Nos
- Miniature toggle switch SPDT - 3 Nos
- Breadboard - 1 No
- Solder, flux - as reqd
- Hook up wires - as reqd

PROCEDURE

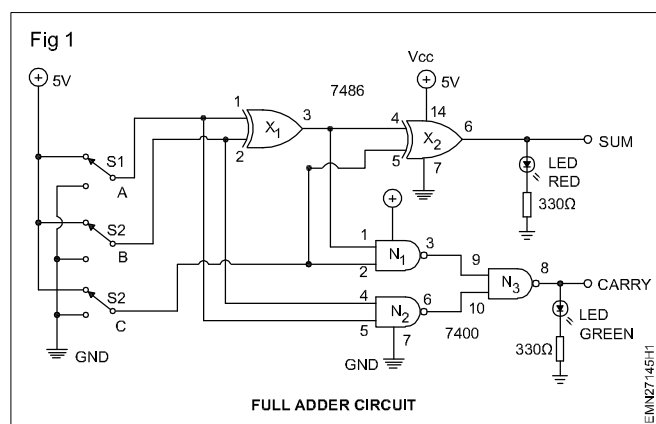TASK 1 : Construction of Full Adder using two Half Adder circuits and verification of truth table

- 1 Collect all the components, check them and assemble the Full adder circuit as shown in Fig 1 on breadboard.



- 2 Use toggle switch S_1 as input A and switch S_2 as input B and switch S_3 as input C.
- 3 Get the assembled circuit checked by the Instructor.
- 4 Switch ON 5VDC supply and operate all the switches for different logic levels either in 5V position for zero volt (GND) position as shown in Table 1.
- 5 Observe the LEDs for each step of combinations, record the observations in Table 1.
- 6 Verify readings with truth table of Half Adder.

Note: Use logic probe to check the status of each pin to confirm the functioning of the gate.

Truth table of Full Adder

Sl. No.	Input			Output	
	A	B	C	Sum	Carry
1	0	0	0		
2	0	0	1		
3	0	1	0		
4	0	1	1		
5	1	0	0		
6	1	0	1		
7	1	1	0		
8	1	1	1		

Table 1

Sl. No.	Input			Output	
	A	B	C	Sum	Carry
1					
2					
3					
4					
5					
6					
7					
8					

- 7 Get the work checked by the instructor.

Construct the adder cum subtractor circuit and verify the result

Objectives: At the end of this exercise you shall be able to

- construct a 4 bit binary adder circuit using IC 7483, IC7486 and verify the result
- construct a 4 bit binary subtractor circuit using IC7483, IC7486 and verify the result.

Requirements

Tools/Equipments/Instruments

- Soldering iron 25W/230V - 1 No
- Trainees tool kit - 1 Set
- Regulated DC power supply 0-30V/2A - 1 No
- Digital multimeter with probes - 1 No
- Logic probe - 1 No
- Data sheet of ICs used - as reqd

Materials/Components

- Miniature toggle switch SPDT - 3 Nos


- IC-7486 with base (14 pin) - 1 No
- IC-7483 with base (16 pin) - 1 No
- Breadboard - 1 No
- Solder, flux - as reqd
- Connecting wires - as reqd
- Resistor 330Ω ¼ W/CR25 - 2 Nos
- Hook up wires - as reqd
- LED 5mm, Red - 4 Nos
- LED 5mm, Green - 1 No
- Resistor 330Ω/¼ W/CR25 - 5 Nos

PROCEDURE

TASK 1: Construction and testing of 4 bit binary adder circuit

- 1 Collect all the components required, test them refer to the data sheet of ICs, assemble the 4 bit binary adder circuit as shown in Fig 1 on bread board.
- 2 Use toggle switch S_1 as data input A_0 , switch S_2 as data input A_1 , and switch S_3 as data input A_2 , and switch S_4 as data input A_3 as shown in Fig 1.
- 3 Use toggle switch S_5 as data input B_0 , switch S_6 as data input B_1 , and switch S_7 as data input B_2 , and switch S_8 as data input B_3 and switch S_9 as mode select switch as shown in Fig 1.
- 4 Get the assembled circuit checked by the Instructor.

Fig 1

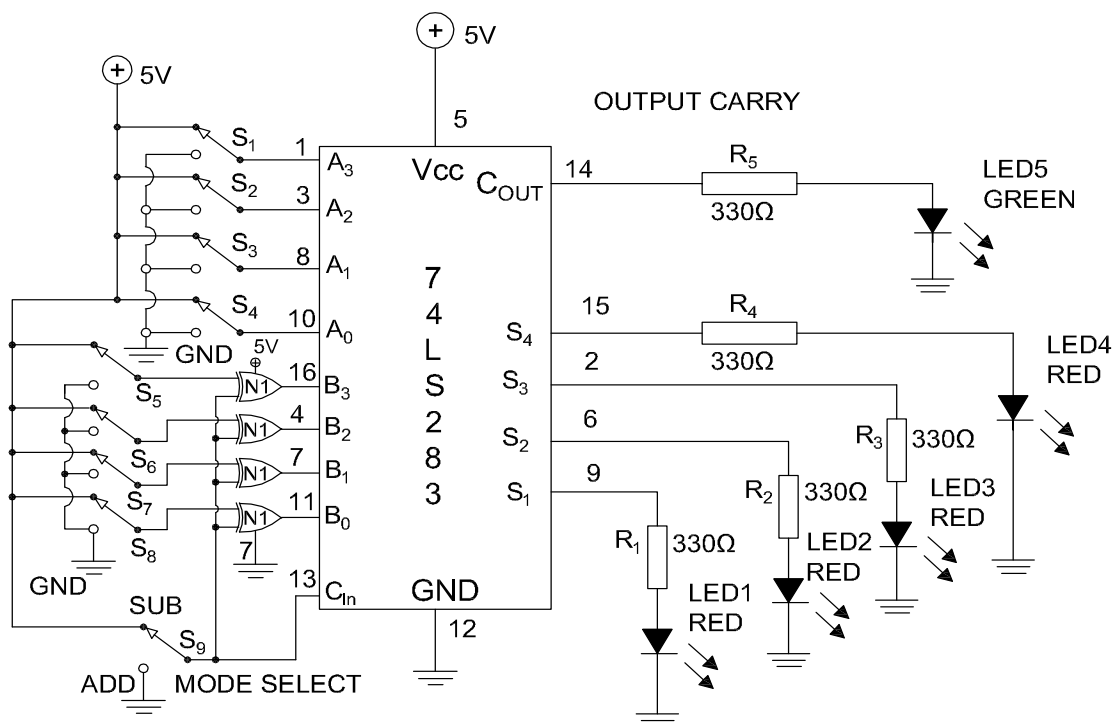

4 BIT BINARY ADDER CUM SUBTRACTOR CIRCUIT

- 5 Switch ON 5VDC supply and operate switches S_1 to S_8 for different logic levels either in 5V position or zero volt (GND) position keeping the switch S_9 at END position to operate the circuit as 4 bit binary adder as shown in Table 1.

- 6 Observe the status of all the five LEDs for each step of combinations record them in Table 1.

Table 1

Sl.No	Inputs				Inputs					Mode switch=OV					Mode switch=5V				
										Status of LEDs					Status of LED				
	A_3	A_2	A_1	A_0	B_3	B_2	B_1	B_0	Carry _{out}	Q_3	Q_2	Q_1	Q_0	C_{out}	Q_3	Q_2	Q_1	Q_0	Carry _{out}
1																			
2																			
3																			
4																			
5																			
6																			
7																			
8																			
9																			
10																			
11																			
12																			
13																			
14																			
15																			
16																			

- 7 Get the work checked by the Instructor.

TASK 2: Construction and testing of 4 bit binary subtractor circuit

Use the assembled circuit for 4 bit binary subtractor function/operation with following steps.

- 1 Set/toggle the mode select switch S_9 to 5VDC position (Logic '1')
- 2 Switch ON 5VDC supply and operate switches S_1 to S_8 for different logic levels either in 5V position or zero volt (GND) position as shown in Table 1.

- 3 Observe the status of all the five LEDs for each step of combinations and record them in Table 1.

- 4 Get the work checked by the Instructor.

Construct and test a 2 to 4 Decoder

Objectives : At the end of this exercise you shall be able to

- construct a 2 to 4 decoder using AND, NOT gates and verify the truth table.

Requirements

Tools/Equipments/Instruments

- Logic probe - 1 No
- Trainees tool kit - 1 Set
- Regulated DC power supply 0-30V/2A - 1 No
- Soldering iron 25W/230V - 1 No
- Digital multimeter with probes - 1 No
- Data sheet of ICs used - as reqd

Materials/Components

- Rosin cored solder - as reqd
- Miniature toggles - 2 Nos
- 14 pin IC Base Switch SPDT - 2 Nos
- Breadboard - 1 No
- IC-7404 - 1 No
- IC-7408 - 1 No
- LED 5mm, Red - 4 Nos
- Resistor 330Ω/¼ W/CR25 - 4 Nos

Note:


1 The Instructor has to guide the trainees to record 5VDC given to gate input as Logic High (1) and GND as Logic Low (0).

2 The status of LED ON as Logic '1' and 'OFF' as Logic '0'.

PROCEDURE

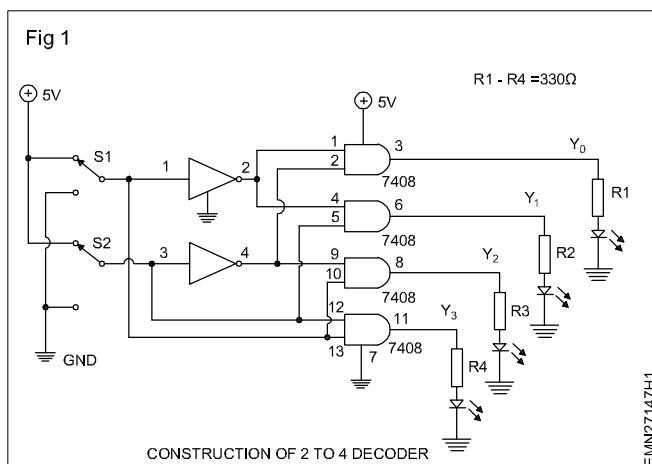TASK 1 : Construction of 2 to 4 decoder circuit and verification of truth table

- 1 Collect all the components, check them, refer to the data sheet of the ICs assemble the 2 to 4 decoder circuit as shown in Fig 1 on breadboard.



- 2 Use toggle switch S_1 as input A and switch S_2 as input B.
- 3 Get the assembled circuit checked by the Instructor.
- 4 Switch ON 5VDC supply and operate switches S_1 & S_2 for different logic levels either in 5V position or zero volt (GND) position as shown in Table - 1.
- 5 Observe the status of LEDs for each step of combinations and record the observations in Table - 1.

Table 1

Sl. No	INPUT		OUTPUT LED Status			
	A	B	Y0	Y1	Y2	Y3
1	0	0				
2	0	1				
3	1	0				
4	1	1				

2 to 4 Decoder TRUTH TABLE:

Sl. No	INPUT		OUTPUT LED Status			
	A	B	Y0	Y1	Y2	Y3
1	0	0	1	0	0	0
2	0	1	0	1	0	1
3	1	0	0	0	1	0
4	1	1	0	0	0	1

- 6 Verify the readings on the Table with the Truth table of 2 to 4 Decoder Truth table given.
- 7 Get the work checked by the Instructor.

Construct and test a 4 to 2 Encoder

Objectives : At the end of this exercise you shall be able to

- construct and test 4 to 2 Encoder.

Requirements

Tools/Equipments/Instruments

- Soldering iron 25W/230V - 1 No
- Trainees tool kit - 1 Set
- DC power supply 0-30V/2A - 1 No
- Digital multimeter with probes - 1 No
- Data sheet of ICs used - as reqd

Materials/Components

- Miniature toggles Switch SPDT - 4 Nos
- Breadboard - 1 No
- IC-7432 - 1 No
- LED 5mm, Red, Green - 1 No each
- Hook up wires - as reqd
- Rosin cored solder - as reqd
- Resistor 330Ω/¼ W/CR25 - 2 Nos

PROCEDURE

TASK 1: Construction of 4 to 2 Encoder circuit and verification of its truth table

- 1 Collect all the components, check them and assemble the 4 to 2 Encoder circuit as shown in Fig 1 on bread board.

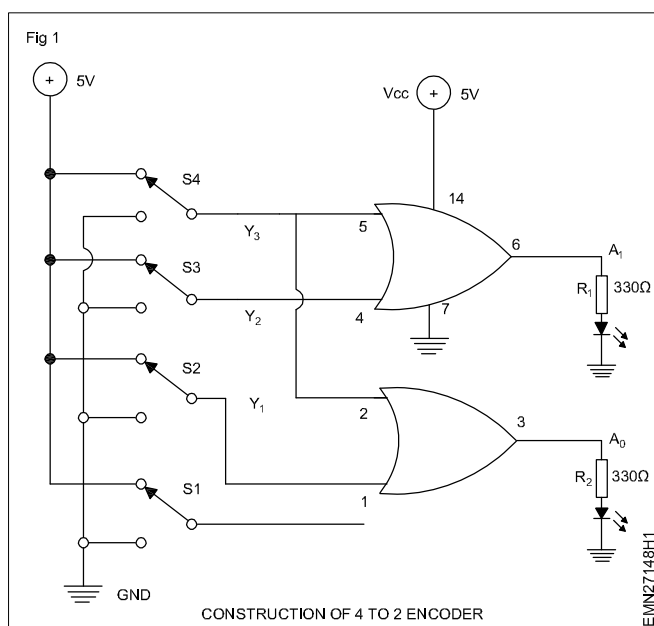


Table 1

SI. No	INPUT				OUTPUT	
	Y3	Y2	Y1	Y0	A1	A0
1	0	0	0	1		
2	0	0	1	0		
3	0	1	0	0		
4	1	0	0	0		

2 to 4 Decoder TRUTH TABLE:

SI. No	INPUT				OUTPUT	
	Y3	Y2	Y1	Y0	A1	A0
1	0	0	0	1	0	0
2	0	0	1	0	0	1
3	0	1	0	0	1	0
4	1	0	0	0	1	1

- 2 Use toggle switch S_1 as input Y_0 , switch S_2 as input Y_1 , switch S_3 as input Y_2 and switch S_4 as input Y_3 .

In the 4 to 2 Encoder using OR gates note that the switch S_1 is kept unconnected to the input, as neither of the outputs depend on it.

- 3 Get the assembled circuit checked by the Instructor.
- 4 Switch ON 5VDC supply, and operate switches S_2 , S_3 and S_4 only for different logic levels either in 5V position or zero volt (GND) position as shown in Table - 1.

- 5 Observe the status of LEDs for each step of combinations and record your observations in Table - 1.

- 6 Verify the readings on the Table with the Truth table of 4 to 2 Encoder given.

- 7 Get the work checked by the Instructor.

Construct and test a 4 to 1 Multiplexer

Objectives : At the end of this exercise you shall be able to

- construct and test 4 to 1 multiplexer circuit using IC74LS151.

Requirements

Tools/Equipments/Instruments

- Soldering iron 25W/230V - 1 No
- Trainees tool kit - 1 Set
- Regulated DC power supply 0-30V/2A - 1 No
- Digital multimeter with probes - 1 No

Materials/Components

- Rosin cored solder - as reqd
- IC-74LS151 - 1 No

- IC 7432 IC base - 1 No
- Digital IC trainer kit with instruction manual - 1 No
- Resistor 330Ω/¼ W/CR25 - 2 Nos
- Breadboard - 1 No
- LED 5mm, Red - 1 No
- Hook up wires - as reqd
- Miniature SPDT toggle switch - 6 Nos
- Data sheet of IC 74LS151 - 1 No

Safety Precaution: Ensure that the IC pins are not bent while inserting into the bread board IC Base.


PROCEDURE

Note: If the digital IC trainer kit is not available in the lab, follow the steps given for this exercise .

TASK 1 : Construction and testing of 4 to 1 multiplexer circuit using IC 74LS151

- 1 Collect the components required, check them and assemble the multimeter circuit as shown in Fig 1 on breadboard.

Use the 16 pin IC base for IC74LS151.

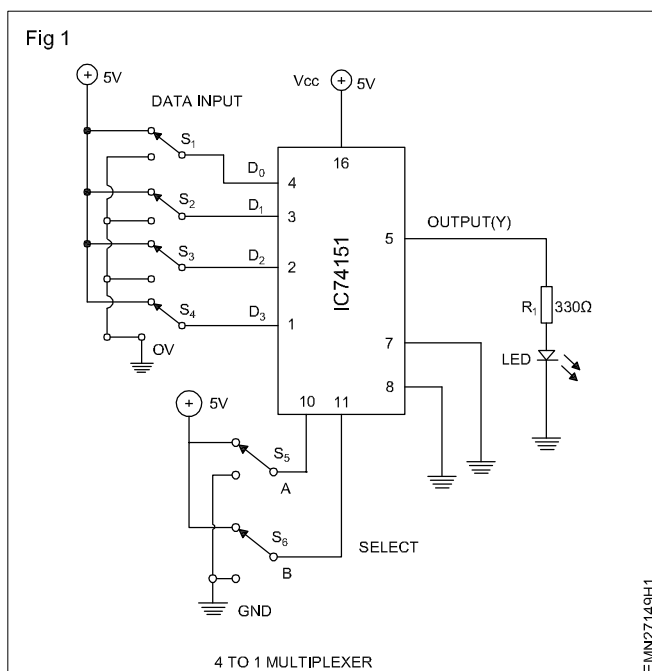

- 2 Use toggle switches either in 5V position or in Zero Volt position for different logic levels as shown in Table-1.
- 3 Get the assembled multiplexer circuit checked by the Instructor.
- 4 Switch ON the 5VDC supply to the circuit and operate switches S1 to S4 for Data inputs and S5 & S6 for selection Sequence.
- 5 Observe the LED for each setting and record it in Table 1.

Note: When data input is not available, multiplexer does not produce output for the select condition.

- 6 Verify the output by keeping data input switches S1 to S4 in 5VDC position and select S5 & S6 randomly.
- 7 Observe the LED and change Data input switches one at a time for the LED to go OFF.

It confirms that input is selected and goes to the output.

- 8 Repeat steps 6 & 7 with different combinations of S5 & S6 and confirm the Data selected.

Table 1

Sl. No.	DATA INPUTS (LOGIC LEVELS)				SELECT SEQUENCE		LED OUTPUT (Y)
	D3	D2	D1	D0	B	A	
1	0	0	0	1	0	0	D0-LED ON
2	0	0	1	0	0	1	D1-LED ON
3	0	1	0	0	1	0	D2-LED ON
4	1	0	0	0	1	1	D3-LED ON
5	1	1	1	1			

9 Get the work checked by the Instructor.

Construct and test a 1 to 4 Demultiplexer

Objectives : At the end of this exercise you shall be able to

- construct and test a 1 to 4 demultiplexer circuit using IC 74LS138.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
• Trainees tool kit	- 1 Set	• IC-74LS138 with data sheet	- 1 No
• Regulated DC power supply 0-30V/2A	- 1 No	• 16 pin IC Base	- 1 No
• Digital multimeter with probes	- 1 No	• LED 5mm, Red, Green	- 4 Nos
• Soldering iron 25W/230V	- 1 No	• Resistors 330Ω/¼W/CR25	- 4 Nos
• Digital IC trainer kit with instruction manual	- 1 Set	• Hook up wires	- as reqd
		• Breadboard	- 1 No
		• Rosin cored solder	- as reqd

Note: If the digital IC trainer kit is not available in the lab, follow the steps given for this exercise.

PROCEDURE

TASK 1 : Construction and testing of 1 to 4 Demultiplexer circuit using IC74LS138

- 1 Collect all the components check them and assemble the demultiplexer as shown in Fig 1 on breadboard.

Use the 16 pin base for IC74LS138.

- 2 Connect the toggle switch at input as shown in the circuit

- 3 Get the assembled circuit checked by the Instructor.
- 4 Switch ON the 5VDC supply to the circuit, Keep S1 at +5VDC for the data input high. Change the settings of switches S2 and S3 for different combination of Data select sequence as shown in Table -1.
- 5 Observe the LEDs for each setting and record the status in Table -1

Note: When data input is not available, Demultiplexer does not produce output for that condition in any of the Data output pins.

- 6 Verify the output by keeping the Data input switch S1 to ground, Select Switch S2 & S3 randomly.
- 7 Observe the LED, Change switches S2 & S3 to other three combinations, for whether any of the LEDs to glow.
- 8 Repeat steps 6 and 7 by keeping the switch S1 at +5VDC and confirm the LEDs are glowing independently as per the selection sequence in Table -1

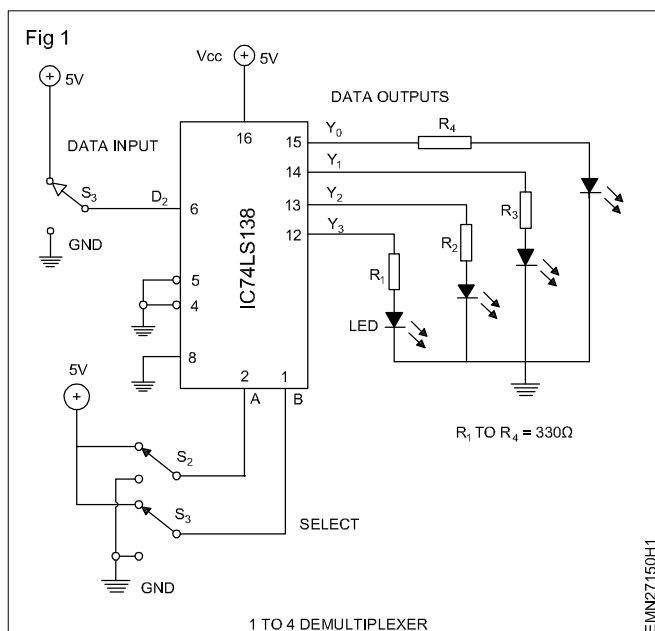


Table 1

Sl. No.	Selection Sequence		Output channels(Pin Nos.) LED ON =1 LED OFF = 0								Remarks
	A	B	Y0 pin 15	Y1 pin 14	Y2 pin 13	Y3 pin 12	Y0 LED	Y1 LED	Y2 LED	Y3 LED	
1											
2											
3											
4											
5											

9 Get the work checked by the Instructor.

Identify different Flip-Flop ICs by the number printed on them

Objectives : At the end of this exercise you shall be able to

- identify different Flip Flop by the number printed on the ICs.

Requirements		
Tools/Equipments/Instruments	Materials/Components	
<ul style="list-style-type: none"> • Trainees tool kit <p>Aids: Data sheet of ICs used for this exercise</p>	<ul style="list-style-type: none"> • 74 LS 73 • 74 LS 74 • 74 LS 76 • 74 LS 107 • 74 LS 109 	- 1 No each

Note: Instructor has to label the different types of logic gates ICs.

PROCEDURE

- 1 Collect the labelled flipflop ICs from the Instructor
- 2 Pick one of the IC from the lot, and identify the code number printed on the IC and noted in Table -1
- 3 Refer to the data sheet of the IC, draw the pinout diagram and mark the details in Table 1.
- 4 Repeat the steps 2 and 3 for remaining labelled logic gates.

Note:

- 1 The Instructor has to provide/ensure the Flipflop ICs with their number printed on them is clearly visible.
- 2 Insert all the ICs on the breadboard.

Safety Precaution: Do not touch the pins of ICs with fingers.

Table 1

Sl.No.	IC Number	Logic gates function	Symbol	Pinout diagram
1		74LS73		
2		74LS74		
3		74LS76		
4		74LS107		
5		74LS109		

- 5 Get the work checked by the Instructor.

Construct and test four bit latch using 7475

Objectives : At the end of this exercise you shall be able to

- Construct and test four bit latch using IC 7475

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Regulated DC power supply 0-30V/2A - 1 No
- Digital multimeter with probes - 1 No
- Data sheet of IC7475 - 1 No


Materials/Components

- Breadboard - 1 No
- IC-7475 (D-Latch) with base - 1 No
- LED 5mm, Red - 4 Nos
- Resistors 330Ω/¼ W/CR25 - 4 Nos
- Miniature toggle Switch SPDT - 5 Nos
- Hook up wires - as reqd

PROCEDURE

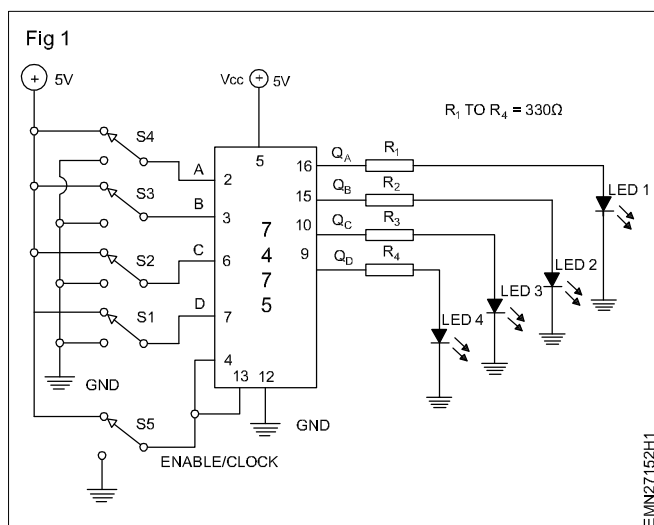TASK 1 : Construction and testing of fourbit batch circuit using IC7475

- 1 Collect all the components, check them refer to the data sheet of the IC, assemble the 4 bit latch circuit as shown in Fig 1 on breadboard.



Use the 16 pin IC base on the breadboard for this exercise.

- 2 Use toggle switch S_1 as data input A, switch S_2 as data input B, switch S_3 as data input C, switch S_4 as data input D and switch S_5 as Enable/clock input.
- 3 Get the assembled circuit checked by the Instructor.
- 4 Switch ON 5VDC supply and operate switches S_1 to S_5 for different logic levels either in 5V position or zero volt (GND) position as shown in Table - 1.
- 5 Observe the LEDs for each step of combinations, record them in Table 1.

Table 1

Sl.No	Inputs				Enable/clock =1				Enable/clock =0			
					Output LEDs				Output LEDs			
	A	B	C	D	Q _A	Q _B	Q _C	Q _D	Q _A	Q _B	Q _C	Q _D
1	0	0	0	0								
2	0	0	0	1								
3	0	0	1	0								
4	0	0	1	1								
5	0	1	0	0								
6	0	1	0	1								
7	0	1	1	0								
8	0	1	1	1								
9	1	0	0	0								
10	1	0	0	1								
11	1	0	1	0								
12	1	0	1	1								
13	1	1	0	0								
14	1	1	0	1								
15	1	1	1	0								
16	1	1	1	1								

6 Get the work checked by the Instructor.

Construct and test R-S Flip-flop using IC 7400 with clock and without clock pulse

Objectives: At the end of this exercise you shall be able to

- construct and test R-S flip-flop using IC 7400 without clock pulse
- construct and test RD flip-flop with clock pulse.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- DC power supply 0-30VDC/2A - 1 No
- Digital multimeter with probes - 1 No


Materials/Components

- Breadboard - 1 No
- IC-7400 NAND gate with data sheet - 1 No
- Miniature toggles switch - 2 Nos
- Hook up wires - as reqd
- LED 5mm, Red, Green - 1 No each
- Resistor 330Ω/¼ W/CR25 - 2 Nos

PROCEDURE

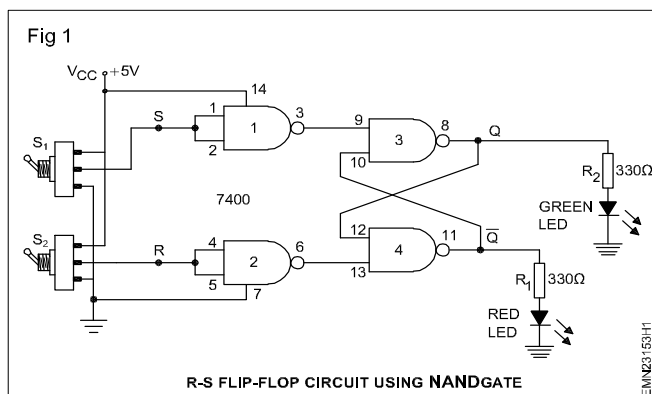TASK 1: Construction and testing of R-S Flip-Flop without clock pulse using IC 7400

- 1 Collect all the components required, check them and assemble the RS flipflop circuit on the breadboard as shown in Fig 1



- 2 Get the assembled RS flipflop circuit checked by the Instructor.
- 3 Switch ON 5VDC supply to the circuit, use switches S_1 and S_2 for setting input logic levels as shown in Fig 1.
- 4 Operate the switches to apply different logic levels and observe corresponding output.
- 5 Record the status of LEDs for each step of logic levels.


Table 1
RS flip-flop using NAND gate

Input		Output				Operating Mode
S	R	Q	Q - LED Status (ON/OFF)	Q	Q - LED Status (ON/OFF)	
0	1					Set
1	1					No Change
1	0					Reset
1	1					No Change
0	0					Forbidden

- 6 Get the work checked by the Instructor.

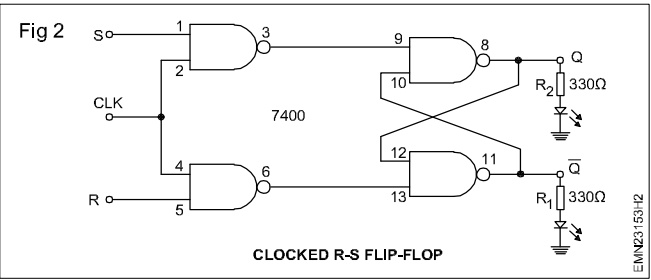TASK 2 : Construction and testing of RS flipflop with clock pulse using IC 7400

1 Modify the RS flipflop circuit into clocked RS flipflop circuit as shown in Fig 2.



- 2 Connect switches S1 and S2 at R and S inputs respectively.
- 3 Switch ON 5VDC supply to the circuit, operate switches S1,S2 apply differnt logic levels to the input keeping clock input at ground/negative.
- 4 Observe the status of LEDs for the above four steps and record in Table 2.
- 5 Connect the clock input to +5VDC and repeat steps 3 and 4 and record the obsevation for next four steps.

Table 2

Clock Input	Input		Output			
	S	R	Q	Q-LED Status (ON/OFF)	Q	Q-LED Status (ON/OFF)
0	0	1				
0	1	0				
0	1	1				
0	0	0				
1	0	1				
1	0	0				
1	1	0				
1	0	0				
1	1	1				

6 Get the work checked by the Instructor.

Verify the truth tables of Flipflop ICs (RS, D, T, JK, MSJK) by connecting switches and LEDs

Objectives: At the end of this exercise you shall be able to

- construct and verify the truth table of RS flip flop by connecting switches and LEDs
- construct and verify the truth table of D flip flop by connecting switches and LEDs
- construct and verify the truth table of T.flip flop by connecting switches and LEDs
- construct and verify the truth table of JK flop by connecting switches and LEDs
- construct and verify the truth table of JK flip flop by connecting switches and LEDs.

Requirements		
Tools/Equipments/Instruments		
• Trainees tool kit	- 1 Set	
• DC power supply - 0-30V/2A	- 2 Nos	
• DMM with probes	- 1 No	
Materials/Components		
• Breadboard	- 1 No	
• IC 74 HC00 (Quad Nand Gate)	- 2 Nos	
• IC 74LS10 (3 Input NAND)	- 1 No	
		• IC MC74HC 73 (Dual/JKFlip-Flop) - 1 No
		• IC 74LS76 (JK-FF) - 1 No
		• Resistors 330Ω/¼ W/CR25 - 4 Nos each
		• LED (Red,Green) - 1 No each
		• Toggle switch - 4 Nos
		• Connecting wire - as reqd
		• Battery (9V) - as reqd
		Aids: • Semiconductor digital IC-Data manual
		• charts

PROCEDURE

TASK 1: Construction of RS flipflop circuit and verification of the truth table.

- Collect the materials, check them and assemble RS flipflop circuit on a breadboard as shown in Fig 1a.
- Get the circuit checked by the Instructor.
 - Apply different Inputs to S and R as given in truth table 1 and record the corresponding output levels and the status of the LED.
 - Thus for different inputs at S and R the corresponding output can be seen through LED Q and Q̄.

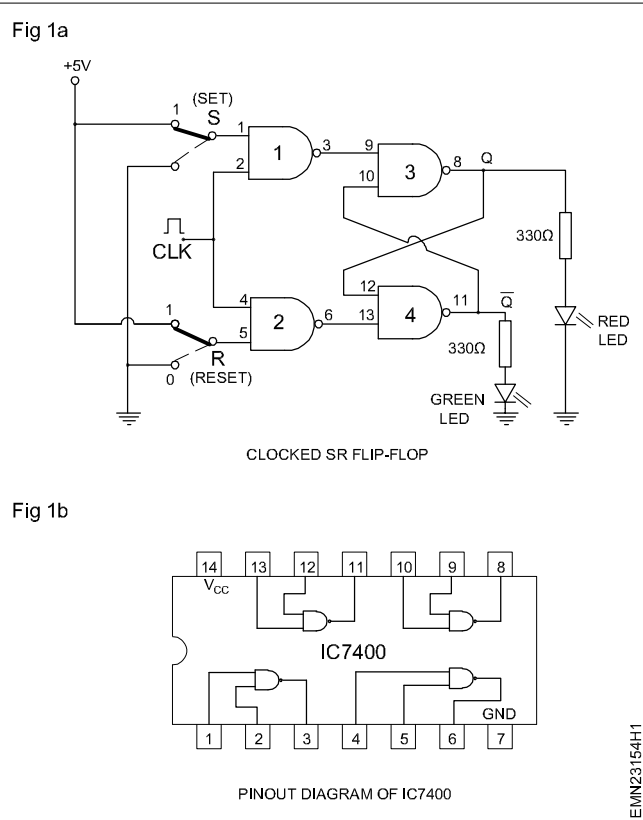


Table 1
Truth table of clocked SR Flip-flop

CLK	INPUT		OUTPUT		State of Flip flop
	S	R	Q	Q̄	
Clock					
LOW	x	x	0	1	Previous state
HIGH	0	0	0	1	No state
HIGH	0	1	0	1	Reset
HIGH	1	0	1	0	High
HIGH	1	1	x	x	In terminate

- Get the work checked by the Instructor.

TASK 2 : Construction of D flipflop circuit and verification of the truth table

- Assemble a D flipflop circuit by referring to Fig 2 on a bread board
- Get the circuit checked by the instructor.
- Apply different input to D Flip Flop as given in the truth table and verify the corresponding output level and the status of LEDs at Q and Q' of the FF.

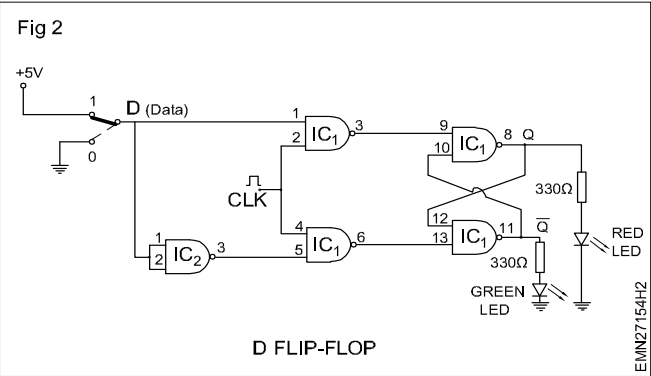


Table 2
Truth table of D Flip-Flop - clocked

Clock	INPUT		OUTPUT
	D	Q	\overline{Q}
LOW	x	0	1
HIGH	0	0	1
HIGH	1	1	0

- Get the work checked by the Instructor.

TASK 3: Construction of T.flip flop circuit and verification of the truth table

- Assemble a T.flipflop on a breadboard as shown in Fig 3a.
- Get the circuit checked by the Instructor
- Apply different inputs to toggle FF as given in the truth table at table and verify the corresponding output level and the status of LED
- Thus for different inputs at T.flip flop corresponding outputs can be seen through LEDs Q and Q'.

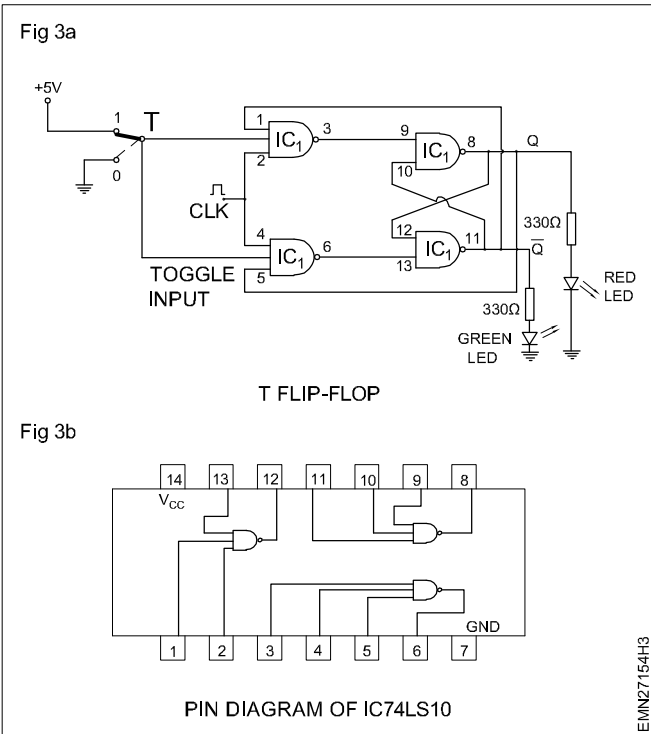



Table 3

Clock	INPUT	OUTPUT		Status of output
		Q	\overline{Q}	
High/Low	T	Q	\overline{Q}	
Low	x	0	1	Previos
High	0	0	1	No change
High	1	1	0	Output-toggles

- Get the work checked by the Instructor.

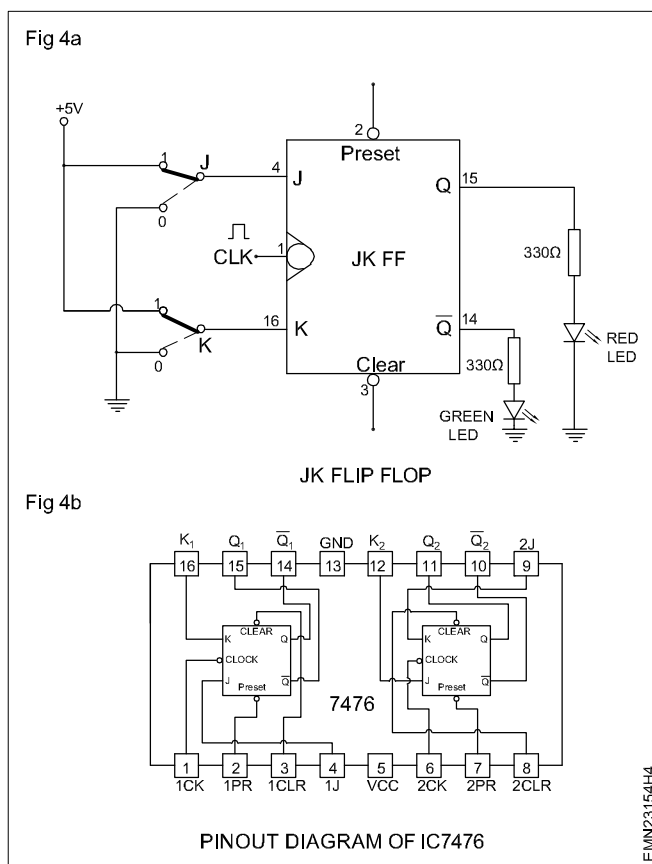TASK 4 : Construction of JK flip-flop circuit and verification of the truth table

- Assemble a Jk flip-flop circuit by referring to Fig 4 on a bread board



- Get the circuit checked by the Instructor.
- Apply different inputs J and K, as given in the truth table 4 and verify the corresponding output levels and the status of LEDs.
- Thus for different inputs of JK flip-flop corresponding outputs can be seen through LEDs Q and Q'.

Table 4
Truth table of JK Flip Flop

Clock Input H/L	INPUTS				OUTPUTS	
	Preset	Clear	J	K	Q	\overline{Q}
X	0	0	X	X	1	1
X	0	1	X	X	1	0
X	1	0	X	X	0	1
L	1	1	0	0	0	Q
L	1	1	1	0	1	0
L	1	1	0	1	0	1
L	1	1	1	1	Toggles	Toggles
L	1	1	X	X	Q	\overline{Q}

- Get the work checked by the Instructor.

TASK 5 : Construction of a master -slave JK flip-flop circuit and verification of the truthtable

- Assemble a MSJK flip-flop circuit by referring to Fig 5 on a breadboard
- Get the circuit checked by the Instructor
- Apply different Inputs J and K, MSJK as given in the truth table 5 and verify the corresponding output levels and status of LEDs.
- Thus for different Inputs of MSJK flip-flop corresponding outputs can be seen through LEDs Q and Q'

Note: MS JK FF.

It may be noted that in the Fig 5. the output of the master J-K FF is led to the input of slave FF. the outputs of slave - FF is used as leedback inputs to master J-k FF. The clk pulse is inverted and applied to slave FF. So the inputs are received by the slave FF only during trailing edge of clock pulse [logic-level-0]. Hence the Master - slave Jk Flip-Flop is a "Synchronons' device as it a passes data with the timing of the clock signal.

When Master receives Input during positive clock signal, slave FF outputs are said to be in latched condition (means no change).

In the truth table, M_1 and M_2 are outputs of Master FF and Q & Q' are the outputs of slave FF.

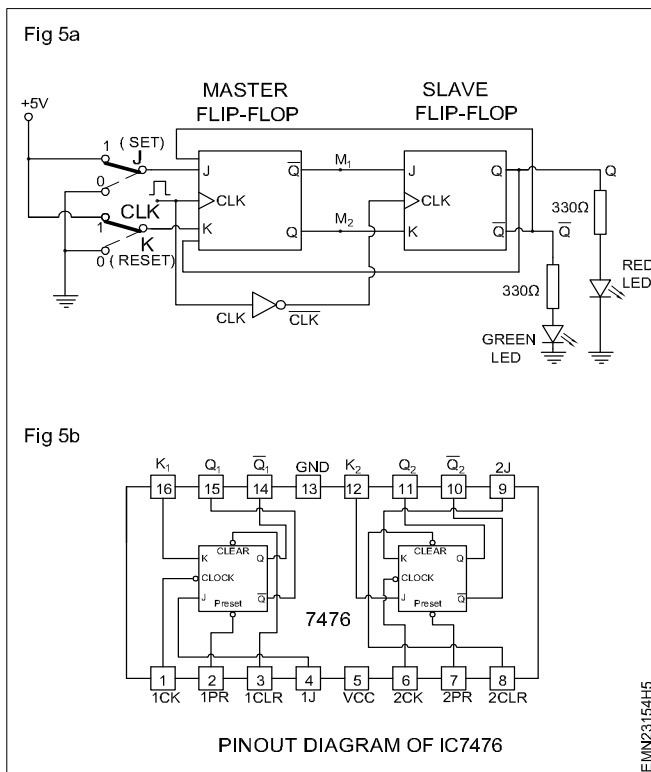


Table 5
Truth table of master slave JK Flip Flop

Trigger	Inputs		Output						Inference
			Present state		Intermediate		Next state		
CLK	J	K	Q	Q	M1	M2	Q	Q̄	
↑	0	0	0	1	0	1	Latched		No Change
↓			0	1	Latched		0	1	
↑			1	0	1	0	Latched		
↓			1	0	Latched		1	0	
↑	0	1	0	1	0	1	Latched		Reset
↓			0	1	Latched		0	1	
↑			1	0	0	1	Latched		
↓			1	0	Latched		0	1	
↑	1	0	0	1	1	0	Latched		Set
↓			0	1	Latched		1	0	
↑			1	0	1	0	Latched		
↓			1	0	Latched		1	0	
↑	1	1	0	1	1	0	Latched		Toggles
↓			0	1	Latched		1	0	
↑			1	0	0	1	Latched		
↓			1	0	Latched		0	1	

- Get the work checked by the Instructor.

Prepare simple digital and electronic circuits using the software

Objectives: At the end of this exercise you shall be able to

- construct EX-OR gate using IC7404, 7408 and 7432 by the simulation software
- construct a positive shunt clipper circuit using discrete components by simulation software.

Requirements

Tools/Equipments/Instruments


- Personal computer installed with simulation software like TINA/Multisim or similar software - 1 No
- Printer - 1 No

Note: This exercise has been developed using the multisim simulation software. The instructor has to follow/guide the trainees as per the steps/sequence with reference to the software available in the Lab/ computer.


PROCEDURE

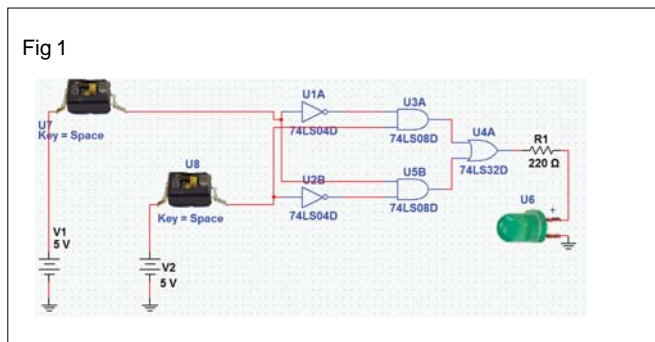TASK 1 : Construction of EX-OR gate using simulation software


- 1 Select the circuit diagram to construct using simulation software. (For example the XOR gate is selected for this exercise) as shown in Fig 1.



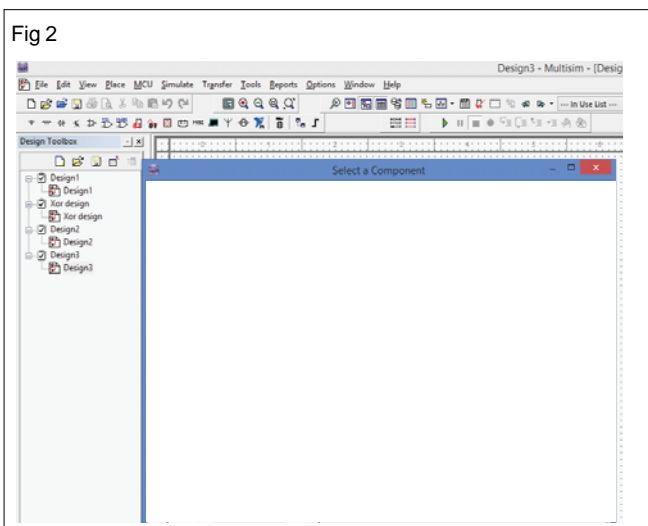- 2 Switch ON computer, open the simulation software through the windows start menu or click on the simulator icon on your desktop and get the first screen as shown in Fig 2.




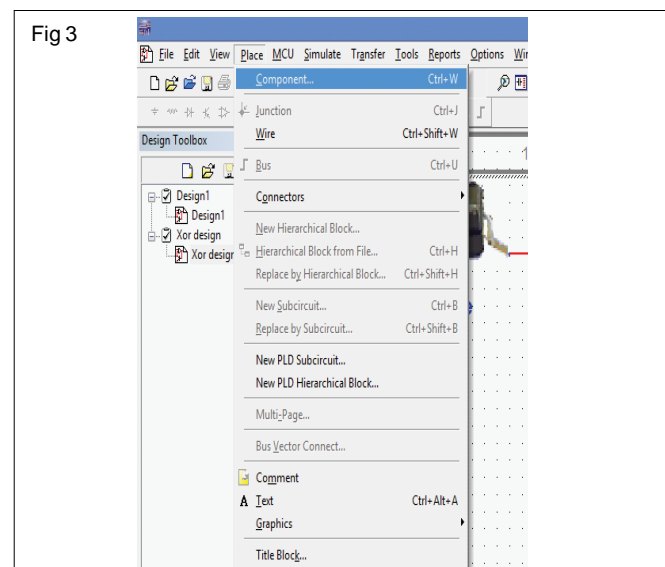- 3 Click on **Place** menu and pull down the options as shown in Fig 3.



- 4 Click on component group, select **TTL** and scroll to **74LS** and select the required IC (**74LS04D**) and click **OK** as shown in the Fig 4.

Fig 4

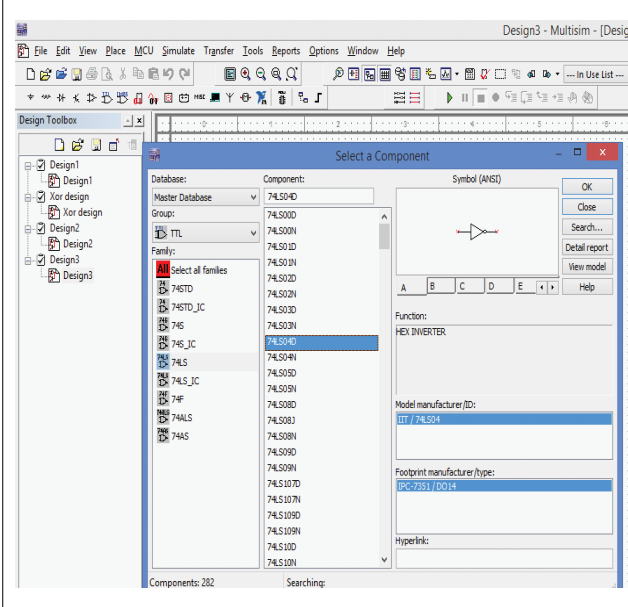

- 5 Click on A and OK, if more than one gate is required click on A and B, etc. as shown in the Fig 5.
- 6 Follow the step 4&5 to select the other logic gates 7408 and 7432 as shown in Fig 6.
- 7 Select the required resistor by referring the figure given in Fig 7 and click OK.

Fig 5

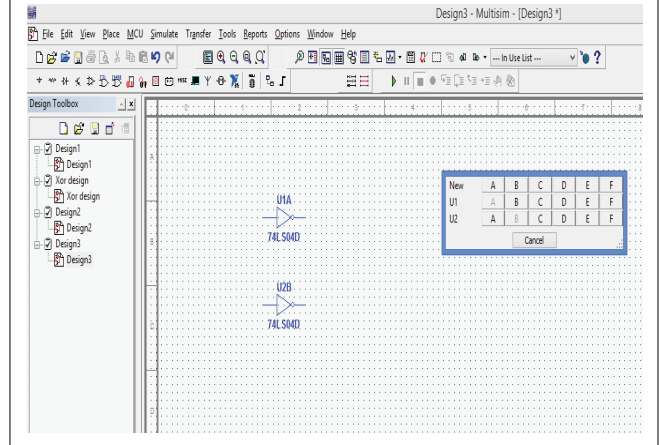


Fig 6



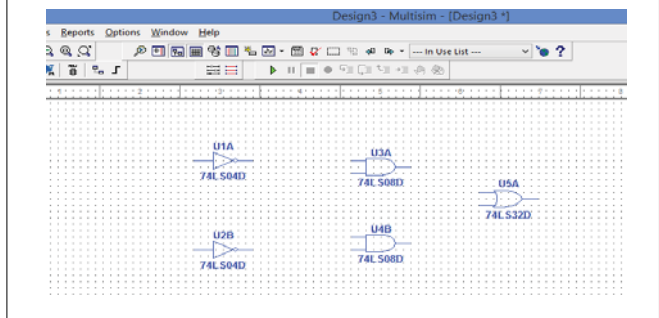


Fig 7

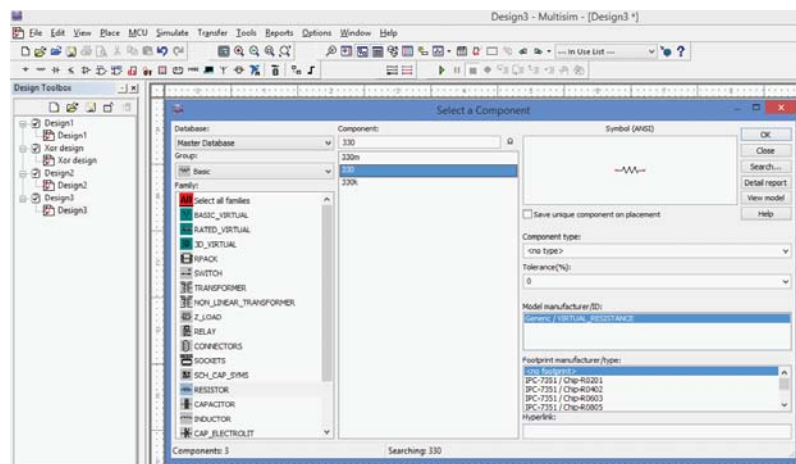

- 8 Select the required LED and click OK.
- 9 Add the power supply and ground to the circuit as shown in Fig 8.

Fig 8

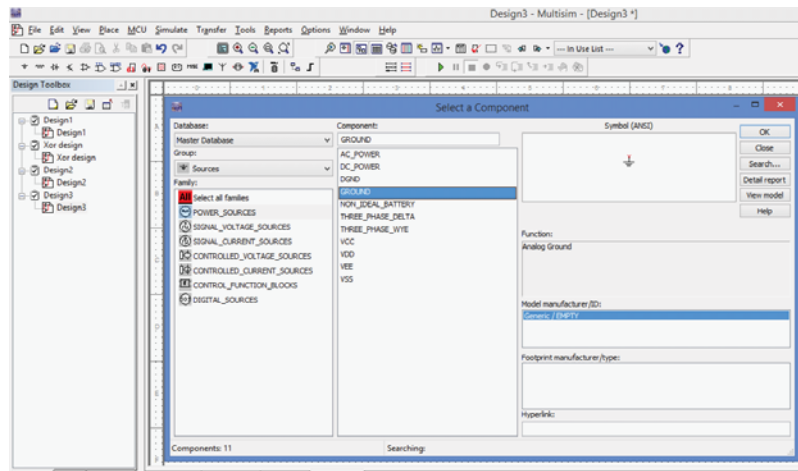


10 Make the wiring of the circuit by following Fig 1. Keep the cursor at one node of the component a dot will appear, move the cursor to the place of wiring the dot will appear at that node, now click the mouse to finish the wiring.

11 Double click on the power supply and change the label as A and B and set the voltages to 0.

12 Double click on the LED and change the label as C as shown in Fig 9 and save it.

Fig 9

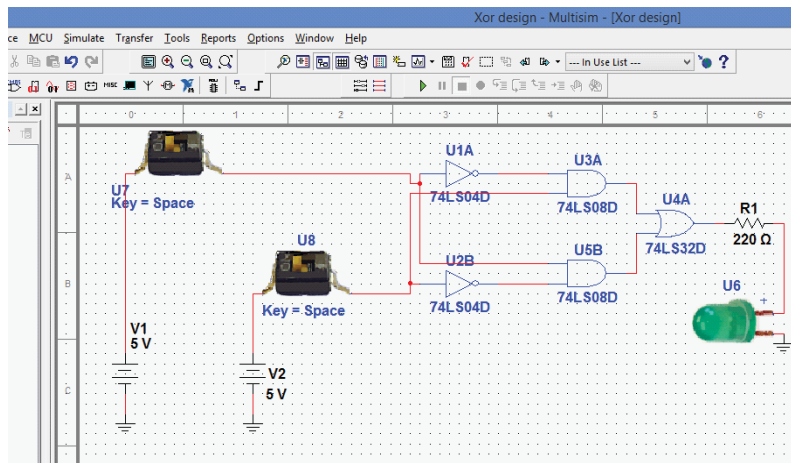

13 Get the work checked by the Instructor.

TASK 2 : Construction of positive shunt clipper circuit using simulation software

- 1 Select the positive shunt clipper circuit by referreing to the circuit as shown in in Fig 10.
- 2 Switch ON the computer, double click on the simulator icon on the desktop.
- 3 Click on semiconductor and then click on diode, drag the diode into the user area as shown in Fig 11
- 4 Double click on the diode in the user area and click on the TYPE.

Fig 10



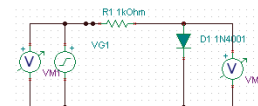


Fig 11

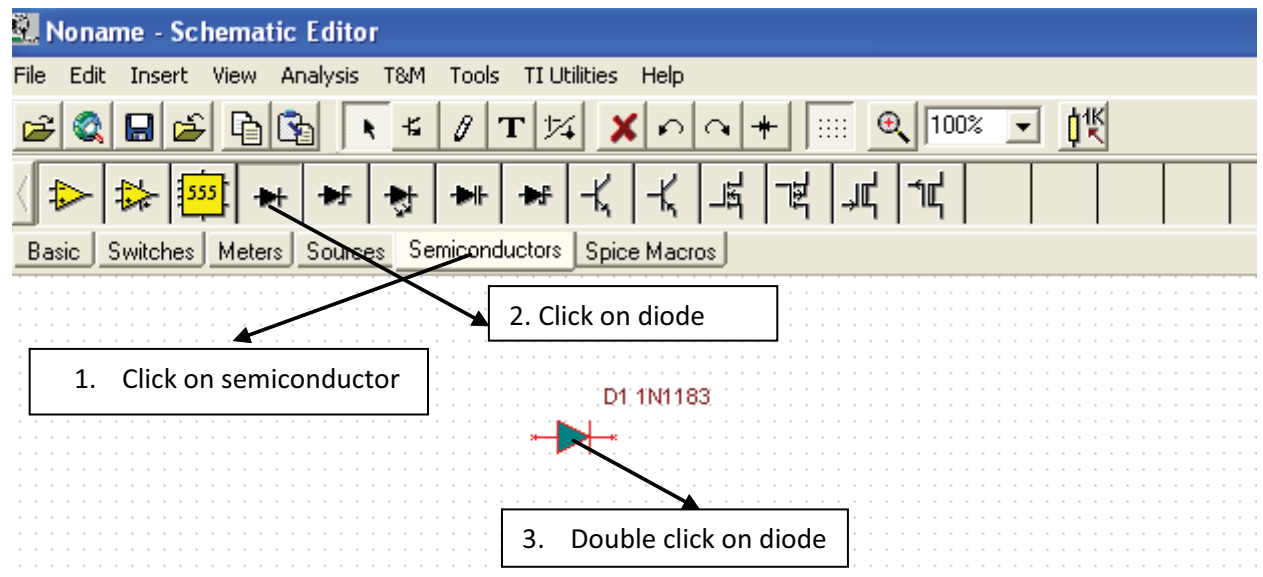

- 5 Select the suitable diode as shown in Fig 12 and Click on OK tab.
- 6 Ensure that the selected diode type number is displayed near the diode symbol.

Fig 12

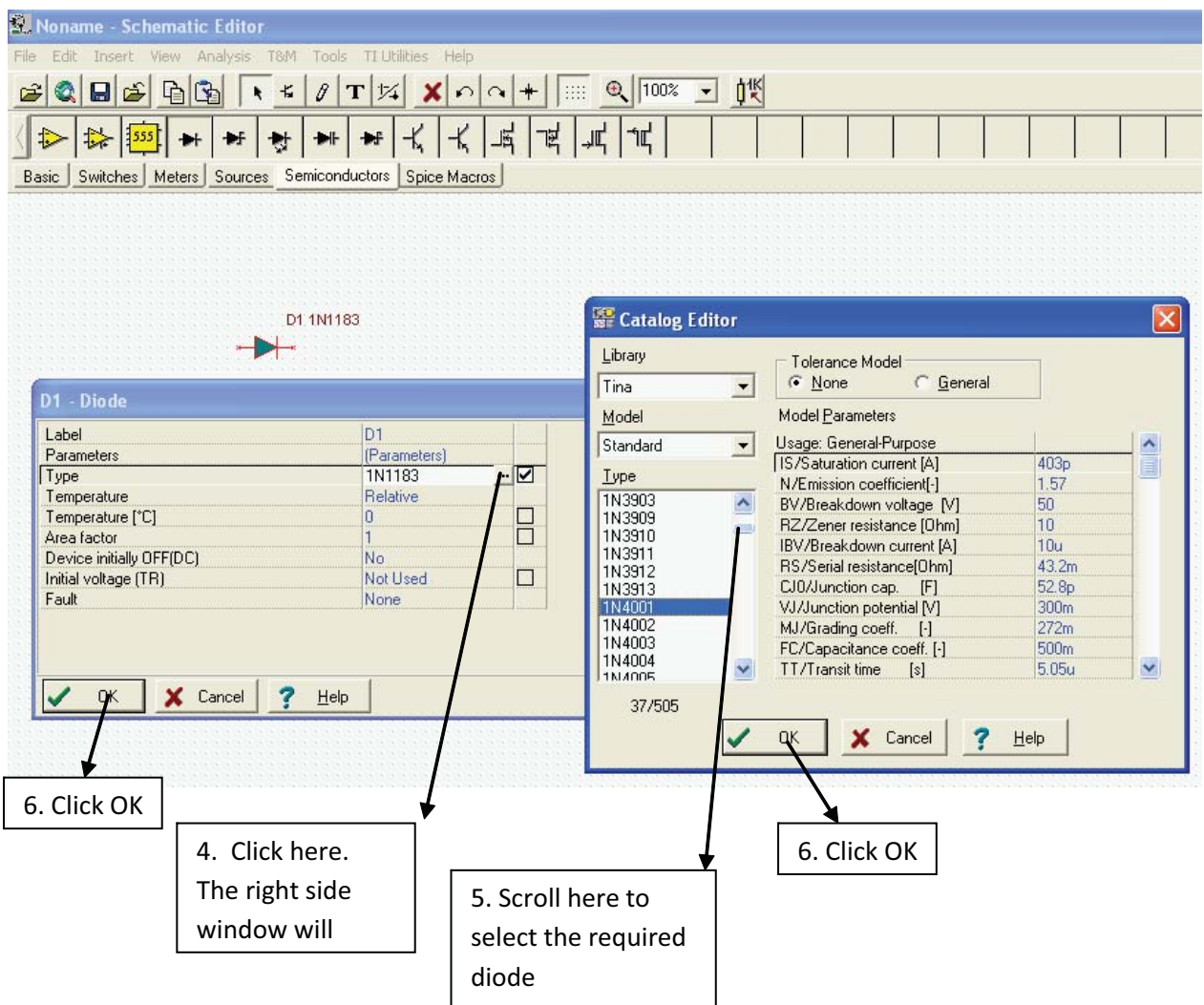

- 7 Right click on the diode select **Rotate Right** if you want to place the diode in the vertical position as shown in Figs 13 & 14.

Fig 13


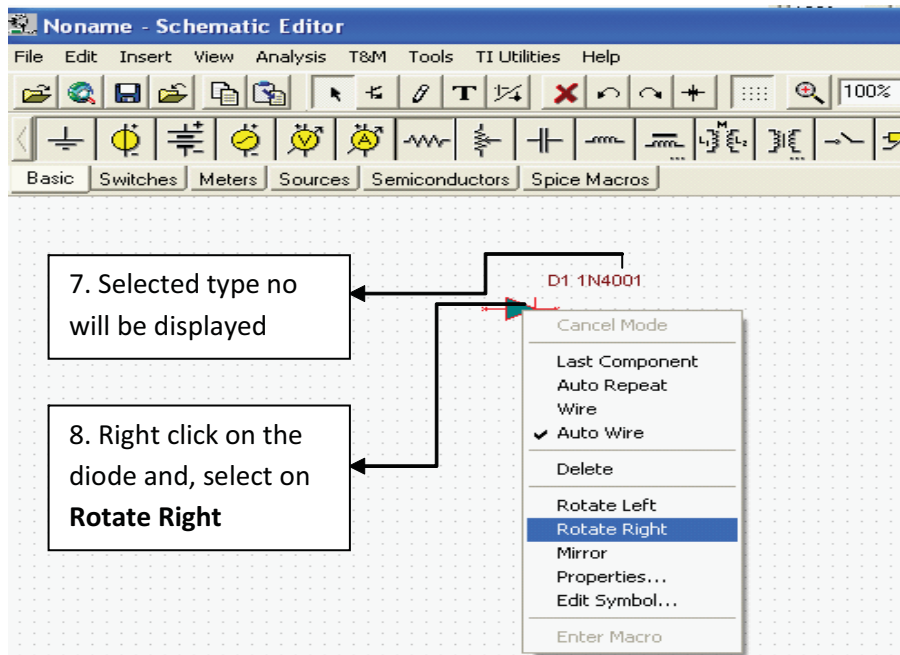



Fig 14

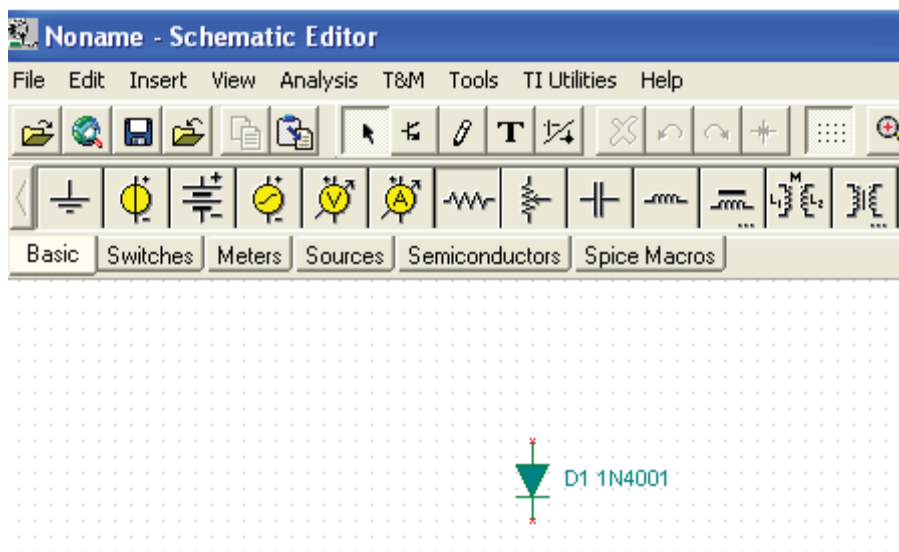

- 8 Click on **Basic** menu to select a resistor and click on resistor, drag the resistor into the user area.
- 9 Double click on selected resistor, type the value of resistor and click OK as shown in Fig 15.

Ensure that the selected resistor value is displayed near the resistor symbol.

Fig 15

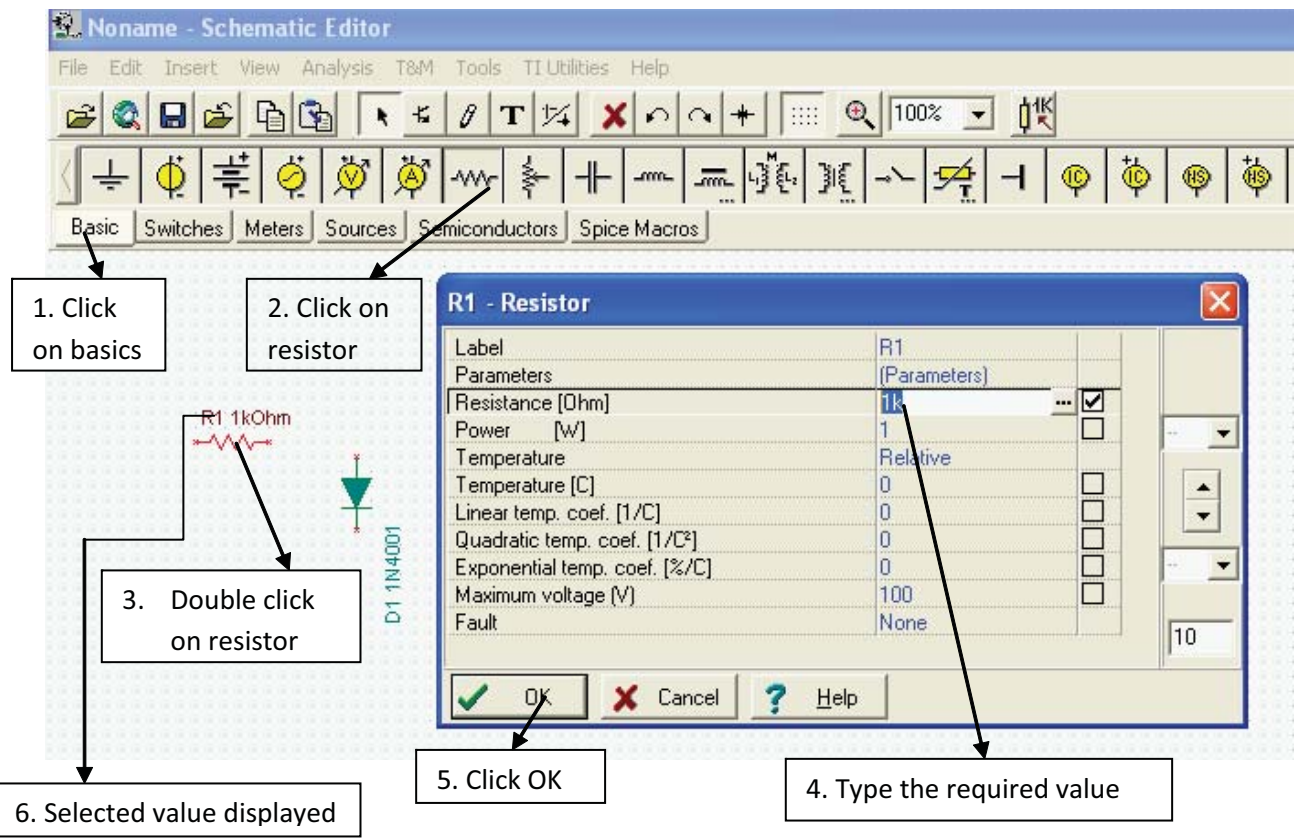


- 10 Keep the cursor at one of the resistor terminal and drag the mouse towards the terminals of the diode make the wiring.

Refer the circuit in figure 10 for making other connections.

- 1 Keep the cursor at the red dot of one of the terminal and then drag the mouse, till the red dot of the other device where you want to make the wiring.
- 2 If any component/device is edited by double clicking on it, the symbol will appear red, otherwise it appear in green colour.
- 3 Press ESC on the keyboard if you have clicked on any symbol which you donot want to use in the circuit.

- 11 Click on the **Sources** menu to connect a voltage generator and voltmeters.
- 12 Click on the **voltage generator** dialog box and double click on the generator symbol.
- 13 Click on **Signal** and then **Unit step** dialog box.
- 14 Click on the required waveform appearing in the pop up window as shown in Fig 16.
- 15 Click on amplitude, frequency and phase to select the required value respectively and click OK and save the circuit.

Fig 16

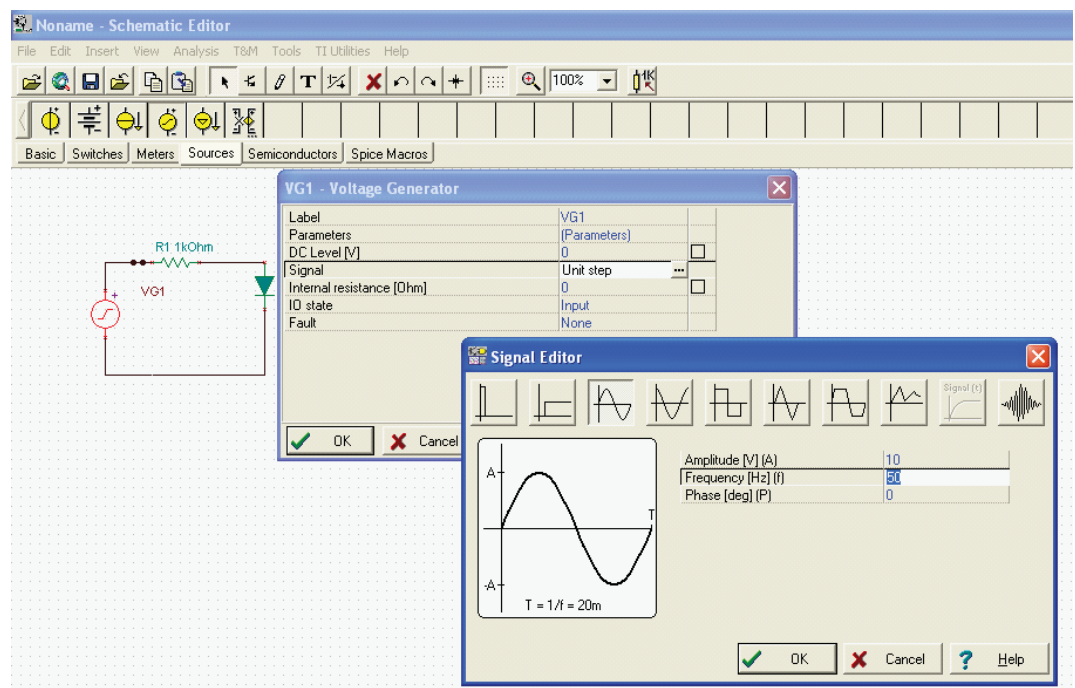

16 Get the work checked by the Instructor.

Simulate and test the prepared digital and analog circuits

Objectives: At the end of this exercise you shall be able to

- test the prepared digital circuits using simulation software
- test the prepared analog circuits using simulation software.

Requirements

Tools/Equipments/Instruments


- Desk top computer with simulation software installed - No

PROCEDURE

TASK 1 : Testing the constructed digital circuit (OR gate) using simulation software

- 1 Switch ON the computer, open the simulation software and open the saved OR gate circuit.
- 2 Click on simulate menu to run the circuit as shown in Fig 1.

Fig 1

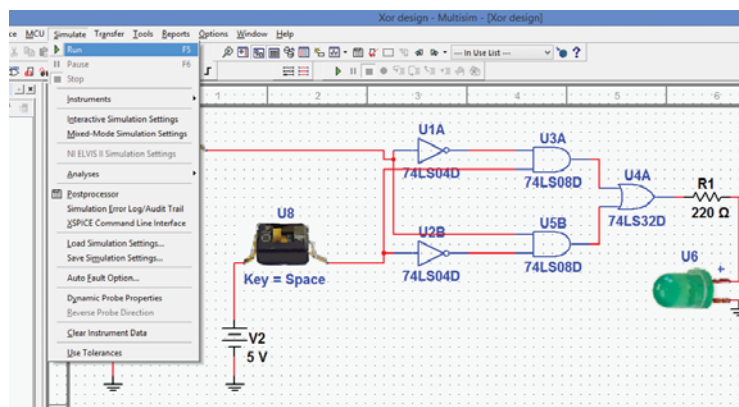


- 3 Modify the supply voltages as shown in the truth table and verify the truth table (If the output is one, the arrow in the LED will become RED (if red LED is selected; otherwise respective colour as shown in Fig 2, if the output is zero the arrow will be no glow).

Truth table of OR gate

S_1	S_2	LED condition
Open	Open	
Open	Close	
Close	Open	
Close	Close	

Fig 2

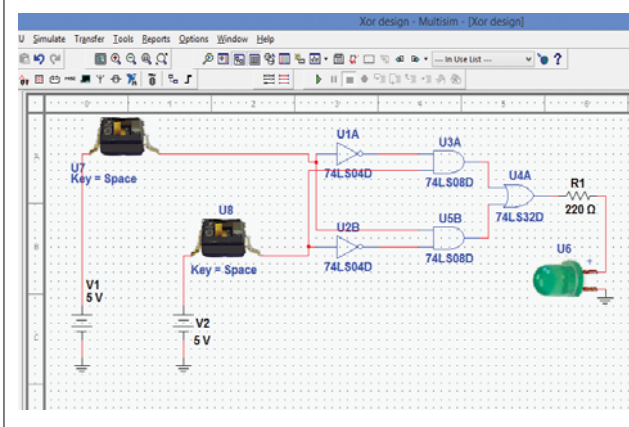

- 4 Get the work checked by the Instructor.

TASK 2 : Testing the prepared analog circuit positive shunt clipper using simulation software

- 1 Open the saved positive shunt clipper circuit.
- 2 Click on **meters** on the menubar.
- 3 Click and drag **volt meter** and connect across the voltage generator.
- 4 Once again Click and drag **volt meter** and connect across the diode (output terminal) as shown in Fig 3.
- 5 Click on **T&M** on the menubar, Select **oscilloscope** and click on it.
- 6 On pop up window Click on **Run** and observe the wave form displayed in the CRO.
- 7 Adjust **Time/div** and **Volt/div** positions to the suitable value as shown in Fig 4.
- 8 So that the waveform clearly seen select second channel by the probe in the CRO and click on the output terminal get both the waveforms visible on the CRO.

Fig 3


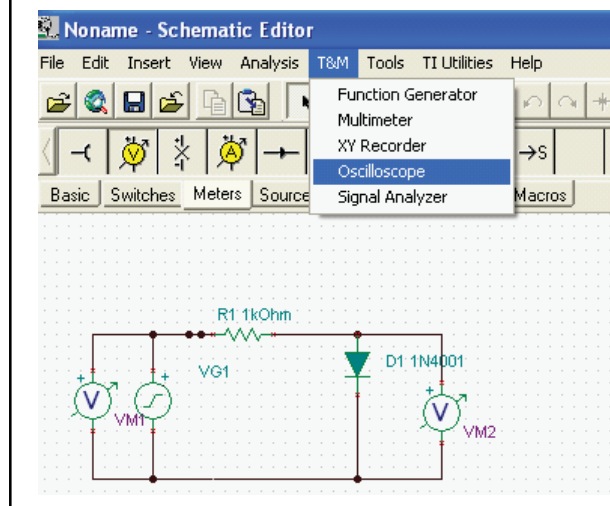


Fig 4

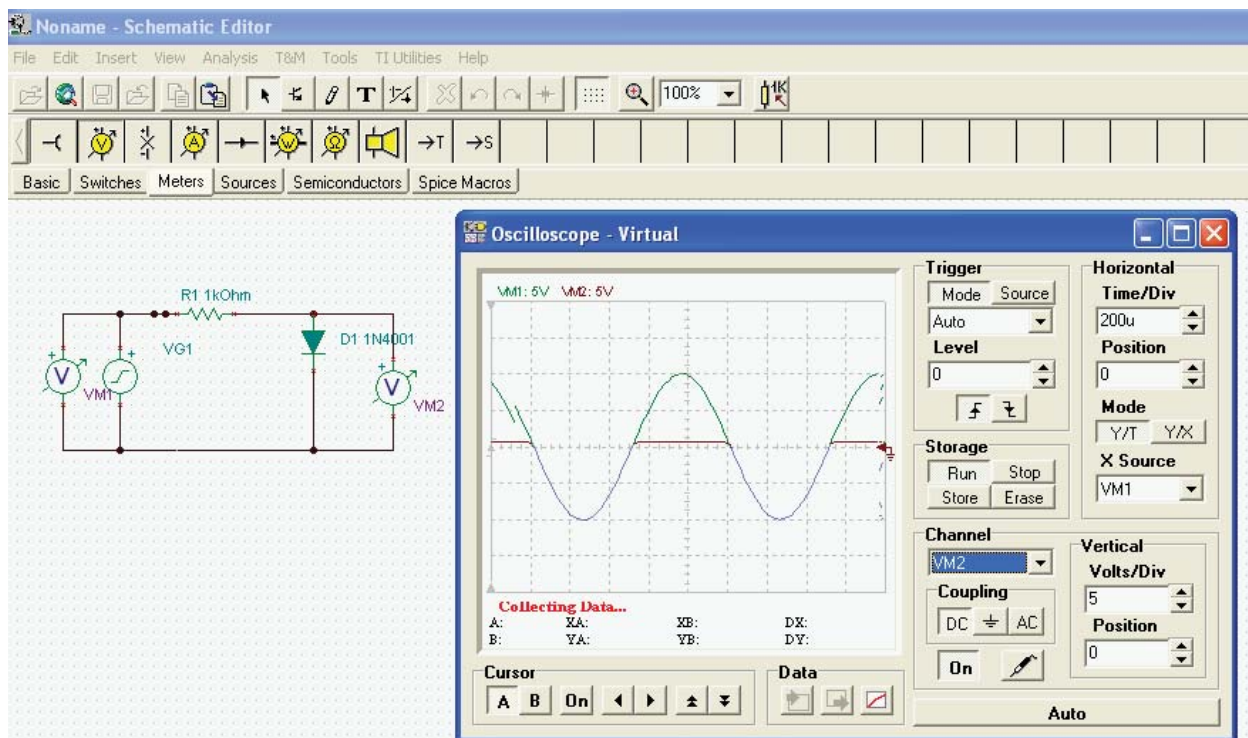

- 9 Click on stop , trace the waveforms and save it.

Save the circuit, so same circuit may be used later for revision.

- 10 Get the result checked by the Instructor.

Convert the prepared circuit into a layout diagram

Objectives: At the end of this exercise you shall be able to

- construct a single stage transistor amplifier using simulation software
- construct the prepared circuit into a layout diagram using simulation software.

Requirements

Tools/Equipments/Instruments

- Personal computer installed with simulation software


- 1 No

PROCEDURE

TASK 1 : Construction of a single stage transistor amplifier circuit using simulation software

- 1 Switch ON the computer, double click the icon on the desktop, open the software and pick the required components from the transistor amplifier circuit.
- 2 Place the required components, assemble the circuit in the work sheet area as shown in Fig 1.
- 3 Select required junction dot, terminal lead place in circuit for coupling required to construct wiring.
- 4 Connect the necessary equipments and instruments to the circuit as shown and save it.
- 5 Get the work checked by the Instructor.


Fig 1

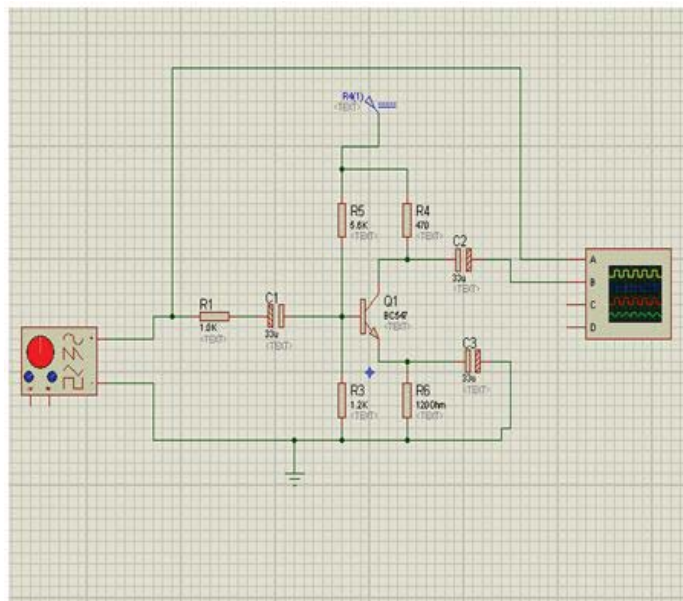

TASK 2 : Conversion of the prepared circuit into a layout diagram.

- 1 Open the circuit for conversion in the user area.
- 2 Click file menu, select convert PCB option and open PCB layout.
- 3 Click view menu, select grid size, and board outline.
- 4 Click and drag the components into the created layout.
- 5 Click for auto routing and save the layout diagram as shown in Fig 2.
- 6 Get the work checked by the Instructor.

Fig 2

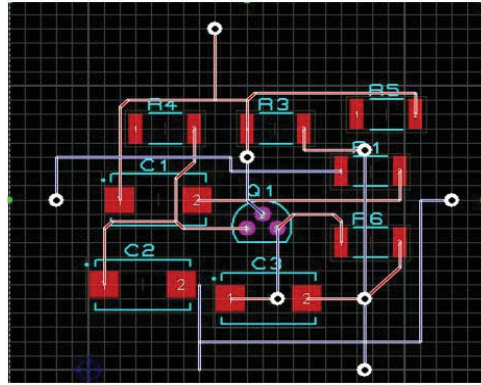

Prepare simple, power electronic and domestic electronic circuit using simulation software

Objectives : At the end of this exercise you shall be able to

- prepare a simple power electronic circuit (half wave rectifier) using simulation software.
- construct a domestic electronic circuit using simulation software.

Requirements


Tools/Equipments/Instruments

- Desk top computer installed with simulation software

PROCEDURE

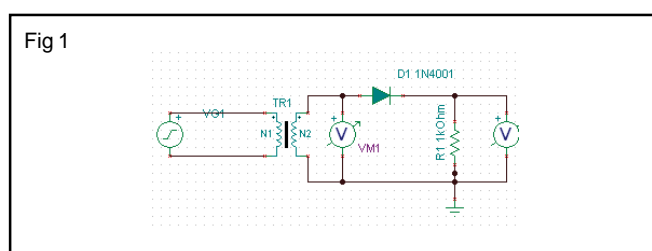TASK 1 : Construction of simple power electronic circuit (half wave rectifier) using simulation software

- 1 Select the components required for constructing the half wave rectifier as shown in Fig 1.



2. Switch ON the computer and double click on the simulator icon available in the desk top.


- 3 Refer to the Ex No. 2.8.155, Task 2, follow steps and select the required resistor, diode and voltmeter by clicking on them.

1 If you need to change the type of diode double click on diode & change its type.

2 To rotate the diode right click on it & select rotate option.


- 4 Click on Basics menu and on transformer, select ideal transformer.

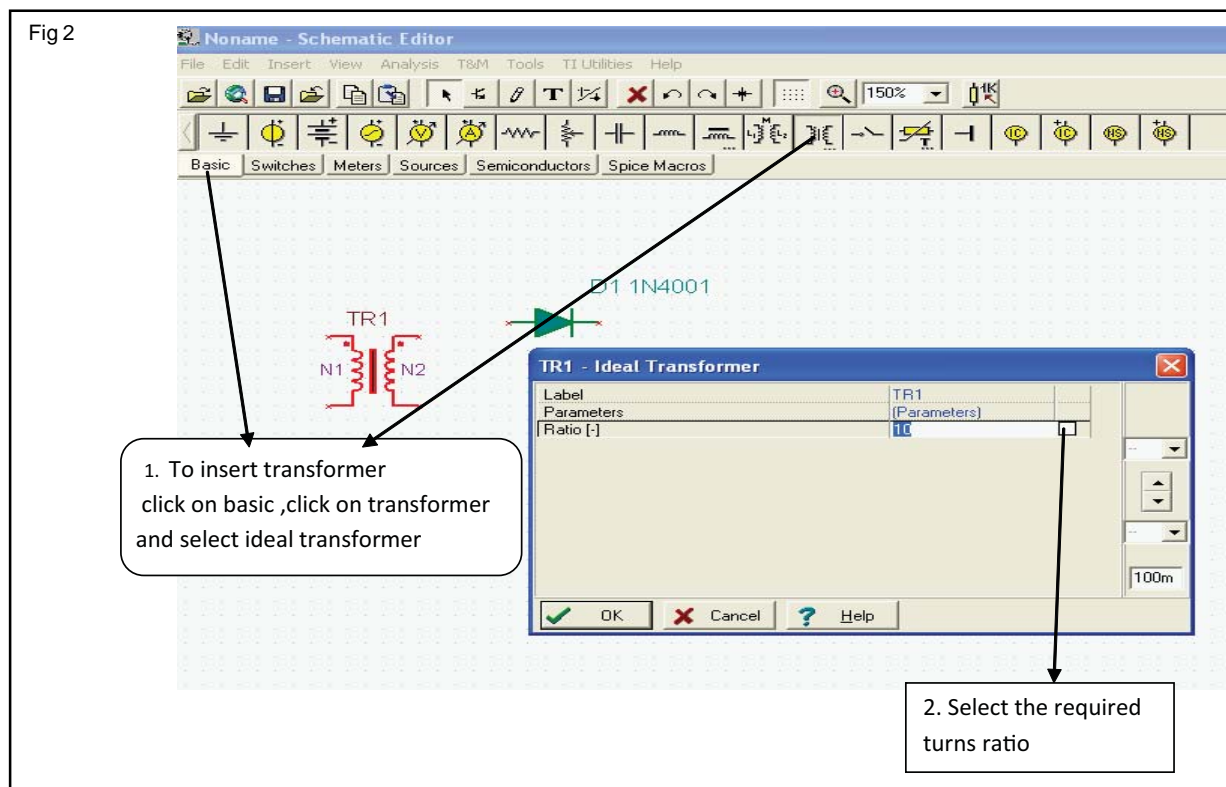- 5 Double click on the transformer, select the required turns ratio as shown in Fig 2.




- 6 Click on **source** menu and insert the voltage source.
- 7 Click on **voltage generator** and double click on voltage generator to fix the parameters as shown in Fig 3.

Fig 3

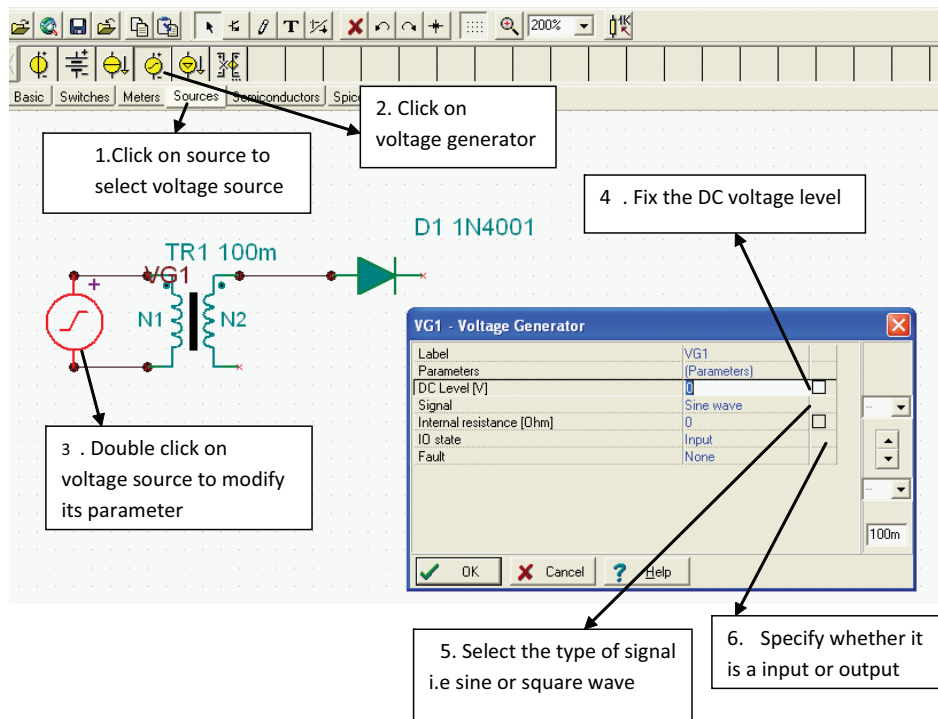

- 8 Click on signal dialogue box, set the type of waveform, amplitude, frequency & phase as shown in Fig 4.


Fig 4

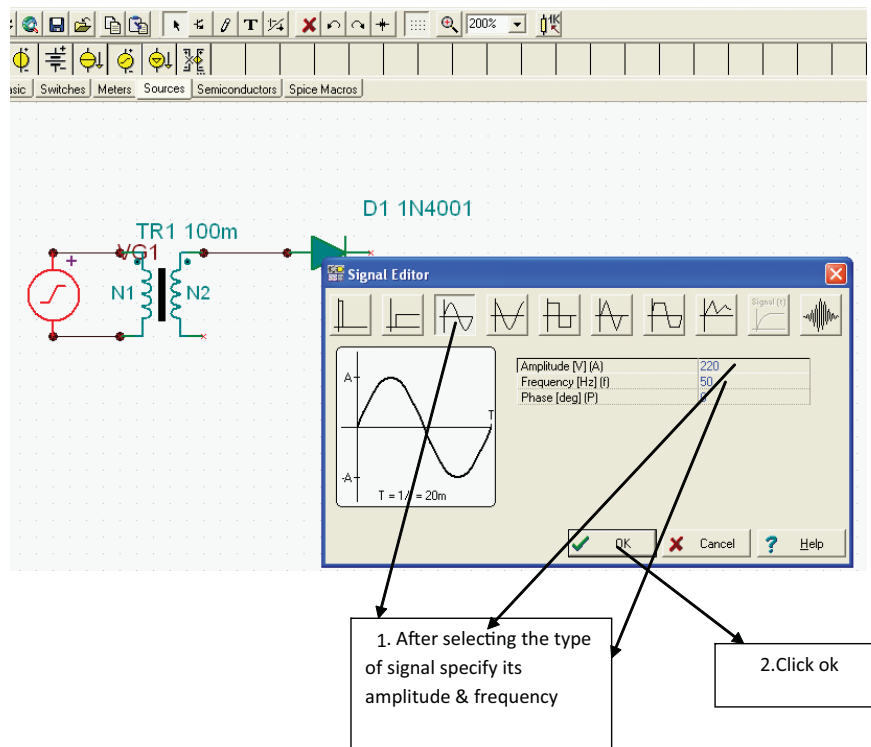

9 Make the connections by referring to the circuit diagram in Fig 1; Keep the cursor on the x mark on the component and drag the mouse wherever it need to be connected.

10 Go to menu bar & click T&M, select CRO as shown in Fig 5, click on it to use CRO.

11 Get the work checked by the Instructor.

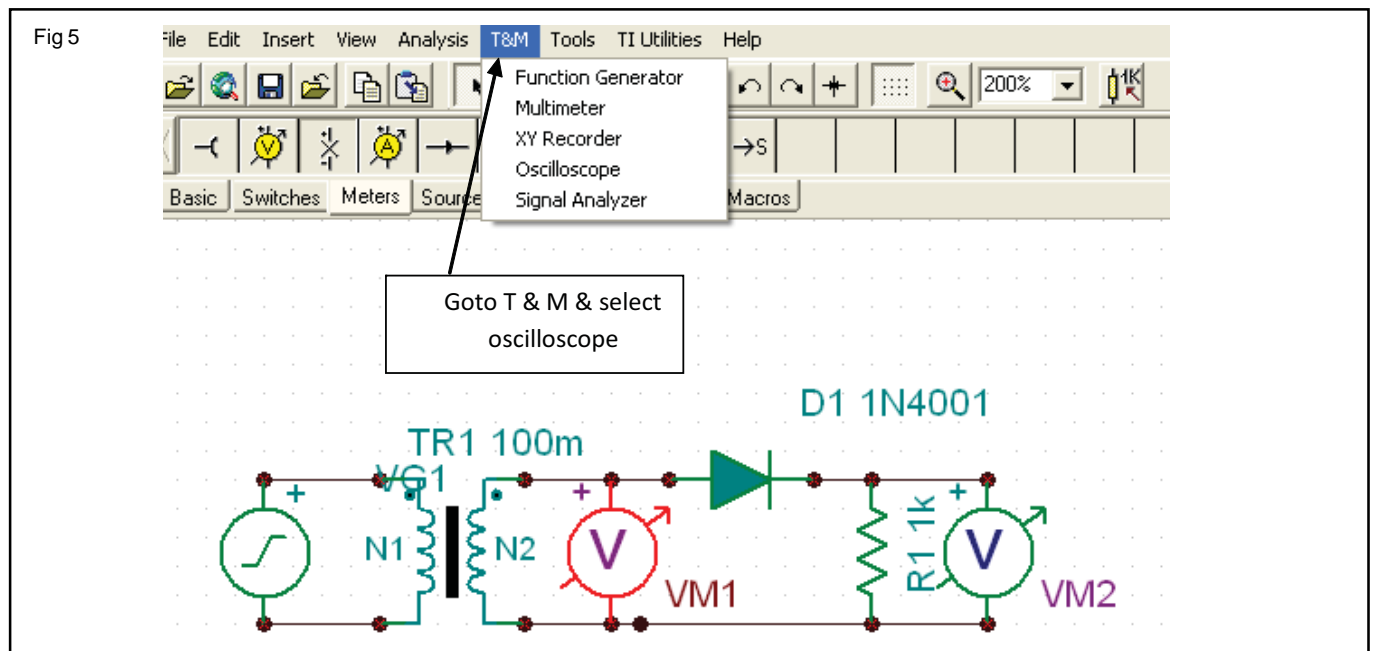


TASK 2 : Construction of electronic lamp dimmer circuit using simulation software

Note:

This exercise /Task has been developed using proteus - ISIS free simulation software.


The Instructor has to guide the trainees to follow each and every critical steps to select the components their values and placement / position, printing their numbers etc to complete the task as per the simulation software available in the lab.

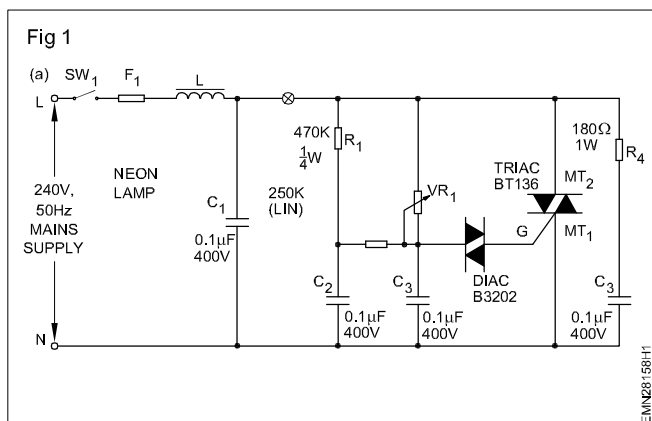1 Select the circuit for construction of electronic dimmer circuit as shown in Fig 1.




- 2 Switch ON the computer, double click the simulator icon on the desktop.
- 3 Open a new project the schematic and go to the schematic capture option.
- 4 Click and select all the parts required from resistors, capacitor to diac and triac into the library as shown in Fig 2.
- 5 Move the cursor, select the triac, left click drag and place it on the user area place and position it on the user area.
- 6 Similarly select and place all the components, voltage source etc as per the diagram of the dimmer circuit.
- 7 Click the cursor to wire the connection on the component tip a red square dot appears move the cursor click again complete the wiring.

Fig 2

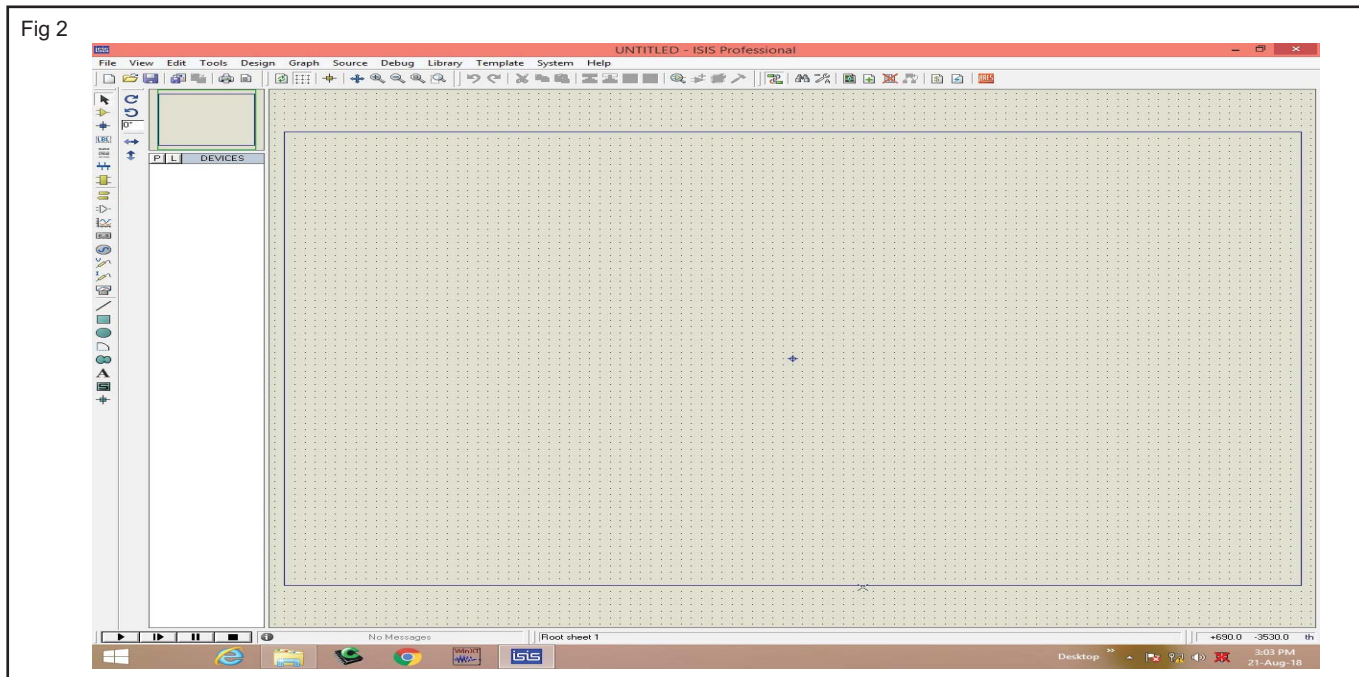

- 8 Close the switch S1 and observe the bulb is ON and adjust the a rheostat VR1 the brightness is reduced as shown in Fig 3.

Fig 3

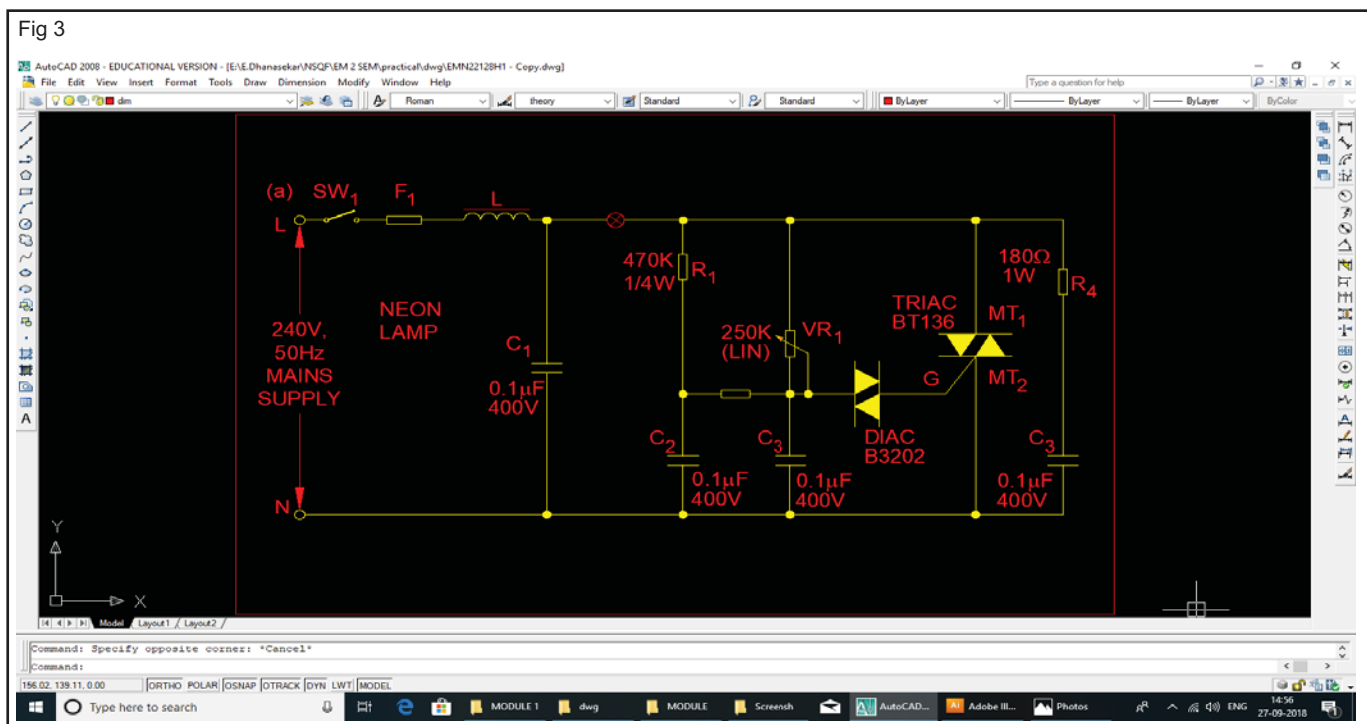

- 9 Get the work checked by the Instructor.

Construct and test a four bit asynchronous binary counter using IC 7493

Objective: At the end of this exercise you shall be able to




- construct and test trace bit asynchronous binary counter using IC 7493. (4 bit ripple counter).

Requirements		
Tools/Equipments/Instruments		Materials/Components
<ul style="list-style-type: none">• Digital multimeter with test probes• DC power supply, 0-30V/2A• Function Generator• Dual trace CRO 0-20 MHz	- 1 No	• Breadboard
	- 1 No	• 74LS47 (BCD-to-7 segment decoder chip)
	- 1 No	• IC 74LS93 (Asynchronous binary counter)
	- 1 No	• LED 5mm, Red
	- 4 Nos	• Resistor 330Ω/¼ W/CR25
	- 4 Nos	• Connecting Hook up wire
	- as reqd	• 7 Segment display (CA)
	- 1 No	

PROCEDURE

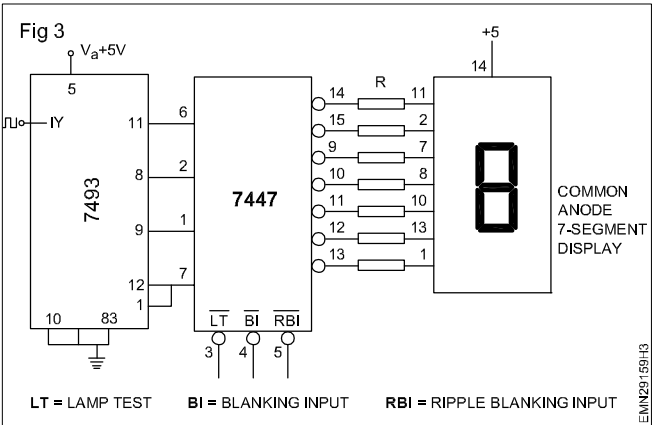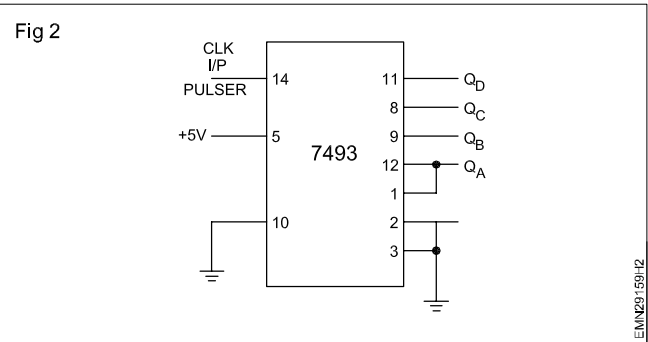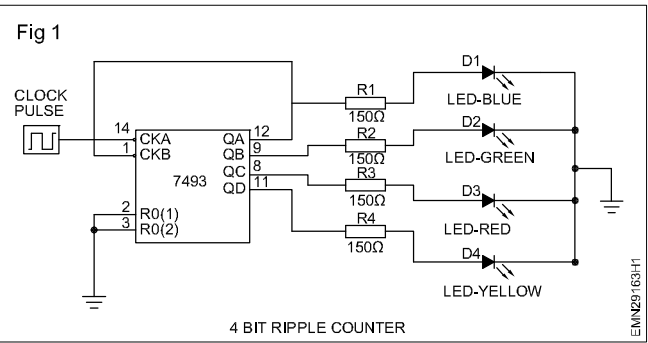TASK 1: Construction and testing of asynchronous binary counter using IC7493 (4 bit ripple counter)

- 1 Assemble the 4-bit ripple counter shown in Fig 1.
Internal diagram of IC 7493 shown in Fig 2.
- 2 Operate the pulser to verify that the count goes from zero (0000) to fifteen (1111).
- 3 Connect the Clock pulse at Pin No. 14 of IC and use a dual trace oscilloscope to observe the waveforms at the clock and the counter outputs.
- 4 Alternately connect seven segment driver IC 7447 to display on seven segment LED as shown in Fig 3.
- 5 Get the work checked by the Instructor.



Construct and test 7493 as a modulus - 12 counter

Objectives: At the end of this exercise you shall be able to
 • construct and test modulus 12 counter using TTL IC-7493.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- DC power supply 0-30V/2A - 1 No
- DMM with probes - 1 No
- Clock pulse generator - 1 No
- Dual trace CRO-20 MHz - 1 No



Materials/Components

- Breadboard - 1 No
- IC 7493 - 1 No
- LED 5mm, Red - 5 Nos
- Resistor 330Ω/¼ W/CR25 - 5 Nos
- Connecting wire (hook - up) - as reqd
- IC 7447 & 7 segment display - 1 Set

The 7493 is a four - bit ripple type binary counter. It consists of four flip-flops which are connected as shown in Figure below. In order to function as a four-bit counter, CP₁ must be externally connected to QA. If both the master reset pins MR₁ and MR₂ are raised high, the four-bit flip-flops are reset to zero.

PROCEDURE

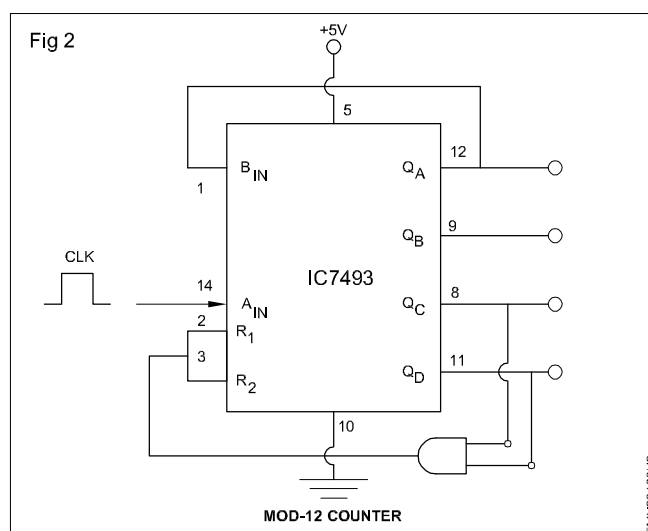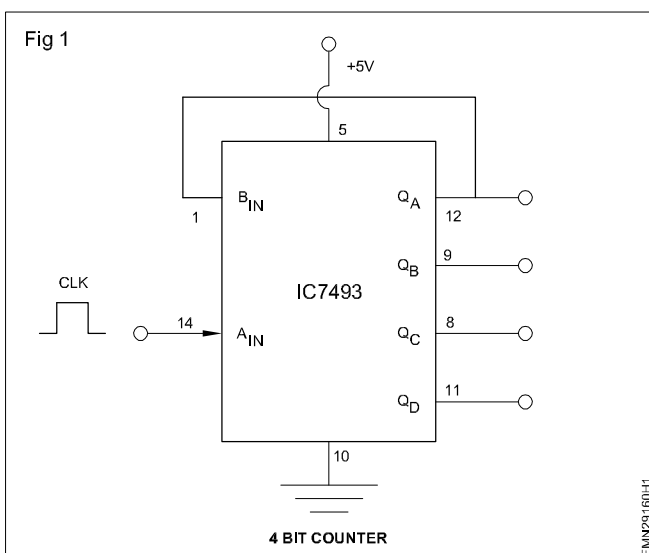- 1 Connect the modulus 12 counter using 7493 on bread board referring to circuit shown in Fig 1 & 2.
- 2 Connect Q_C & Q_D (pins 8 & 11) to MR₁ & MR₂ (pins 2 & 3) respectively.
- 3 Get the assembled circuit checked by the instructor
- 4 Switch on +5V regulated DC power supply.
- 5 Press CLEAR-A & CLEAR-B push buttons switch once, to clear the outputs of all flip flops.



- 6 Record the Q-outputs (Q_A to Q_D) of all the 4-flip flops based on the LEDs status.
- 7 Apply one clock pulse at the input (first PIN of IC-7493 i.e Cp₁) using the single shot pulser.
- 8 Record the output logic levels and the status of LEDs A,B,C,D in Table 1.
- 9 Repeat the steps with 7-segment driver IC 7447 & 7seg display as shown in Fig 3 of Ex 2.9.159.

Table 1

Input	Four bit mod-12 counter			
Count	QD	QC	QB	QA
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				
11				

10 Get the recorded reading checked by the Instructor.

Construct and test a four bit synchronous binary counter using IC 74163

Objectives: At the end of this exercise you shall be able to

- construct and test synchronous binary counter using IC 74163.

Requirements

Tools/Equipments/Instruments

- Multimeter with probes - 1 No
- DC power supply, 0-30V/2A - 1 No
- Clock pulse generator 1 Hz - 1 No
- Dual trace CRO, 0-20 MHz - 1 No

Materials/Components

- Breadboard - 1 No
- I.C 74LS47 - 1 No
(BCD-to-7 segment decoder chip)
- IC 74LS163 (synchronous binary counter) - 1 No
- IC 7404 - 1 No
- LED 5mm, Red - 4 Nos
- Resistor 270Ω/¼ W/CR25 - 4 Nos
- Lengths of jumper wire/connecting wire (hook-up) - as reqd

Inside the IC74163

There are two separate enable inputs, ENT and ENP, setting either of these inputs to logic 0 stops counting asynchronously. Ripple Carry Output (RCO) is normally at logic 0 and goes to logic 1 when counter reaches its highest count i.e., '1111'. It is used in cascading multiple 74163 ICs. Load is an active, low input which allows the count on 'ABCD' to reflect on 'Q_A Q_B Q_C Q_D' at active clock edges. CLR is also an active low input which clears counter as asynchronously to '0000'.

PROCEDURE

TASK 1 : Construction and testing of synchronous binary counter

- 1 Collect all the components, check them and assemble the circuit on the breadboard as shown in Fig 1. The Pin details of IC 74163 is shown in Fig 2.
- 2 Get the assembled circuit checked by the Instructor.
- 3 Apply clock pulses using pulse Generator and observe the counter outputs in LEDs and noted in Table 1.
- 4 Make CLR input to logic-0 and reset the counter.


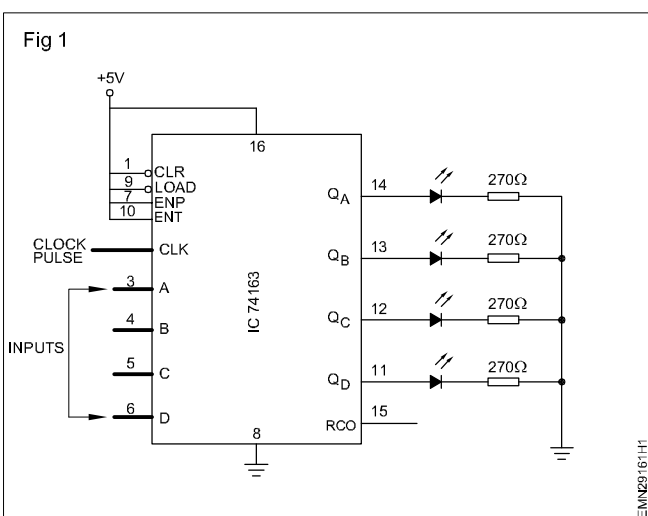


Fig 2

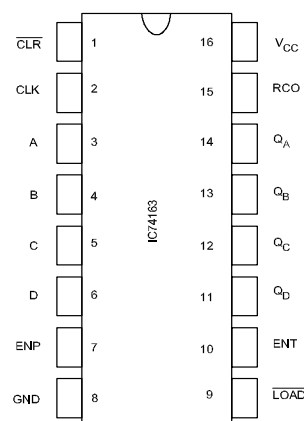

- 5 Repeat counting by making CLR input to logic - 1.
- 6 Use IC 74LS47 and 7 - segment LED as shown in previous exercise 2.9.159 to obtain & view a decimal - counted value on display.
- 7 Record the readings in Table 1.

Table 1

S.No.	Pulse count	Q _D	Q _C	Q _B	Q _A	7-Seg display reading

8 Get the work checked by the Instructor.

Construct and test synchronous Decade counter

Objectives: At the end of this exercise you shall be able to


- construct and test synchronous decade counter.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
<ul style="list-style-type: none">• Trainees tool kit• DC power supply, 0-30V/2A• Logic with probes	- 1 Set	• IC 74LS90 (Decade counter)	- 1 No
	- 1 No	• IC 7447 (7-seg driver)	- 1 No
	- 1 No	• 7-seg display	- 1 No
		• Resistor 330Ω/¼ W/CR25	- 8 Nos
		• LED Red, Green	- 4 Nos

- 1 Assemble a ripple binary counter on a breadboard referring to the circuit shown in Fig 1.
- 2 Get the assembled circuit checked by the instructor.
- 3 Switch on +5V regulated DC power supply. Press CLEAR push button switch once, to clear the outputs. Observe the Q-outputs (Q₀ to Q₃) based on the LEDs status (ON/OFF) in Table 1 of record sheet.
- 4 Apply one clock pulse at the input at pin 14 and record the output logic levels. Observe outputs of IC 7490 using logic probe.
- 5 Repeat step 4 and verify the output logic levels for successive clock pulse input and observe the status of output QA, QB, QC and QD after giving each clock pulse at the input as shown in Table 1.
- 6 Repeat step 3 to clear the output of all flip-flops.
- 7 Use IC 74LS47 and 7-seg display to observe the count value in decimal.
- 8 Get the work checked by the Instructor and observe counter output on 7 seg display.

Table 1

Clock Pulse	QD	QC	QB	QA
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

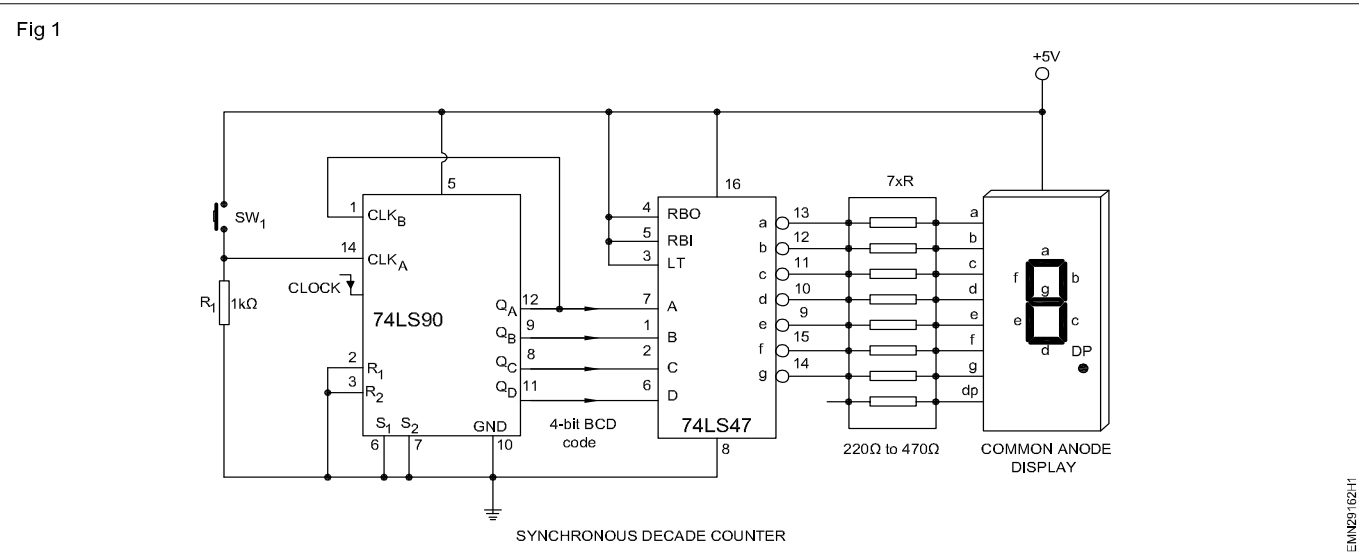

Construct and test an UP/DOWN synchronous decade counter using 74190 and monitor the output on LEDs

Objectives: At the end of this exercise you shall be able to

- construct an up/down counter using IC 74LS190
- test the counter for counting UP and counting DOWN.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Regulated power supply 0-30V/2A - 1 No
- Logic probe - 1 No
- Single shot pulser - 1 No

Materials/Components

- Breadboard - 1 No
- IC74LS190 (Up/down decade counter) - 1 No
- LED 5mm (Red, Green, Amber, Yellow) - 1 No each
- Resistors 220Ω, ¼ W/CR25 - 4 Nos
- Switches SPDT - 2 Nos
- Connecting wires/ Hook up wires - as reqd


PROCEDURE

TASK 1: Construction of synchronous UP/DOWN decade counter using 74 LS190

- 1 Collect all the components, check them and assemble the circuit of a up/down decade counter on a breadboard using IC74LS190 as shown in Fig 1.
- 2 Get the assembled circuit checked by the instructor.

Note:

- Up/Down decade counter counts from 0 to 9 and then recycles to '0' again.
- Pin-5 determines the direction of count when this input is high the counter counts down, when it is low, the counter counts up.
- MAX/MIN - The output at this pins counts high when the counter is reached at NINE (1001).

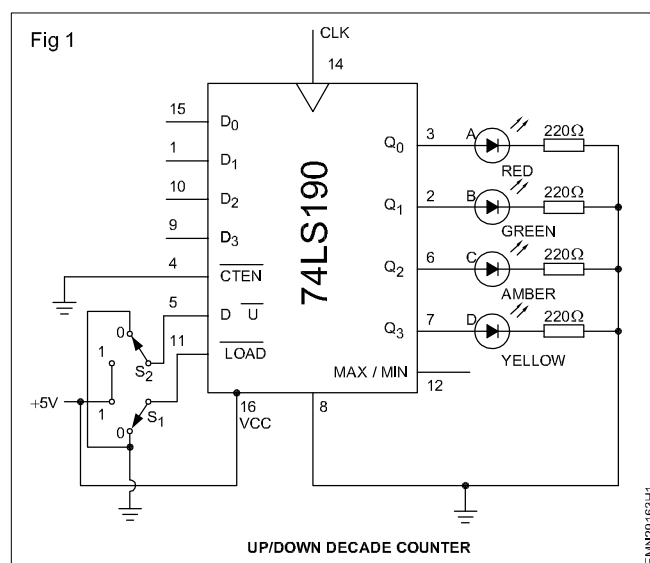

TASK 2: Setting the decade counter to count-up mode and test

- 1 Switch ON the supply and apply +5V regulated DC supply to the circuit.
- 2 Apply logic-0 to the control pin D to make the counter count-up through a toggle switch.
- 3 Apply logic 0 to the pins D₀ to D₃. Apply logic-0 to the control pin \overline{LOAD} momentarily and raise it back to Logic-1 state with a toggle switch.
- 4 Refer Table 1 of record sheet and feed clock pulses at clock input (pin 14) using single shot pulser. Record the status of LED(s) at outputs Q₃, Q₂, Q₁ and Q₀.
- 5 Record the logic levels at Q₃, Q₂, Q₁, and Q₀ using the logic probe in Table 1.
- 6 From the recorded readings at steps 4 and 5 conclude whether the counter is counting-up or down.
- 7 Get the recorded output and your conclusion checked by the Instructor.

This sets output Q₃, Q₂, Q₁, Q₀ to logic-0 levels.

- 8 Repeat steps 3, 4, 5 and 6 to recheck satisfactory working of the counter.

Table 1 Up counter

D/ \bar{U} Pin No.5	Clock input Pin No.14	\overline{LOAD} Pin No.11	Status of LEDs			
			D ₀	D ₁	D ₂	D ₃
0	x		0	0	0	0
0	↑	1	x	x	x	x
0	↑	1	x	x	x	x
0	↑	1	x	x	x	x
0	↑	1	x	x	x	x
0	↑	1	x	x	x	x
0	↑	1	x	x	x	x
0	↑	1	x	x	x	x
0	↑	1	x	x	x	x
0	↑	1	x	x	x	x

Conclusion: _____

- 9 Get the work checked by the Instructor.

TASK 3: Setting the decade counter to count-down mode and test

- 1 Feed D₃, D₂, D₁ and D₀ with 1001 (binary 9) by applying suitable voltage levels (logic-1=+5V and logic-0=0V).
- 2 Apply logic-0 to \overline{LOAD} input (pin-11) momentarily and raise it back to logic-1 level.
- 3 Apply logic-1 to D/U (Down/Up, pin 5) such that the counter is prepared for count-down operation.
- 4 Refer Table 2 and feed clock pulses at clock input (Pin 14). On feeding each clock pulse record the output Q₃, Q₂, Q₁ and Q₀.
- 5 From the recorded readings at step 4, conclude whether the counter is counting-up or counting-down.
- 6 Repeat steps 1 to 5 to recheck satisfactory working of the down-counter.
- 7 Get the working of the circuit and the recorded output checked by the Instructor.

This sets the outputs Q₃, Q₂, Q₁ and Q₀ to 1001 such that this becomes the starting value for the down counter.

Table 2-Down Counter

D/ \bar{U} Pin No.5	Clock input Pin No.14	\overline{LOAD} Pin No.11	Status of LED(S)			
			D ₀	D ₁	D ₂	D ₃
x	x		1	0	0	1
1	↑	1				
1	↑	1				
1	↑	1				
1	↑	1				
1	↑	1				
1	↑	1				
1	↑	1				
1	↑	1				

Conclusion: _____

Identify and test common anode and common cathode seven segment LED display using multimeter

Objectives: At the end of this exercise you shall be able to
• test the common anode and common cathode by using multimeter.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
• Multimeter with probes		• Seven segment LED (common anode)	- 1 No
		• Seven segment LED (comon cathode)	- 1 No

PROCEDURE

TASK 1 : Testing the seven segment - LED display and identify the type

- 1 Collect the components from Instructor. Check the 7-seg display units by using multimeter.
- 2 Identify the given display whether it is common anode (or) common cathode using data book.
- 3 Check each segment using multimeter in diode mode as shown in Fig 1. (Each segment is an LED inside when forward biased LED glows when reverse biased LED does not glow). Refer to Fig 3 to know the common terminal.



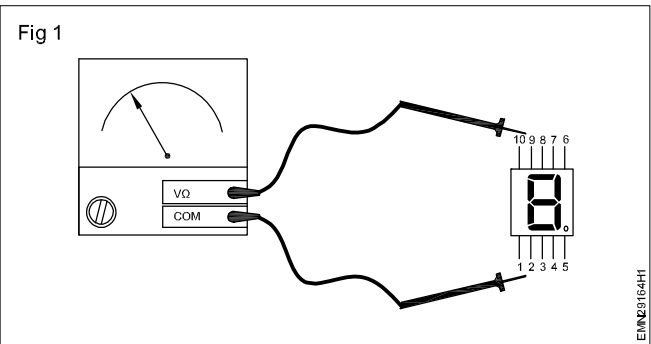
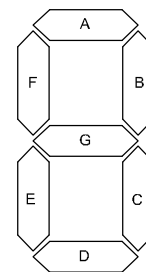


Fig 2

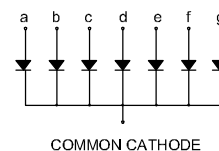

EMN29164H2

Fig 3

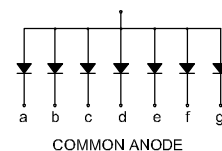

EMN29164H3

- 4 Multimeter +ve terminal is connected to common pin and -ve terminal is connected to all pins.
- 5 7 Segment pins are 10 numbers and 2 pins are common. 1 pin is dot (Details of Pin).
- 6 Repeat the checking procedure for the other type of display.
- 7 Get the work checked by the Instructor.

Display the two digit count value on seven segment display using decoder/driver ICs

Objectives : At the end of this exercise you shall be able to

- construct and test a decade counter using IC No.7490 with a BCD to seven segment decoder/driver and 7-segment display
- construct a 2 digit counter & display count value.

Requirements		
Tools/Equipments/Instruments		
• Trainees tool kit	- 1 Set	
• DC power supply, 0-30V/2A	- 1 No	
• Logic probe	- 1 No	
Materials/Components		
• IC-7490	- 2 Nos	
• IC-7447	- 2 Nos	
		<ul style="list-style-type: none"> • IC base 14 pin - 2 Nos • IC base 16 pin - 2 Nos • 7-segment LED display FND507 - 2 Nos • Resistors 330Ω/¼W/CR25 - 7 Nos • Logic probe - 1 No • Single shot logic pulser - 1 No • General purpose IC TB/Bread board - 1 No • Solder, flux - as reqd • Connecting wires - as reqd

PROCEDURE

TASK 1: Construction and testing of a decade counter using IC7490

- 1 Collect all the components, check them and assemble the decade counter using IC 7490 on the bread board as shown in Fig 1.

Make use of IC base to connect IC7490

- 2 Reset the counter output by applying logical 1 input momentarily to reset input pins 2 & 3.
- 3 Test and record the output logic levels in Table 1 using logic probe.
- 4 Apply a clock pulse at Pin no. 14 using single shot logic pulser and note down the output logic levels in Table 1 at QA, QB, QC & QD using logic probe.
- 5 Repeat step 4 for different clock pulses and record the observations in the table.

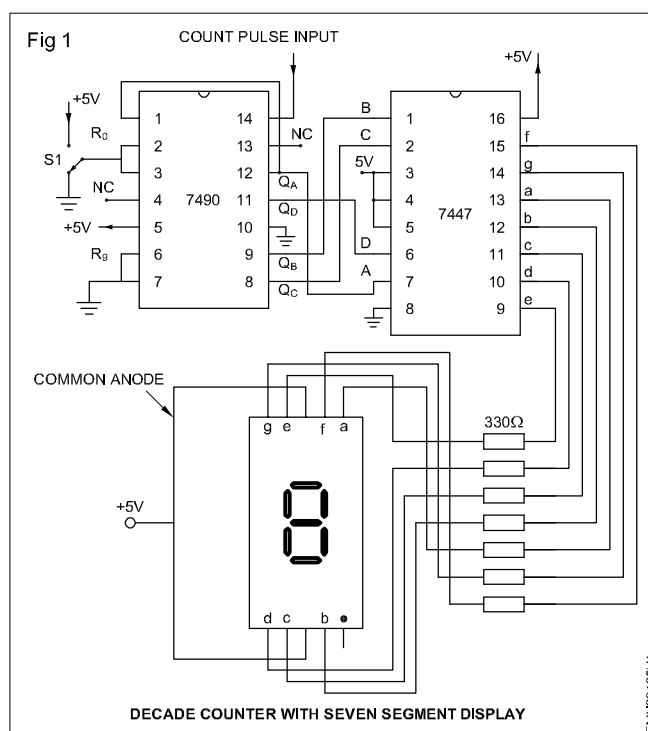


Table 1 Testing of decade counter IC7490

Clock input	Output				Decimal number displayed
	Q _D	Q _C	Q _B	Q _A	
0 (reset)					
1					
2					
3					
4					
5					
6					
7					
8					
9					
10					


6 Get the work checked by the Instructor.

TASK 2: Construction and testing of decoder/driver with seven segment display for two digit count value

- 1 Assemble the circuit shown in Fig 2 with decoder/driver 7-segment display refer Fig 1 and construct the remaining part of the circuit using decoder/driver IC7447 on the same bread board used in the previous task.
- 2 Connect the seven segment display module to the decoder/driver by referring to Fig 1.
- 3 Get the assembled circuit checked by the instructor.
- 4 Reset the counter output by applying logical 1 input momentarily to reset input pins 2 & 3 and record the 7-segment output of 7447 and the number displayed on seven segment display in Table 2.
- 5 Apply a clock pulse at Pin no.14 using single shot logic pulser and note down the number displayed on seven segment display in Table 2.
- 6 Repeat step 5 for different clock pulses and record the observations.

Compare and relate the output levels of IC7490 and the corresponding displayed values on the seven segment display for each of the clock pulse applied at Pin no.14.

Fig 2

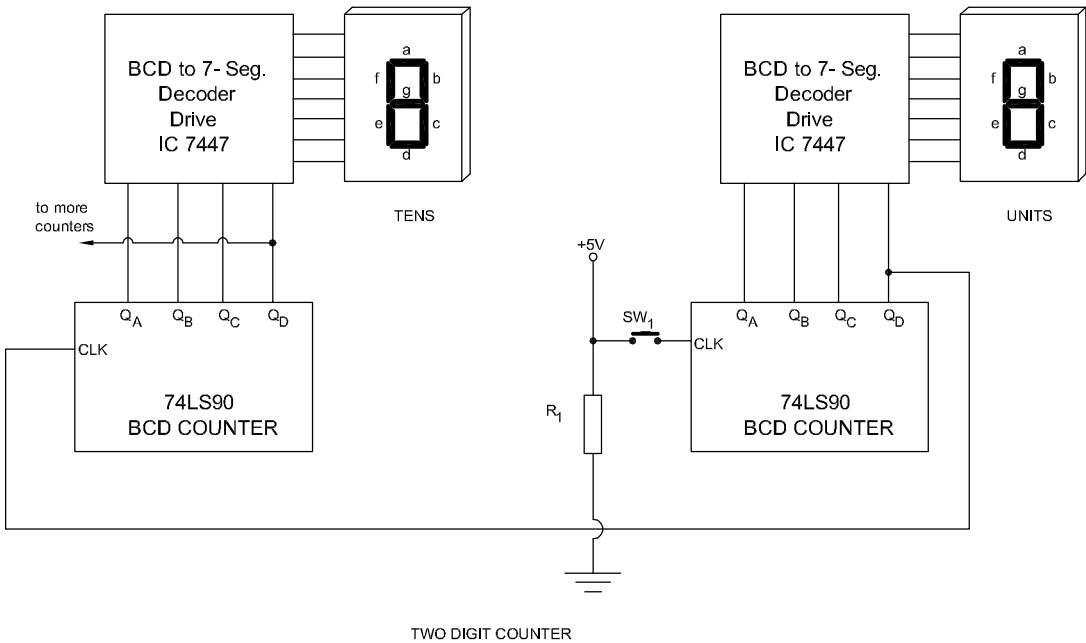

EMN29/6512

Table 2

Clock input	Output of 7490				7-segment display reading	Output of 7447						
	Q _D	Q _C	Q _B	Q _A		a	b	c	d	e	f	g
Reset												
1												
2												
3												
4												
5												
6												
7												
8												
9												
10												

7 Get the work checked by the Instructor.

Construct a shift register using RS/D/JK Flip- Flop and verify the result

Objectives: At the end of this exercise you shall be able to

- construct a shift register RS flip-flop
- construct a shift register D flip-flop
- construct a shift register JK flip-flop.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- DC power supply, 0-30V/2A - 1 No
- Data sheet of the IC used - as reqd
- Digital multimeter with probes - 1 No


Materials/Components

- Hook up wire/connecting wires - as reqd
- Breadboard - 1 No
- IC 74279, IC 74379 - 1 No each
- Miniature toggle switch SPDT - 2 Nos
- LED 5mm, Red - 4 Nos
- Resistor 330Ω/1/4W/CR25 - 4 Nos
- IC 7476 - 4 Nos

PROCEDURE

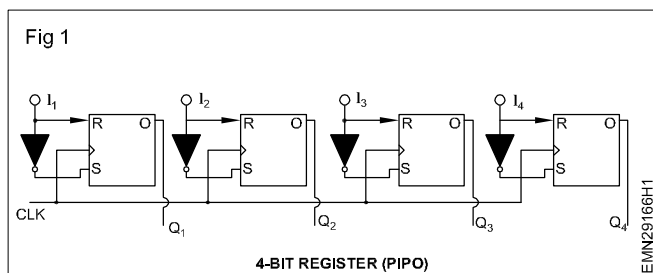TASK 1: Construction of a shift registers using RS Flip-Flop IC 74279

- 1 Collect the components check them and assemble the circuit of a shift register on a breadboard as shown in Fig 1.



- 2 Get the assembled circuit checked by the Instructor.
- 3 Apply logic 0 to clear input (cr), measure and record the output logic level in Table 1.
- 4 Apply logic-1 to clear input (cr). Apply data input of the FF. Input set I_1 , I_2 , I_3 and I_4 at
- 5 Give one clock pulse at the clock input. Record the output logic level in the Table 1.
- 6 Apply logic 0 to serial input. Repeat steps 5.
- 7 Apply logic 1 to serial input and Repeat step 5.

Table 1

Clock	Clear Input	Serial Input	Parallel O/P			
			Q_4 MSB	Q_3	Q_2	Q_1 LSB
X	0	x				
↓	1	1				
↓	1	0				
↓	1	0				
↓	1	1				

- 8 Get the record verified by the Instructor.

TASK 2: Construct a Shift registers using D flip-flop IC 74379

- 1 Refer Fig 2 and assemble the circuit of a shift register on a bread board using IC 74379.

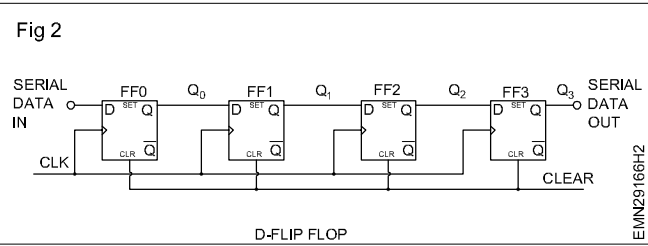


Table 2

CLOCK PULSE	Q3	Q2	Q1	Q0
0	0	0	0	0
1	0	0	0	1
2	0	0	1	1
3	0	1	1	1
4	1	1	1	1
5	1	1	1	0
6	1	1	0	0
7	1	0	0	0

EMN25166H2a

- 2 Get the assembled circuit checked by the Instructor.
- 3 Apply logic-0 to clear input (cr) measure and record the output logic levels in Table 2.
- 4 Give one clock pulse at the clock input. Record the out logic level in the Table 2.
- 5 Apply logic 0 to serial input. Repeat step 4.
- 6 Apply logic 1 to serial input and Repeat step 4 and similarly apply the serial data $(1111)_2$
- 7 Get the recorded readings verified by the Instructor.

TASK 3: Construction of a shift register using JK-Flip-Flop IC-7476

- 1 Refer Fig 3 and wire the circuit of a shift register on a circuit bread board using IC-7476.
- 2 Get the assembled circuit checked by the Instructor.
- 3 Apply logic-0 to clear input(C).Measure and record the output logic levels Q_A , Q_B , Q_C and Q_D in Table 3.
- 4 Apply logic-1 to Clear input (Cr), Apply serial/data input to the circuit.
- 5 Give one clock pulse at the clock input. Record the output logic levels in the Table 3.
- 6 Apply logic-0 to serial input. Repeat step 5 and give the second and third clock pulses.
- 7 Apply $(1001)_2$ as serial input to SIPO register in steps of one bit at time and repeat step-5.

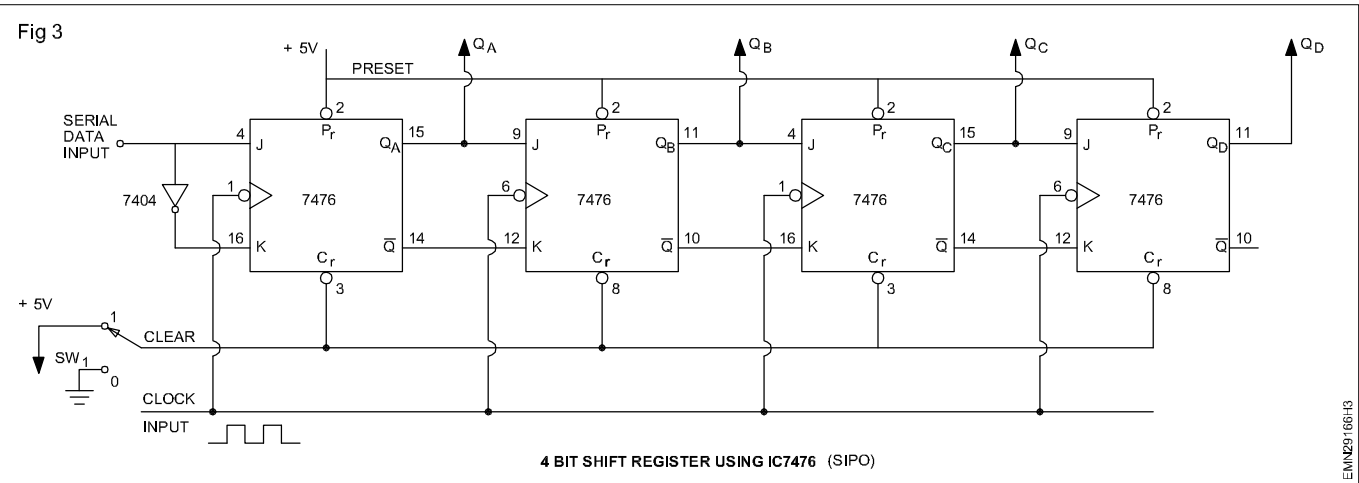


Table 3
4 BIT SHIFT REGISTER USING IC7476
4-bit shift left register using 7476 JK-Flip-Flop

Clock	Clear Input	Serial Input	Parallel O/P			
			Q _D MSB	Q _C	Q _B	Q _A LSB
X	0	x				
↓	1	1				
↓	1	0				
↓	1	0				
↓	1	1				

8 Get the recorded readings verified by the Instructor.

Construct a test four bit SIPO register

Objectives: At the end of this exercise you shall be able to
 • construct and test 4 bit SIPO register using IC 7495.

Requirements

Tools/Equipments/Instruments

- Multimeter with probes - 1 No
- DC power supply, 0-30VDC/2A - 1 No
- Logic probe - 1 No
- Single Shot Pulser - 1 No
- Trainees tool kit - 1 Set

Materials/Components

- Breadboard - 1 No
- IC 7495 miniature toggle - 1 No
- Switch SPDT - 1 No
- Solder Flux - as reqd
- Hookup wires - as reqd
- LED 5mm, Red - 4 Nos
- Resistors 330Ω/¼ W/CR25 - 4 Nos

PROCEDURE


TASK 1 : Construction and testing of 4 bit serial in, parallel out (shift right)

- 1 Collect all the components, check them and assemble the circuit to a serial in, parallel out (SIPO) (shift right) shift register as shown in Fig 1.
- 2 Get the assembled circuit checked by the Instructor.
- 3 Power 'ON' circuit. Apply logic-1 to mode control input and also apply a clock pulse to clock input and record the parallel output logic levels Q_A , Q_B , Q_C and Q_D (should be 0000).

With mode control input at logic '1', parallel inputs $A=B=C=D=0$, results in Q_A , Q_B , Q_C and Q_D equal to 0000.

During shift right, parallel inputs are in don't care condition i.e not necessary to be kept in 0.

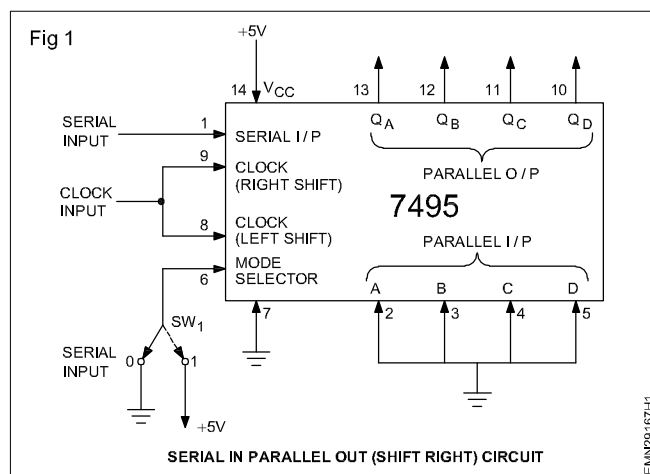- 4 Apply logic-0 to mode control. Apply clock pulse to clock input and serial inputs to circuit as in Table 1. Record the corresponding output logic levels.



- 5 Get the working of the circuit and recorded readings checked by the Instructor.
- 6 Switch OFF the DC supply.

Table 1
Serial in, parallel out (Shift right)

Mode control	Clock Input	Parallel Input				Parallel Output			
		Q_A	Q_B	Q_C	Q_D	Q_A	Q_B	Q_C	Q_D
1	↓	0	0	0	0	0	0	0	0
		Serial Input							
0	↓	1							
0	↓	1							
0	↓	1							
0	↓	1							

Construct and test four bit PIPO register

Objectives: At the end of this exercise you shall be able to

- construct and test a 4 bit shift register using IC 7495.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- DC power supply, 0-30V/2A - 1 No
- Logic probe - 1 No
- Single Shot Pulser - 1 No

Materials/Components

- Breadboard - 1 No
- IC 7495 (4 bit shift register) - 1 No
- Miniature toggle switch SPDT - 5 Nos
- Connecting wires/Hook up wires - as reqd
- LED 5mm, Red - 4 Nos
- Resistor 330Ω/¼ W/CR25 - 1 Nos

PROCEDURE

TASK 1: Construction and testing of a 4-bit shift register using IC-7495 (PIPO)

- 1 Collect the components, check them and assemble the circuit of a 4 bit shift register on a bread board using IC-7495 as shown in Fig 1.
- 2 Get the assembled circuit checked by the Instructor.
- 3 Switch ON main supply and connect RPS. Apply +5V DC to IC-7495.
- 4 Apply logic-1 to mode control input through switch SW₁.
- 5 Apply 1011 as a parallel input data through switches SW₂, SW₃, SW₄ and SW₅. Give clock pulse to clock input by using single shot pulser. Record the output logic levels Q_A, Q_B, Q_C and Q_D in Table 1.
- 6 Repeat step 4 and 5 for different parallel inputs and record corresponding output logic levels in Table 1.
- 7 Get the working of the circuit & recorded readings checked by the Instructor.
- 8 Switch-off the DC supply to the circuit.

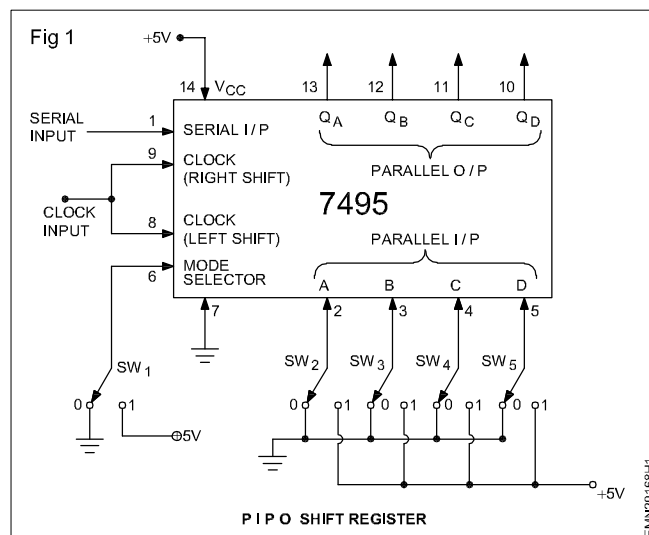


Table 1
4-bit shift register using IC-7495

Mode control	Clock Input	Parallel Input				Parallel Output			
		D	C	B	A	Q _D	Q _C	Q _B	Q _A
1	↓	1	0	0	1				
1	↓	1	0	1	1				
1	↓	1	1	0	1				
1	↓	1	1	1	1				

Construct and test bidirectional shift register

Objectives: At the end of this exercise you shall be able to


- construct and test bidirectional shift register using IC 74194.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
<ul style="list-style-type: none">Trainees tool kitDigital multimeter with probesRegulated DC power supply, 0-30VDC/2AClock pulse generator 1 HzCRO Dual trace 20 MHzData sheet of the IC	- 1 Set	<ul style="list-style-type: none">Miniature toggle switch SPST	- 9 Nos
	- 1 No	<ul style="list-style-type: none">Breadboard	- 1 No
	- 1 No	<ul style="list-style-type: none">I.C 74LS194(bidirectional shift register)	- 1 No
	- 1 No	<ul style="list-style-type: none">LED 5mm, Red	- 4 Nos
	- 1 No	<ul style="list-style-type: none">Resistor 330Ω/¼ W/CR25	- 4 Nos
	- 1 No	<ul style="list-style-type: none">Connecting Hook up wires	- as reqd
	- as reqd		

PROCEDURE

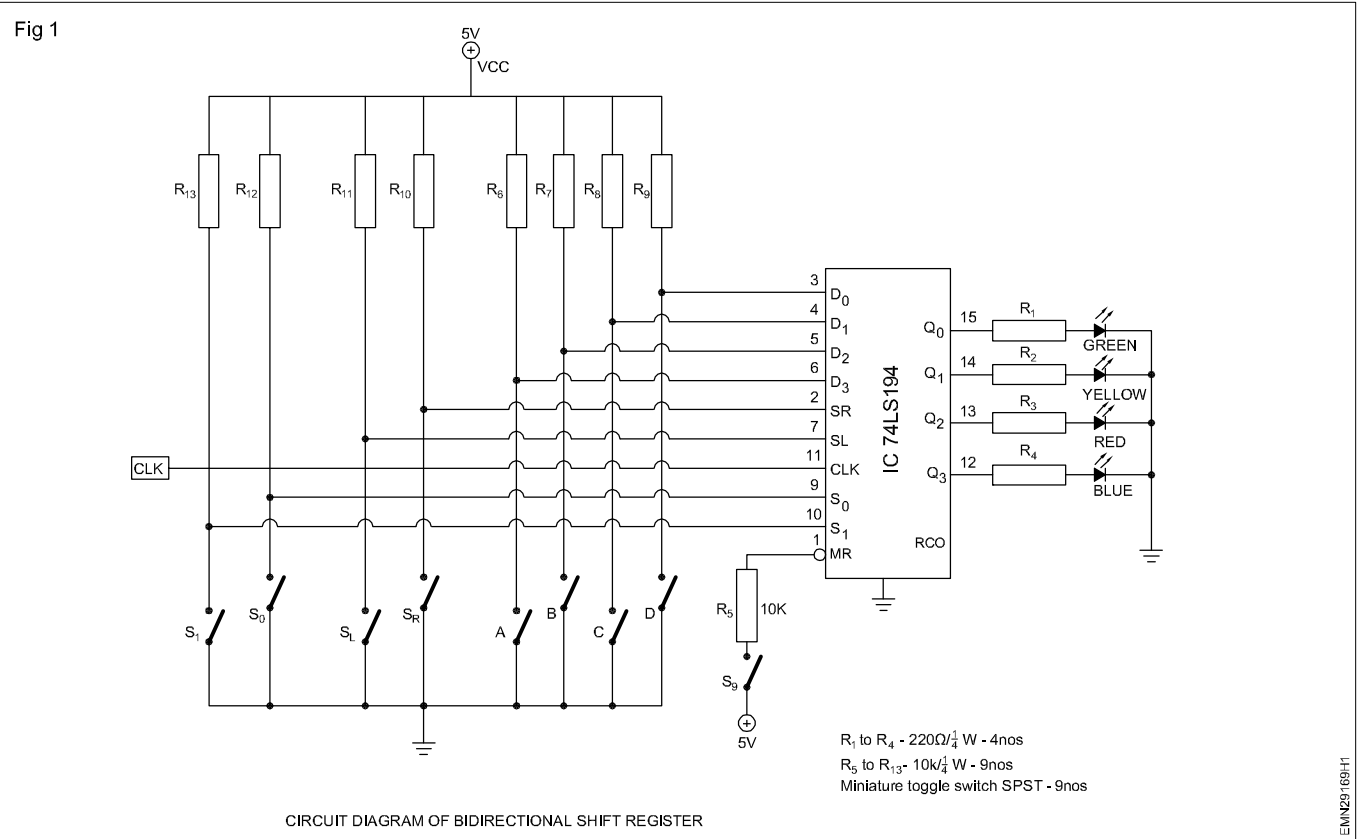TASK 1 : Construction and testing of bidirectional shift register using IC74LS194

- 1 Collect all the components required, test them, refer to the pin out diagram on the data sheet of the IC, assemble the bidirectional shift register circuit as shown in Fig 1 on broad board.
- 2 Use toggle switches for data input pins for A, B, C and D, and also for S₁, S₀, Data Shift Left (DSL), Data Shift Right (DSR) and for Master Reset/Clear pins as shown in Fig 1.



- 3 Get the assembled circuit checked by the Instructor.
- 4 Switch ON 5VDC supply and operate all the switches as per the Truth tables given below for different logic levels either in 5V position or in zero volt (GND) position as shown in the Tables.
- 5 Observe the status of all the LEDs for each step of combinations, record them in the respective tables given.
- 6 Set the switches as per the Truth Table - 1 and observe the LEDs and record in Table - 1

Truth Table 1

MR	S ₁	S ₀	DSR	DSL	CP	D ₀	D ₁	D ₂	D ₃	Q ₀	Q ₁	Q ₂	Q ₃
0	x	x	x	x	x	x	x	x	x	x	x	x	x

- 7 Repeat the steps parallel data loading operation as shown in truth table -2 below and verify the output with clock pulse.

Truth Table 2

MR	S ₁	S ₀	DSR	DSL	CP	D ₀	D ₁	D ₂	D ₃	Q ₀	Q ₁	Q ₂	Q ₃
1	1	1	x	x	CLK	1	1	1	1	1	1	1	1

- 8 Switch DSL input to logic '1' as shown in truth table -3 and observe the shifting of logic '1' to the LEFT, truth table 3.
- 10 Switch DSR input to logic '1' as shown in truth table -5, follow the condition MR=1, S₀=1, S₁=0, DSL=X, DSR=1, observe the outputs for each clock pulse and verify the shift right logic '1'.

Truth Table 3

n clock pulses	Q ₀	Q ₁	Q ₂	Q ₃
0	0	0	0	0
1	0	0	0	1
2	0	0	1	1
3	0	1	1	1
4	1	1	1	1

Truth Table 5

n clock pulses	Q ₀	Q ₁	Q ₂	Q ₃
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1

- 9 Observe the output with each clock pulse and verify. Change the logic input to DSL as logic '0' follow the condition MR=1, S₀=0, S₁=1, DSL=0, DSR=X, observe the outputs as shown in truth table -4 for each clock pulse and verify the shift left logic '0'.
- 11 Change the input to DSR as logic '0' and follow the condition MR=1, S₀=1, S₁=0, DSL=X, DSR=0, as per the truth table -6; observe the outputs for each clock pulse and verify the shift right of logic '0'.

Truth Table 4

n clock pulses	Q ₀	Q ₁	Q ₂	Q ₃
0	1	1	1	1
1	1	1	1	0
2	1	1	0	0
3	1	0	0	0
4	0	0	0	0

Truth Table 6

n clock pulses	Q ₀	Q ₁	Q ₂	Q ₃
0	1	1	1	1
1	0	1	1	1
2	0	0	1	1
3	0	0	0	1
4	0	0	0	0

- 12 Switch S_0 & S_1 to logic '0' follow the condition $MR=1, DSL=0, DSR=0, S_0=X, S_1=X$, observe the outputs for each clock pulse as per the truth table -7 for HOLD operation, and verify the output truth table 7.
- 13 Get the work checked by the instructor.

Truth Table 7

n clock pulses	Q_0	Q_1	Q_2	Q_3
0	Previous data just before S_0 & S_1 both switched to logic '0'			
1				
2				
3				
4				

Use analog IC tester to test various analog ICs

Objectives: At the end of this exercise you shall be able to

- identify various analog ICs with their specifications
- test the analog ICs using analog IC tester.

Requirements			
Tools/Equipments/Instruments		Materials/Components	
• Analog/IC Tester with operating manual	- 1 No	• Assorted analog ICs such as Op-Amp and timer ICs (IC 74, LM 324 IC 555)	- Minimum 3 Nos each
• Semiconductor Data book/manual	- as reqd		

Keep a minimum of 10 nos of assorted labeled ICs on a table at two places and instruct the trainees to pick one IC at a time to carry out the testing work. Instructor should demonstrate the operation of IC tester available in the laboratory. A typical IC tester is shown in Fig 1.

PROCEDURE

TASK 1 : Identification of various Analog ICs with their specifications and pin diagram

- Pick one of the labeled IC from the assorted lot and record its product code /label number printed on the body.
 - Minimum output current $I_{out(min)}$
 - Slew rate of the IC
 - Any other parameter applicable to this IC
 - Typical applications.
- Refer to the data sheet semiconductor international data book for Op-Amp / Timer (which ever applicable) and record the following specifications of the given IC;
 - Type of package
 - Manufacturers name
 - Number of OP-Amps/timers in the IC
 - Rated maximum DC supply voltage
 - Open-loop gain A_{VOL}
- Count the number of pins in the given IC. Make a rough sketch of the IC. Identify and record the pin numbers.
- Repeat the steps for atleast four different ICs having different product code.

Table 1

Sl.No.	Label No.	IC Number	Manufacturer name	$V_{cc\ max}$	A_{VOL}	$I_{OUT\ (min)}$	Application	Pin diagram

- Get the work checked by the Instructor.

TASK 2 : Testing of the given Op- Amp and Timer IC with Analog IC Tester

IC Tester has self test button. On pressing it, The IC tester performs self Diagnostic test its own hardware. It has two modes of operations

- 1 Quick test - To test and give result immediately.
- 2 Stepwise test - To know which portion of hardware in IC has failed. In this method, even if one AMP in a dual Op- Amp IC is GOOD that IC can be used.

- 1 Refer to the instruction operation manual of IC tester, familiar with operation of analog/universal IC tester available in laboratory.

Use operator manual note down the library of analog ICs of the tester to know which ICs may be tested with the tester as shown in Fig 1.

Fig 1



Analog IC Tester

- 2 Pick one of the labelled IC, identify the pin no. 1, orient it/as per the ZIF socket position.
- 3 Open the level of the ZIF socket and insert the IC into position carefully.

Note: ZIF socket refers to Zero Insertion Force. It is a type of socket for mounting electronic devices that is designed not to stress or damage them during Insertion.

- 4 Switch on the power switch of IC tester enter the IC number on the keypad of the IC tester and press TEST key and see the result.

Note: The IC tester comprises of programs /set of testing procedure to test every analog IC available in its library. it checks the procedures of various steps and produces the result as GOOD or BAD on the display provided in it.

- 5 Find out whether the given IC is GOOD (or) BAD by observing the display of the IC tester and record the result in Table 2.
- 6 Repeat the exercise for at least 3 Op-Amps and 3 Timer IC to show the difference between good and defective and record in Table 2.

Table 2

Sl.No.	IC No. test	Mode	Condition of IC

- 7 Get the work checked by the Instructor.

Construct and test various Op-Amp circuits Inverting, Non-inverting, Summing Amplifiers

Objectives : At the end of this exercise you shall be able to

- construct and test Inverting amplifier using LM 324
- construct and test Non-Inverting amplifier using LM 324
- construct and test summing amplifier and differential amplifier using LM 324.

Requirements

Tools/Equipments/Instruments

- Analog/Universal IC Tester with instruction manual - 1 No
- CRO, 20 MHz Dual trace - 2 Nos
- Semiconductor Data book - 1 No
- Analog/Digital multimeter with probes - 1 No
- Dual regulated DC power supply 0-30V/2A - 1 No
- Function generator - 1 No
- Trainees tool kit - 1 Set

Materials/Components

- Op-Amp ICs LM324, UA741 - 2 Nos each
- Breadboard - 2 Nos each
- Resistors 10 k Ω , 1/4 W/CR25 - 7 Nos
- 100 k Ω , 1/4 W/CR25 - 1 No
- Hook up wires/connecting wires - as reqd
- IC base (8 pin), DIP - 2 Nos
- Diodes 1N4001 - 4 Nos


PROCEDURE

TASK 1 : Construction and testing of an inverting amplifier

- 1 Collect all the required components from the instructor and check them with multimeter; use IC tester for checking ICs.
- 2 Identify the type of package and pins of the given Op-Amp using Data book.
- 3 Refer to circuit diagram shown in Fig 1 and assemble the inverting amplifier circuit on bread board.
- 4 Get the assembled circuit checked by the Instructor.

Always keep an IC base fixed on the breadboard for inserting the Op-Amp IC.

- 5 Connect +12V, -12V and GND of dual DC power supply to pin 4, pin 11 and GND respectively.
- 6 Prepare the CRO for measurements and apply 0.2V_{p-p} at the input.
- 7 Measure the output using DMM and CRO.
- 8 Vary the input voltage and observe the output variations using multimeter and oscilloscope; record the observation in Table 1.
- 9 Change the value of feedback resistor R_F and R_{in} observe the variation in gain and record them in Table.
- 8 Get the completed work checked by the Instructor.

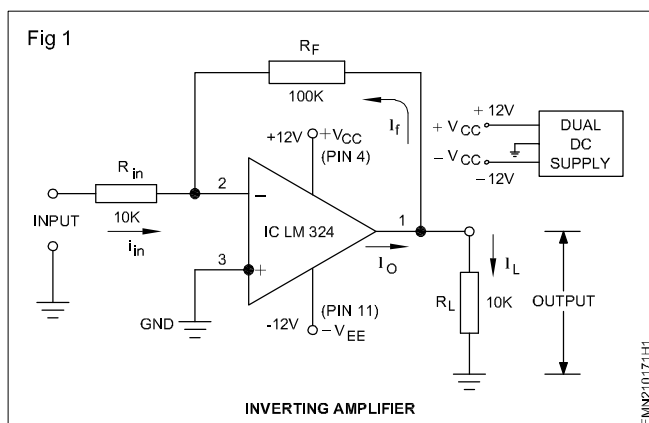

TASK 2 : Construction and testing of a non-inverting amplifier using IC LM324

- 1 Refer to the circuit diagram shown in Fig 2 and modify the assembled circuit on Bread board.
- 2 Get the assembled circuit checked by the Instructor.
- 3 Repeat steps 5 to 8 of Task 1 and record the observations.
- 4 Repeat the steps 9, record the observations and calculate the gain and record them.

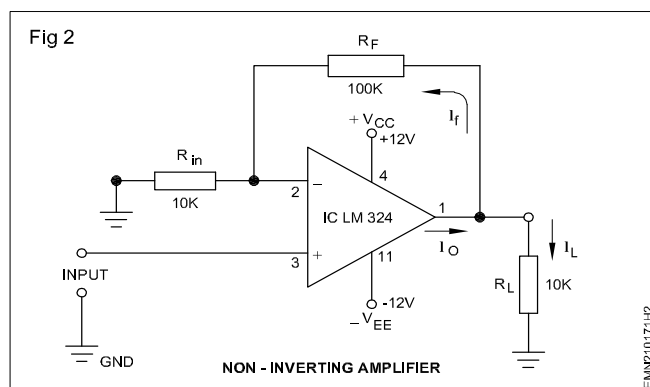


Table 1

S.No.	Input voltage applied (V_i)	Output voltage		Gain normal observed values V_{out} / V_{in}		Gain x V_{in} = Volt Calculate values	
		Inverting amplifier	Non inverting amplifier	Inverting amplifier	Non inverting amplifier	Inverting amplifier (R_f/R_{in}) x V_{in}	Non inverting ($1+(R_f/R_{in})$)x V_{in}
1	0.2V						
2	0.4V						
3	0.6V						

- 5 Get the work checked by the Instructor.

TASK 3 : Construction and testing of a summing amplifier using IC LM324

Carry out the experiment on a Bread board. The suitable values for input voltage are kept such that.

$$\frac{R_F}{R_1} = \frac{R_F}{R_2} = \frac{R_F}{R_3} = \frac{R_f}{R_{in}}$$

- 1 Collect all the required items, check the components and assemble the circuit according to the amplifier circuit shown in Fig 3.


Note the inputs have been applied to inverting terminal.

- 2 Get the assembled circuit checked by the instructor.
- 3 Switch ON the dual DC power supply measure the output using multimeter and CRO.

Use the given formula to calculate the output voltage for summing amplifier.

- 4 Verify the results obtained & compare with the calculated values.

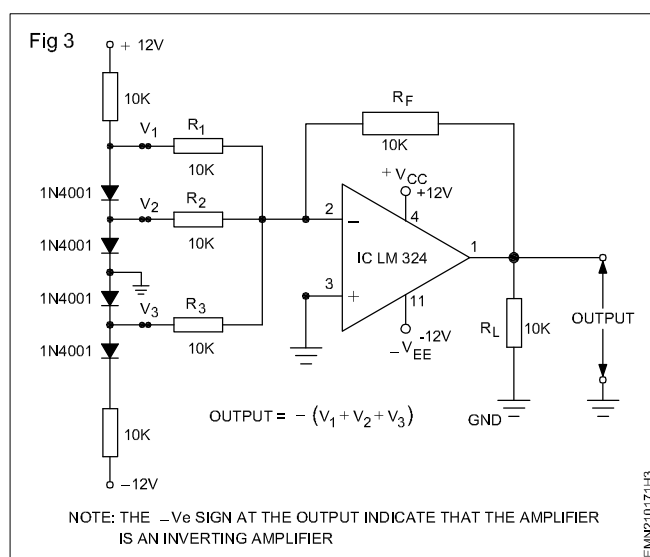To apply inputs to noninverting terminal exchange the inputs applied on inverting and non inverting terminals.



Observation table

Table 2

S.No.	Configuration	Output voltage	Result
1	When inputs V_1 , V_2 & V_3 have been applied on -Ve terminal	$V_o =$	Is O/P proportional to sum of inputs? (Yes / No)
2	When input V_1 , V_2 & V_3 have been applied on +Ve terminal	$V_o =$	Is output proportional to sum of inputs? (Yes / No)

Formula to calculate output voltage of summing amplifier

i For Inverting Amplifier

$$V_o = - \left(\left(\frac{R_f}{R_{in}} \times V_1 \right) + \left(\frac{R_f}{R_{in}} \times V_2 \right) + \left(\frac{R_f}{R_{in}} \times V_3 \right) \right) = \frac{R_f}{R_{in}} (V_1 + V_2 + V_3)$$

ii For Non-Inverting Amplifier

$$V_o = \left(\left(1 + \frac{R_f}{R_{in}} \right) V_1 + \left(1 + \frac{R_f}{R_{in}} \right) V_2 + \left(1 + \frac{R_f}{R_{in}} \right) V_3 \right) = \left(1 + \frac{R_f}{R_{in}} \right) (V_1 + V_2 + V_3)$$

If $R_f = R_{in}$

$$V_o = 2 (V_1 + V_2 + V_3)$$

TASK 4 : Construction and testing of Differential Amplifier using LM324

- 1 Modify the components values and assemble the circuit shown in Fig 4.
- 2 Get the assembled circuit checked by the instructor.

- 6 Compare the calculated value with observed.
- 7 Get the work checked by the Instructor.


Note: A $R_{f1} = R_{f2} = R_f$ and $R_1 = R_2 = R_{in}$

$$V_o \text{ Output} = (V_2 - V_1) \frac{R_f}{R_{in}}$$

Observation table

Table 3

Input to Differential Amplifier		Output to (V_o) calculated	Output Observed (V_o)
V_1	V_2		
0.5V	1V		
+1V	-2V		
-2V	+2.5V		

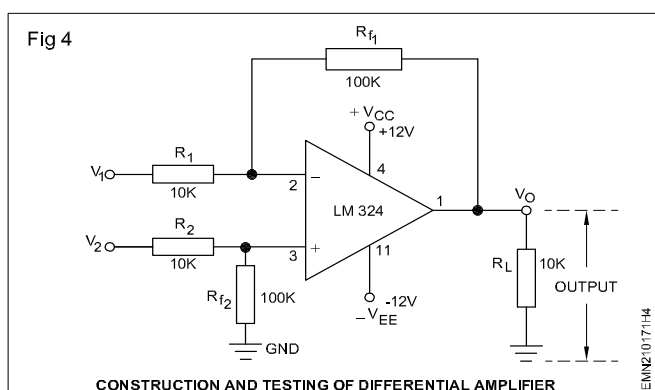

- 3 Repeat step 5 of Task 1.
- 4 Apply the DC inputs to the differential amplifier circuit at pin 2 and pin 3 through 10k resistors as per the Table 3.
- 4 Measure the output using Multimeter and record in given table.
- 5 Change the input values at V1 and V2 and record the output readings in Table 3.

Construct and test Differentiator and integrator


Objectives : At the end of this exercise you shall be able to

- construct and test differentiator circuit using Op-Amp IC 741
- construct and test integrator circuit using Op-Amp IC 741.


Requirement	
Tools/Equipments/Instruments/ Data Book	Materials/Components
<ul style="list-style-type: none"> • Trainees tool kit - 1 Set • CRO 20MHz dual trace - 1 No • Digital multimeter with probes - 1 No • Voltmeter 0-10V - 1 No • Regulated dual DC power supply 0-30V/2A - 1 No • Function generator - 1 No 	<ul style="list-style-type: none"> • Resistors 1kΩ, 10kΩ, 4.7kΩ ¼ W/CR25 - each 1 No • IC 741 Op-Amp - 1 No • Capacitor 0.1 μF/25V - 1 No • Hook up wire - as reqd • Breadboard - 1 No • Graph sheet (Linear) - 1 No

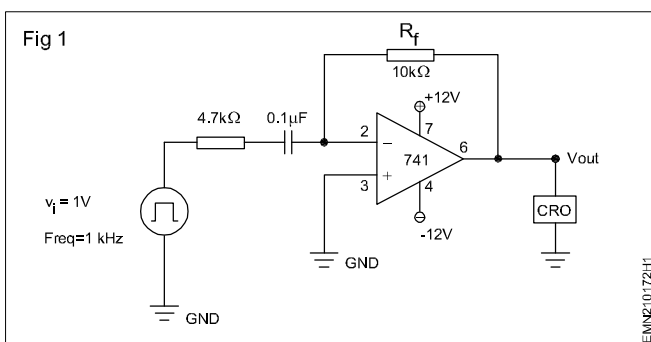TASK 1 : Construction and testing of a differentiator circuit

- 1 Collect and check the components for the good working condition and assemble the circuit on the bread board as shown in Fig 1.



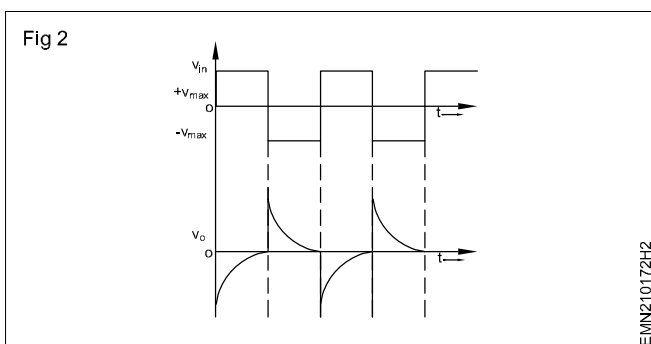- 2 Get the assembled circuit checked by the Instructor. Calculate RC time constant ($T = R_f C$).




- 3 Give a square wave input of 1 V_{p-p} to the inverting terminal and set the frequency to 1/T in the function generator.
- 4 Switch ON the dual power supply and set it to +12V and -12V and GND as shown in Fig 1.

Note: For a differentiator,


$$V_O = R_f C \frac{d(V_{in}(t))}{dt}$$

- 5 Prepare the CRO for measurement and observe the output waveform on the CRO.
- 6 Vary the frequency to 1/10T and observe the waveform.
- 7 Vary the frequency to 1/0.1T and observe the waveform.
- 8 Draw output and input waveform of the circuit as shown in 2 on a graph sheet for all the 3 steps.
- 9 Repeat the above procedure for different input signals viz. triangular waveform and sinwave waveform as shown in Fig 3.

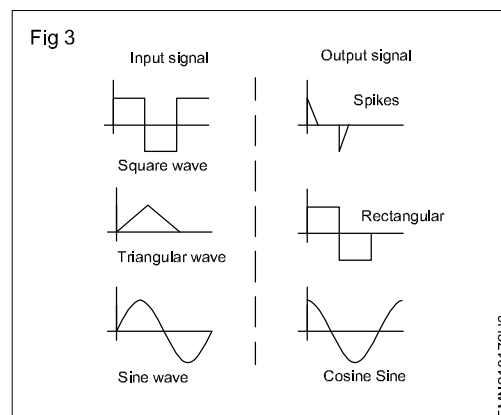

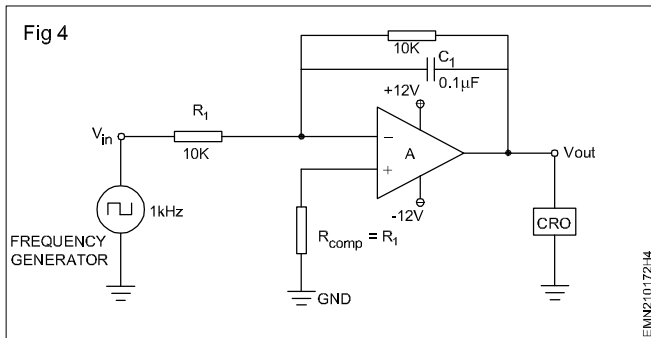TASK 2 : Construction and testing of a integrator circuit

- 1 Check the components for their good working condition and connect the circuit on the bread board as shown in the Fig 4.




- 2 Calculate RC time constant($T=R_1C$).
- 3 Apply a non sinusoidal input of 1 V_{p-p} to the inverting terminal and set the frequency to $1/T$ in the function generator.

Note: For a Integrator:

$$V_O = - \frac{1}{R_1 C_1} \int V_{in} dt$$

- 4 Switch ON the dual power supply and set it to +12V, -12V and GND connections.
- 5 Observe the output waveform on the CRO.
- 6 Vary the frequency to $1/10T$ and observe the waveform.
- 7 Vary the frequency to $1/0.1T$ and observe the waveform.
- 8 Draw output and input waveform of the circuit as shown in Fig 5, on a graph sheet for all the 3 steps.
- 9 Repeat the same procedure for different input signals viz. square wave, triangular waveform.

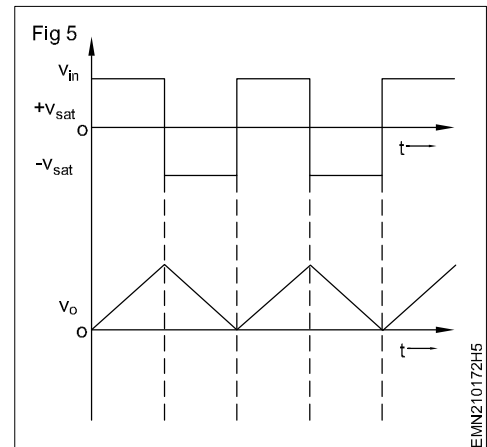

- 10 Get the result checked by the Instructor.

Construct and test a zero crossing detector

Objectives : At the end of this exercise you shall be able to

- verify the operation of a zero crossing detector circuit using Op-Amp IC741.

Requirement			
Tools/Equipments/Instruments/ Data Book		Materials/Components	
• CRO Dual trace 0-20 MHz	- 1 No	• Breadboard	- 1 No
• Signal Generator	- 1 No	• IC 741	- 1 No
• Regulated dual DC power supply 0-30V/2A	- 1 No	• Diode 1N4007	- 2 Nos
• Trainees tool kit	- 1 Set	• Resistor 1kΩ, ¼ W/CR25	- 3 Nos


PROCEDURE

TASK 1: Construction and testing of Zero crossing detectors using Op-Amp IC741

- 1 Collect all the materials check the working condition using the multimeter and assemble the circuit as shown in Fig 1 on bread board.

Check the IC using the IC tester.

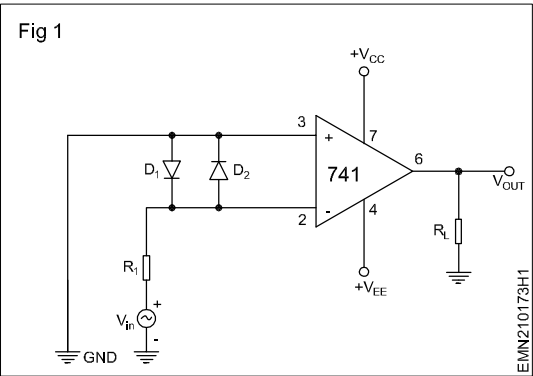- 2 Connect the reference Input to zero crossing detector, pin no 3 to GND.
- 3 Get the assembled circuit checked by the Instructor.





- 4 Connect the input sinewave signal, obtained from a Function generator, at 1 kHz/1 V_{p-p}.
- 5 Prepare the CRO for measurements and connect the input and output to dual channel CRO, and compare the input and output wave forms with Fig 2 and record the observations in Table 1.
- 6 Get the work checked by the Instructor.

Observation Table

Table 1

Parameter	Waveform	Time
Input - Voltage (V _{in}) = _____		
Output - Voltage (V _{out}) = _____		

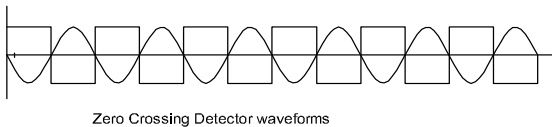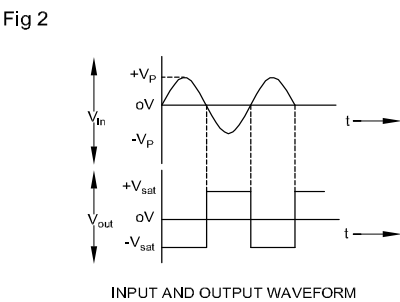

Note: Instructor may guide the trainees to note that output waveform changes state, whenever the input sinewave signal crosses the zero level. The circuit works as an Inverting Comparator.

Construct and test instrumentation amplifier

Objectives : At the end of this exercise you shall be able to

- construct and test Instrumentation amplifier circuit using IC LM324.

Requirement

Tools/Equipments/Instruments/Data Book

- Function generator - 1 No
- CRO dual trace 20MHz - 1 No
- Dual regulated DC power supply 0-30V/2A - 1 No
- Trainees tool kit - 1Set
- Digital multimeter with probes - 1 No
- Data sheet of the IC LM324 - as reqd


Materials/Components

- Resistors ¼ W/CR25
1kΩ - 4 Nos
- 100kΩ - 4 Nos
- 1kΩ POT - 1 No
- IC LM324 - 1 No
- Breadboard - 1 set

PROCEUDRE

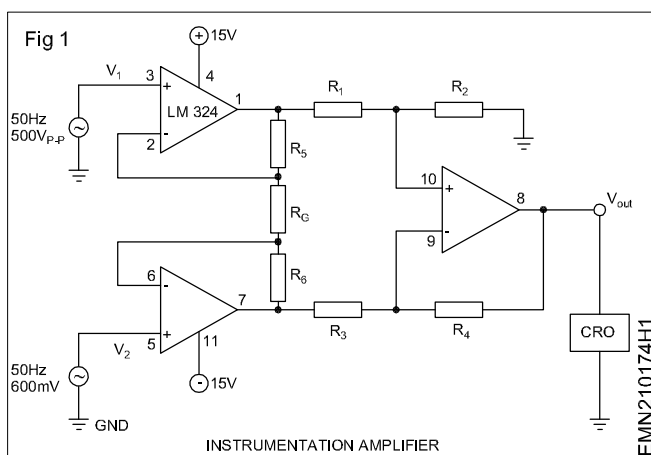TASK 1 : Construction and testing of an Instrumentation amplifier circuit

- 1 Collect all the components, test them and refer to the pin out diagram of the IC and assemble the circuit as per the circuit diagram shown in Fig 1.



- 2 Get the assembled circuit checked by the Instructor.
- 3 Set the inputs V_1 and V_2 at different values but at the same frequency.
- 4 Switch ON the dual power supply and set the voltage + 15V, -15V and GND.
- 5 Prepare the CRO for measurements and measure the output at the output pin.
- 6 Calculate the theoretical gain from the given formula and verify the practical values.

Formula

$$\text{Voltage gain } A_v = \frac{V_o}{V_2 - V_1} = \left(1 + \frac{2R_1}{R_{\text{gain}}}\right) \times \left(\frac{R_3}{R_2}\right)$$

Table

Sl.No.	Applied input voltage	Voltage gain AV	Output voltage calculated (V_o)	Result Observed Output ' V_o '
1	$V_1 =$ $V_2 =$	$V_o =$		

- 7 Get the work checked by the Instructor.

Construct and test a Binary weighted and R-2R Ladder type Digital- to- Analog converters

Objectives: At the end of this exercise you shall be able to

- assemble and test a digital to analog converter using R-2R ladder network using Op-Amp.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Regulated dual DC power supply 0-30V/2A - 1 No
- DC power supply 15V/500 mA - 1 No
- Digital multimeter with probe - 1 No

Materials/Components

- ICLM741 - 1 No
- Data sheet of the ICs used - as reqd
- Resistor, carbon film 10 kΩ/¼ W/CR25 - 16 Nos
- Breadboard - 1 No
- IC Base 8 pin - 1 No
- Hook up wire - as reqd
- Miniature toggle switch SPDT - 4 Nos

PROCEDURE

TASK 1: Construct and test D to A converter using R-2R ladder network

- 1 Collect all the components, check them; Refer Fig 1 and assemble the op-amp circuit using IC741 with 8 pin IC base on bread board.
- 2 Get the assembled circuit checked by the Instructor.
- 3 Connect the dual DC power supply +15, -15V and GND terminals to the IC741 referring to Fig 1.

- 8 Repeat step 7 for different binary input combinations.
- 9 Calculate the theoretical V_o by using the formula for different binary input combinations and record the same in Table 1.

Formula for theoretical output V_o

$$V_o = \frac{D_0 \cdot 2^0 + D_1 \cdot 2^1 + D_2 \cdot 2^2 + D_3 \cdot 2^3}{2^3}$$

Digital Input = logic 0/logic 1

Note: For (eg) If the 4 bit binary inputs are [D0 D1 D2 D3 - Decimal values = 7.

The equivalent analog value of the D to A converter can be calculated as follows:

As logic - 2 refer to 5V, $V_{ref} = 5V$ in the circuit.

For the binary inputs 1110, the input voltage x at pin 2 of Op - Amps, is

$$V_x = [(2^0 \times 1) + (2^1 \times 1) + (2^2 \times 1) + (2^3 \times 0)]$$


$$\text{Analog} = \frac{1}{16} (7) = \left(\frac{7}{16} \right)$$

$$\text{O/P } V_o = \frac{7}{16} \times 5V$$

For binary Input $(-1111)_2$

Analog output will = -5V

(-1 is the inverting amplifier gain).

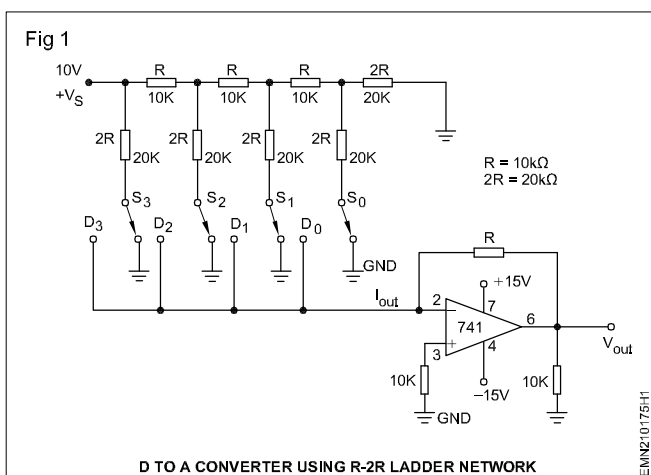

- 4 Assemble the remaining part of R-2R ladder network on bread board ensuring four terminal connections D_0 to D_3 which are digital inputs.
- 5 Use the toggle switches S_0 to S_3 and operate them to provide logic levels low (GND) and high (1) as per the Table 1.
- 6 Get the work checked by the Instructor.
- 7 Apply binary logic inputs at D_0 to D_3 as per Table 1, measure voltage at the output of the Op-Amp and record them in Table.

Table 1

Decimal Value of Input	4-bit Digital Input				V _o Calculated	V _o Measured
	D ₃	D ₂	D ₁	D ₀		
0	0	0	0	0		
1	0	0	0	1		
2	0	0	1	0		
3	0	0	1	1		
4	0	1	0	0		
5	0	1	0	1		
6	0	1	1	0		
7	0	1	1	1		
8	1	0	0	0		

10 Get the work checked by the Instructor.

Construct and test Astable multivibrator circuit using IC 555

Objectives: At the end of this exercise you shall be able to

- assemble and test an astable multivibrator circuit using IC 555
- measure pulse repetition frequency (PRF), rise time and fall time of the pulses.

Requirements

Tools/Equipments/Instruments

- Regulated DC power supply 0-30/2A - 1 No
- Trainees tool kit - 1 Set
- CRO 20MHz, Dual trace - 1 No
- Digital multimeter with probes - 1 No

Materials/Components

- Bread board - 1 No
- IC base, 8 pin DIL - 1 No
- IC 555 - 1 No

- Carbon resistors, ¼ W/CR25
 - 1k Ω - 1 No
 - 10k preset - 1 No
- Preset, 10k Ω - 1 No
- Capacitors
 - 0.01 μ F/25V - 1 No
 - 0.1 μ F/25V - 1 No
 - 4.7 μ F/25V - 1 No
- Speaker, 8 Ω , 2" or any small speaker (used in pocket radios) - 1 No
- LED 5mm, Red - 1 No
- Hook up wires - as reqd


PROCEDURE

TASK 1 : Construction and testing of an astable Multivibrator using IC 555

- 1 Collect all the required components, check them and assemble the astable multivibrator circuit on breadboard as shown in Fig 1.
- 2 Get the assembled circuit checked by the Instructor.
- 5 Prepare the CRO for measurements.
- 6 Switch ON DC voltage to the circuit and check for continuous rectangular pulses at the output of the circuit using the CRO.


If there is no output, switch off the voltage to the circuit and check the circuit connections. Take the help of the Instructor, if necessary.

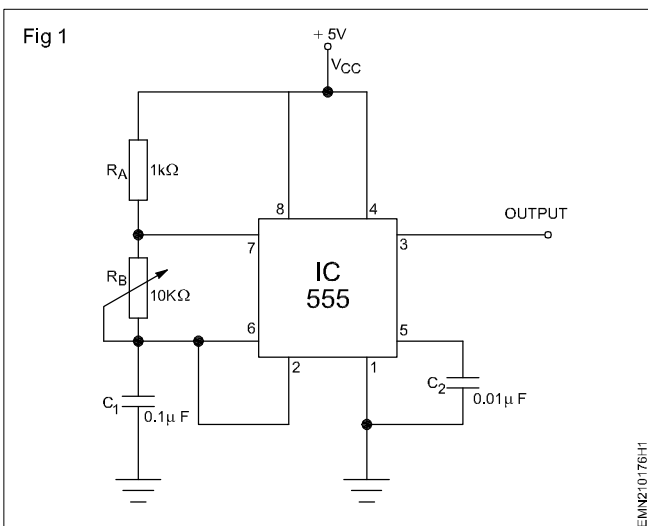- 7 Measure and record the ON-time, OFF-time and PRF (pulse repetition frequency) of the output pulses.
- 8 Measure and record the rise-time and fall-time of the pulses as shown in Fig 2.




Place and fix the IC in the IC socket ensuring that the IC pins do not get bent or come out of the IC base.

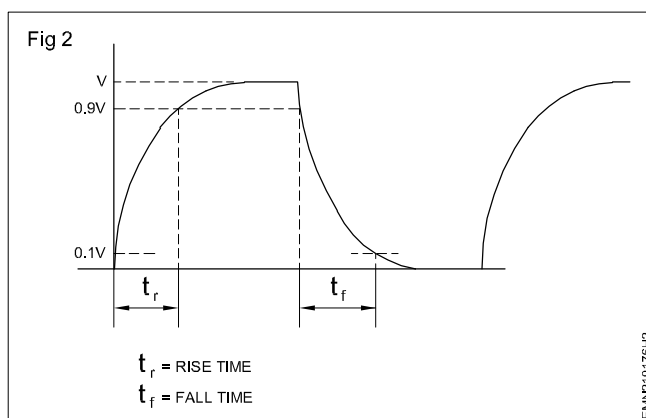- 3 From the values of the circuit components, calculate and record the ON-time(t_{ON}), OFF-time(t_{OFF}) and the pulse repetition frequency(PRF) of output.
- 4 Get the calculated values checked by the instructor.



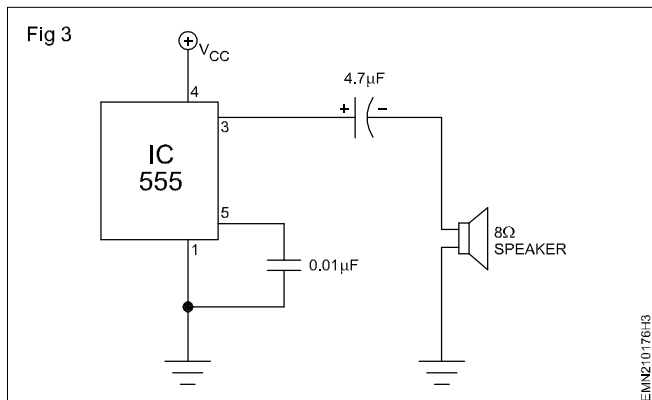- 9 Connect a capacitor 4.7μF and a 8Ω, 2 inch speaker at the output in series with a capacitor as shown in Fig 3.



- 10 Switch ON the DC supply and listen to the audible sound from the speaker. Change the position of the preset 'RB' and check for changed frequency output from the speaker.
- 11 Measure and record output frequencies and duty cycle at four different positions of preset.
- 12 Get the working of astable multivibrator circuit and the recorded readings checked by the Instructor.

Note:

The frequency (or) PRF of Astable multivibrator is:

- $f = \frac{1.44}{(R + 2RB)C}$
- $t_{OFF} = 0.693 \times RB \times C$
- $t_{ON} = 0.693 (RA + RB) C$
- $D = \text{Duty Cycle} = \frac{(RA + RB)}{(RA + 2RB)}$

- 1 (a) Measured ON-time (t_{ON}) : _____
- (b) Measured OFF-time (t_{OFF}) : _____
- (c) Measured pulse repetition frequency (PRF) : _____
- (d) Duty cycle : _____
- 2 Rise time of pulse (Observed) : _____
- 3 Fall time of pulse (Observed) : _____
- 4 (a) Audible output heard from speaker : YES/NO
- (b) Frequency/pitch of audible output from speaker varies with position of preset : YES/NO

Table 1

Resistance of preset RB	Output Frequency	Waveform on CRO

Construct and test Monostable multivibrator circuit using IC 555

Objective : At the end of this exercise you shall be able to

- assemble and test a monostable multivibrator using IC 555.
- use the monostable multivibrator as a touch switch.

Requirements

Tools/Equipments/Instruments

- Digital multimeter with probes - 1 No
- Trainees tool kit - 1 Set
- Storage oscilloscope/CRO-0-20 MHz dual trace - 1 No
- Regulated DC power supply 0-30V/2A - 1 No

Materials/Components


- Breadboard - 1 No
- 8-pin IC base - 1 No
- IC 555 - 1 No

- Carbon resistors, 1/4 watt
 - 10 M Ω - 1 No
 - 33 k Ω 330 Ω , 1M Ω - 1 No
- Capacitors 25VDC
 - 0.01 μ F - 1 No each
 - 4.7 μ F - 2 Nos
- LED 5mm, Red - 1 No
- Push-button switch (Push-to-ON) - 1 No
- Hook up wires - as reqd

PROCEDURE

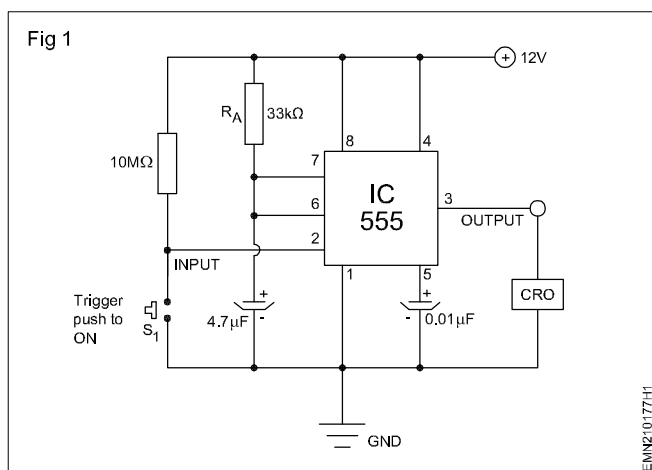TASK 1 : Construction and testing of Monostable multivibrator circuit using IC 555

- 1 Collect all the materials required and check them.
- 2 Assemble the monostable multivibrator on breadboard referring to the circuit diagram shown in Fig 1.



- 3 Get the assembled circuit checked by the instructor.
- 4 Switch ON the 12VDC supply to the circuit.
- 5 Prepare the CRO for measurements and connect the CRO at the output of the monostable multivibrator.

- 6 Press the push-button(trigger signal) and observe the output pulse on the CRO.
- 7 Keep pressing and releasing the trigger button and measure the ON-time(t_{ON}) of the output pulse. Record the reading in Table 1&2.

If the CRO has a storage option, use it to measure the pulse width conveniently. Take the help of the instructor to use the storage option.

- 8 Connect the CRO probe at pin No. 2 of the IC; keep pressing and releasing the trigger button and observe the trigger input waveform on the CRO. Sketch the observed waveform in the space provided in the Table 2.
- 9 Change the value R_A from 33 K Ω to 1 M Ω . Connect the LED with a 330 Ω resistor in series at the output pin 3 to GND.
- 10 Switch ON DC supply to the circuit; press the push-button (trigger) and observe the LED glow for a few seconds and turn OFF again. Record your observation.

Table 1

S.No.	R_A	C	Time	
			Calculated $T=1.11 \times R_A C$	Measured
1	33k Ω	4.7 μ F		
2	1M Ω	4.7 μ F		

Table 2

Wave form at Trigger Input Pin -2	Wave form at Output Pin-3

11 Get the work checked by the Instructor.

TASK 2 : Construction and testing of Monostable multivibrator as a touch switch

- 1 Remove the push-button switch connected at pin No.2 of the IC. Connect a wire of about 0.5 metres skinned at both ends at pin No. 2 of IC.
- 2 Switch ON DC supply to the circuit. Touch once, the free end of the wire by your fingers and observe the LED glow. Repeat this step a few more times and record your observation.

The circuit is now working as a touch-switch.

- 3 Get the working of the touch-switch checked by the Instructor.

Construct and test VCO (V to F converter) using IC 555

Objectives : At the end of this exercise you shall be able to
• construct and test VCO circuit using IC 555.

Requirements

Tools/Equipments/Instruments

- Trainees tool kit - 1 Set
- Digital multimeter with probes - 1 No
- Regulated DC power supply 0-30V/2A - 1 No


Materials/Components

- Bread board - 1 No
- Resistor 100k Ω , 1k Ω , 220 Ω 1/4 W/CR25 - 1 No each
- IC 555 - 1 No
- Capacitor 0.01 μ F/25V - 1 No
- Loud speaker 8 Ω /1W - 1 No
- Hookup wire - as reqd
- 10k Linear potentiometer - 1 No

PROCEDURE

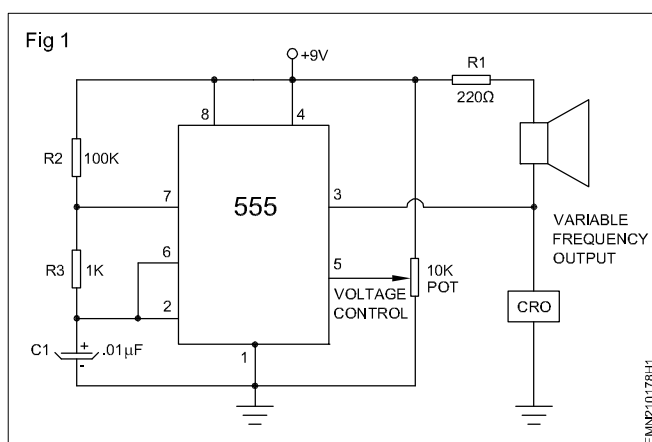TASK 1 : Construction and testing of VCO circuit using IC 555

- 1 Collect all the materials required for the circuit diagram shown in the Fig 1 and check them for their working condition using multimeter.



- 2 Assemble the components on breadboard according to the circuit shown in Fig 1.
- 3 Get the assembled circuit checked by the Instructor.
- 4 Switch ON 9V DC supply to the circuit from the Regulated DC power supply.
- 5 Prepare the CRO for measurement, and observe the waveform at pin no.3.

- 6 Adjust the DC control voltage at pin no. 5 and observe the sound and measure the effect on the output of the circuit.

This observation, conclude that the output of the circuit (i.e the frequency of astable multivibrator) varies on varying the control voltage at pin no. 5 then the circuit behaves as voltage controlled oscillator.

- 7 Change the DC control voltage settings as per the table and record the readings in Table 1.

Table 1

Sl.No.	Input Voltage	CRO readings
1	1.5V	
2	3V	
3	4.5V	
4	7.5V	

- 8 Get the work checked by the Instructor.

Construct and test 555 timers as pulse width modulator

Objective: At the end of this exercise you shall be able to

- construct and test a PWM circuit using IC555 to generate pulse width modulated output.

Requirements

Tools/Equipments/Instruments/Data Book

- Trainees tool kit - 1 Set
- Digital multimeter with probes - 1 No
- Regulated DC power supply 0-30V/2A - 1 No
- Function generator - 1 No
- AF signal generator - 1 No

Materials/Components

- Breadboard - 1 No
- IC 555 - 1 No
- IC Base-8 pin - 1 No
- Diode 1N4001 - 1 No

- Resistor
15k Ω , carbon, $\frac{1}{4}$ W - 1 No
10k Ω , carbon, $\frac{1}{4}$ W - 1 No
5.6k Ω , carbon, $\frac{1}{4}$ W - 1 No
- Capacitors 25V DC
0.1 μ F, ceramic disc - 2 Nos
10 μ F - 1 No
- LED 5mm, Red - 1 No
- Push-button switch (Push-to-ON) - 1 No
- Hook up wires - as reqd


PROCEDURE

TASK 1 : Construction and testing of PWM circuit using IC 555

- 1 Collect all the materials required identify the components as per the circuit diagram. Ensure working condition of the components by using multimeter and IC tester.
- 2 Assemble the PWM control circuit using IC 555 as shown in Fig 1.
- 3 Switch ON 12V DC power supply.
- 4 Connect the square wave input as carrier, from function generator. Set the waveform to the required duty cycle and AF signal as message.
- 5 Observe the output LED at pin 3 and the brightness of the LED.
- 6 Prepare the CRO for measurement and observe the out waveform verify PWM frequency and duty cycle; record the waveform in Table 1.

Table 1

Function Generator frequency	A.F. Generator frequency	Output waveform	Remarks

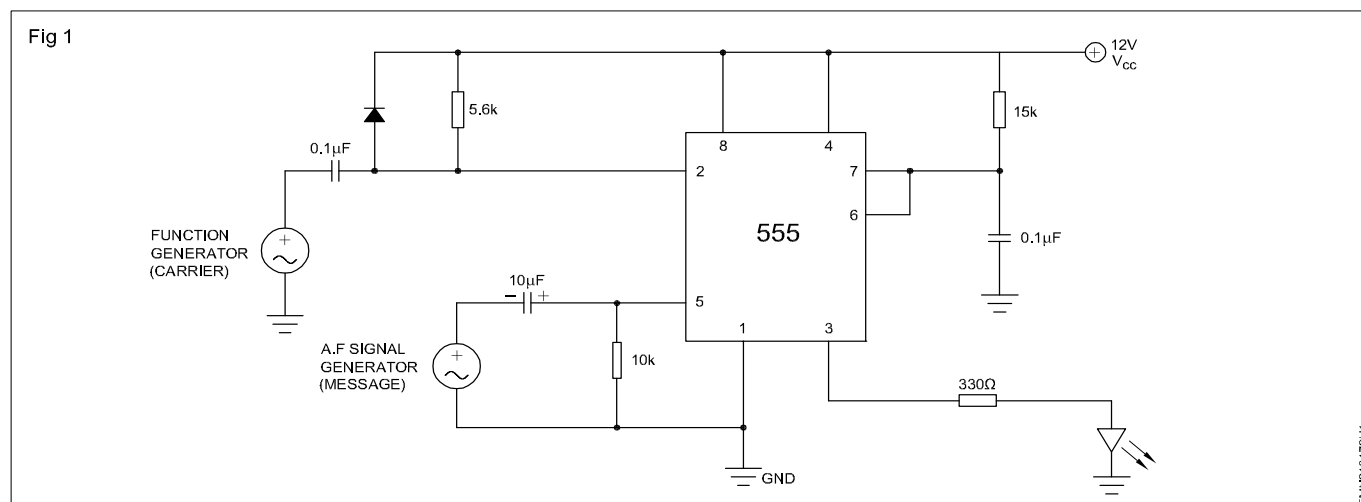

- 7 Get the result checked by the Instructor.

